


Tutorial 5 report

EE5311 (Digital IC design)


- Amogh G. Okade (EP22B020)


Question 1

Part a – Rising transition at D (and Q)

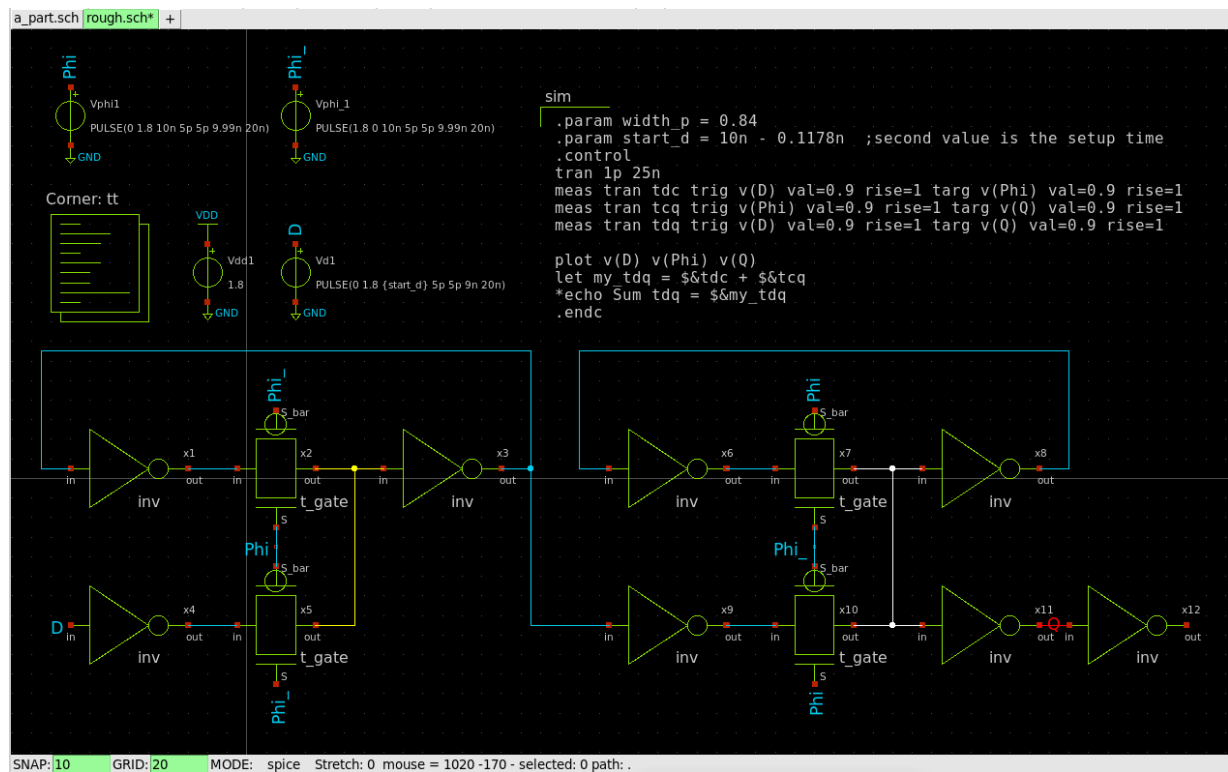


 - Plot of the input (D) vs output (Q) when t_{DC} is the setup time –



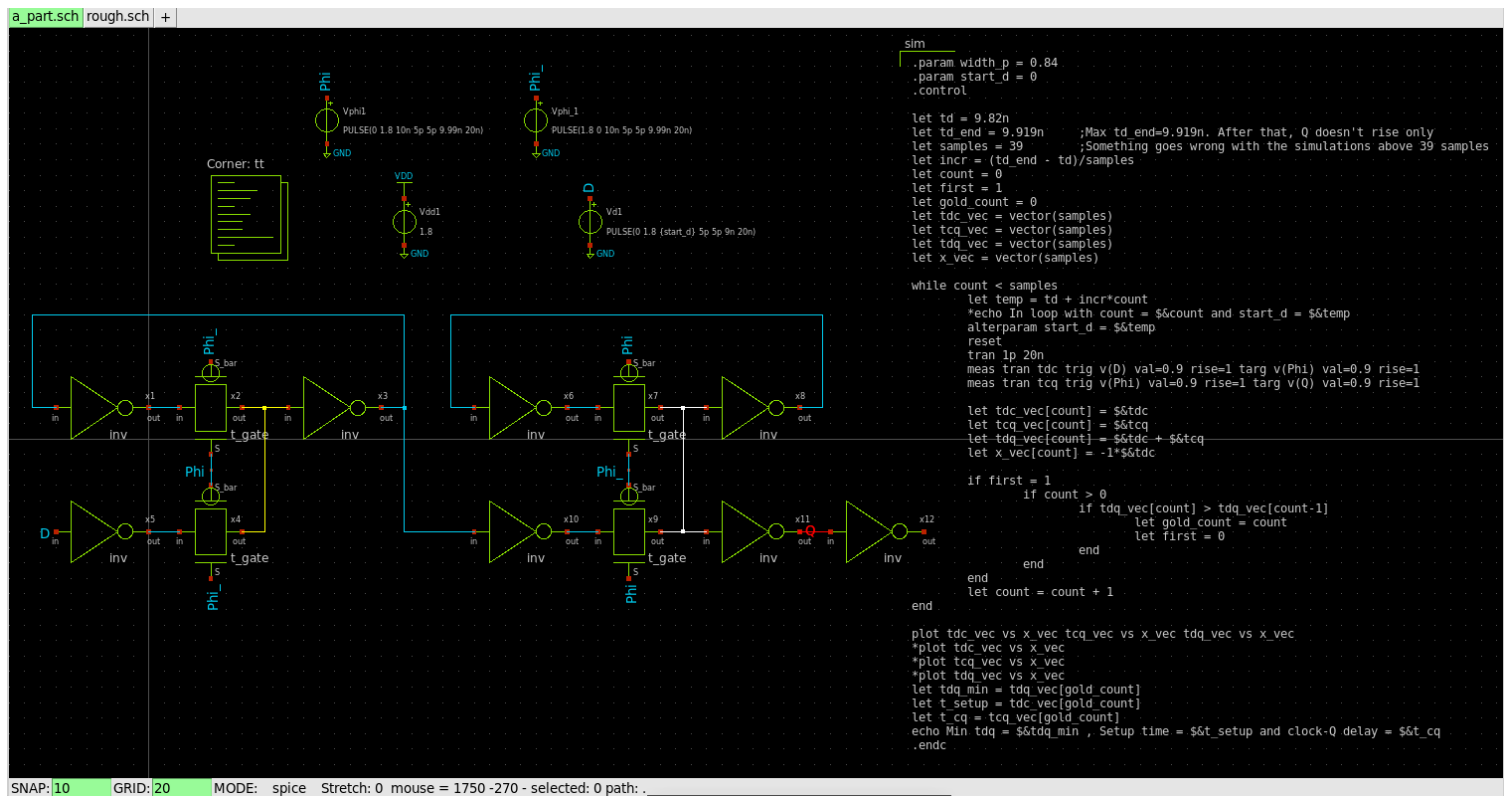

 - Plot showing the variation of t_{DC} , t_{CQ} and t_{DQ} for different values of t_{DC} –



- Values (from simulation)

```

tdc = 1.004047e-10 targ= 1.000250e-08 trig= 9.884700e-09
Min tdq = 2.13836E-10 , Setup time = 1.1654E-10 and clock-Q delay = 9.72958E-11
ngspice 9 -> █

```

- Minimum t_{DQ} = 0.213836 ns
- Setup time = 0.11654 ns
- Clock-Q delay = 97.2958 ps

- Accurate values (from probing around the simulated t_{setup})


```

tdc = 1.178000e-10 targ= 1.000250e-08 trig= 9.884700e-09
tcq = 9.601704e-11 targ= 1.009852e-08 trig= 1.000250e-08
tdq = 2.138170e-10 targ= 1.009852e-08 trig= 9.884700e-09
ngspice 9 -> █


```


- Minimum t_{DQ} = 0.213817 ns
- Setup time = 0.1178 ns
- Clock-Q delay = 96.01704 ps

Part b – Falling transition at D (and Q)

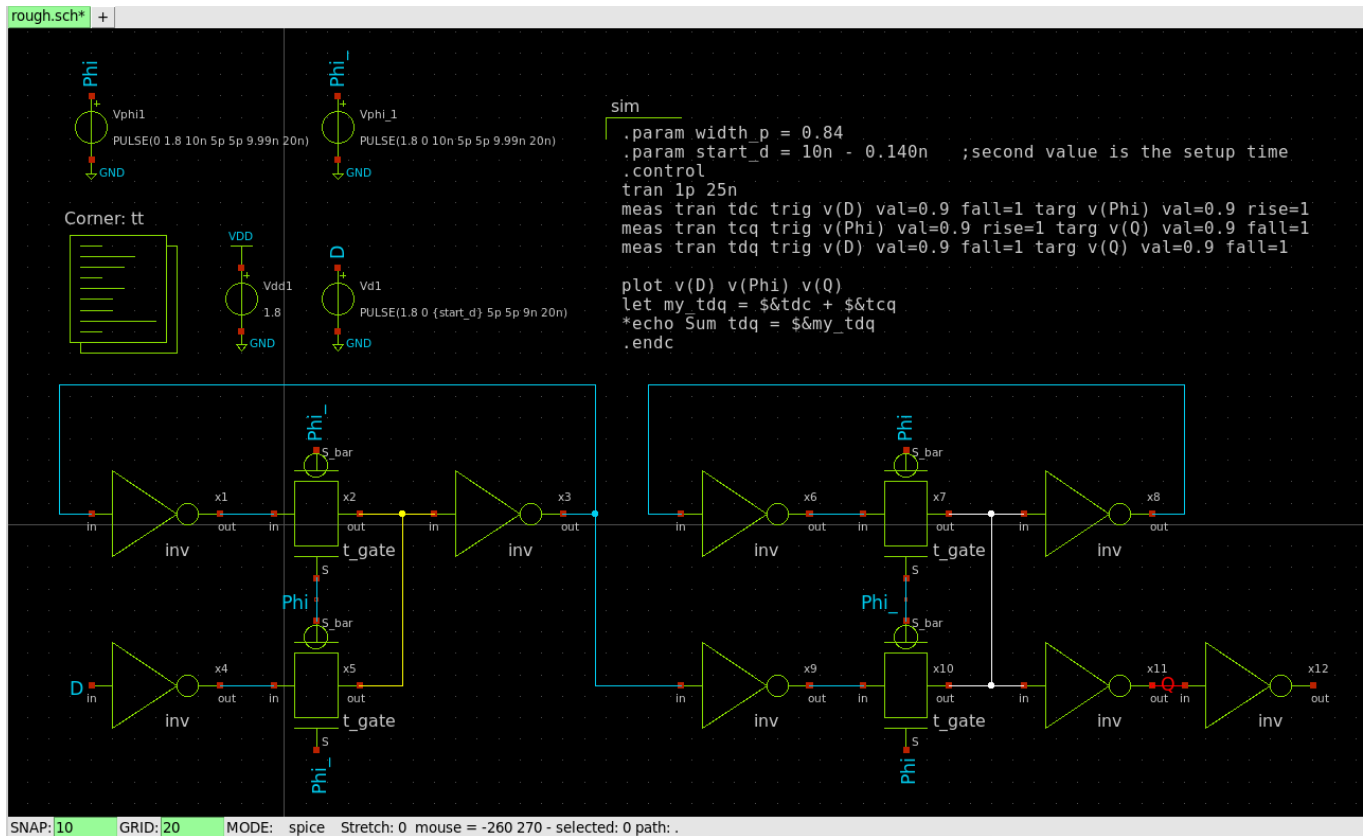


 - Plot of the input (D) vs output (Q) when t_{DC} is the setup time –



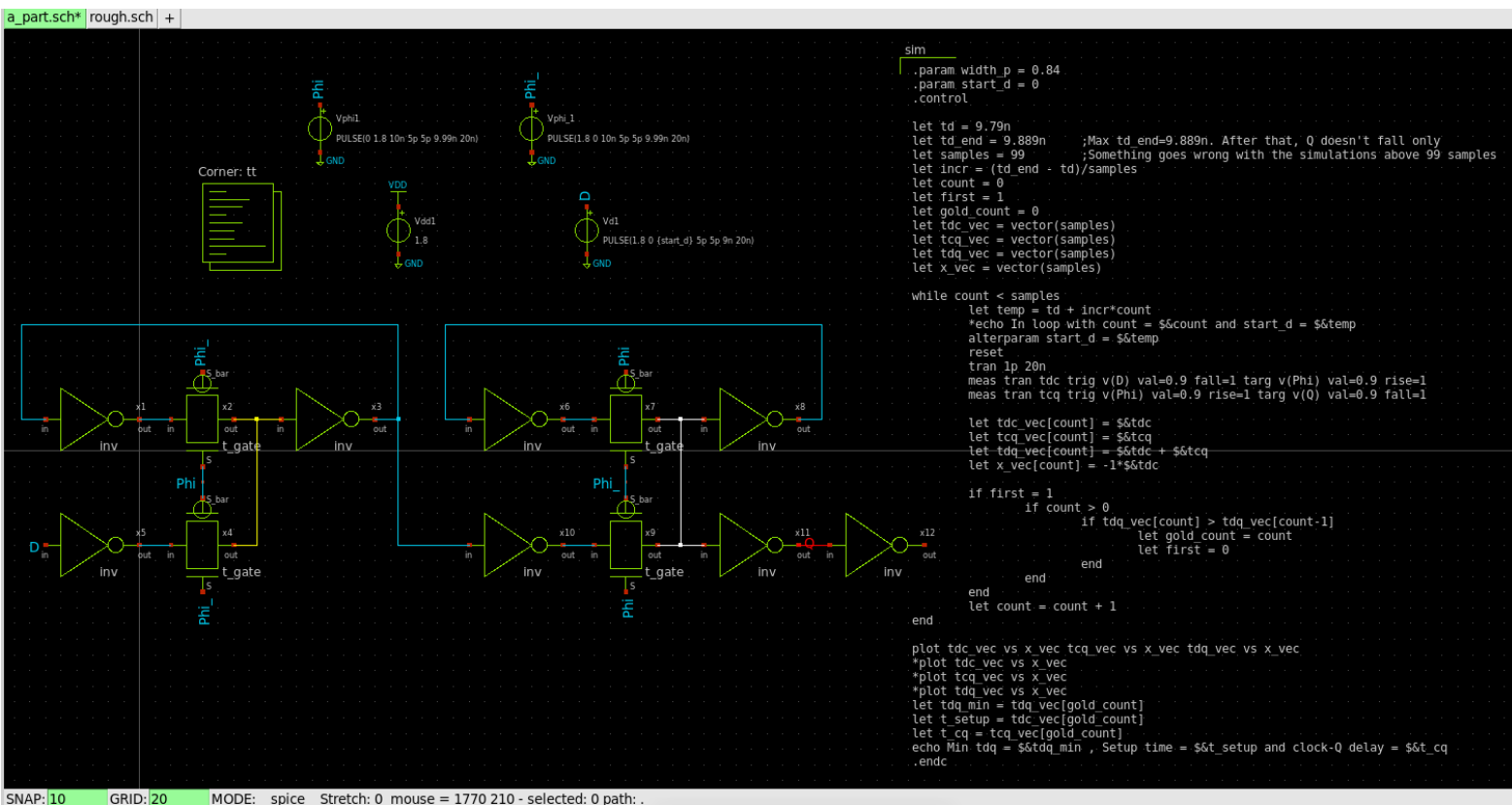

 - Plot showing the variation of t_{DC} , t_{CQ} and t_{DQ} for different values of t_{DC} –



- Values (from simulation)

```

Min tdq = 2.70318E-10 , Setup time = 1.39E-10 and clock-Q delay = 1.31318E-10
ngspice 11 ->

```

- Minimum t_{DQ} = 0.270318 ns
- Setup time = 0.1390 ns
- Clock-Q delay = 0.131318 ns

- Accurate values (from probing around the simulated t_{setup})

```

NO. of data rows = 25000
tdc                = 1.400000e-10 targ= 1.000250e-08 trig= 9.862500e-09
tcq                = 1.302994e-10 targ= 1.013280e-08 trig= 1.000250e-08
tdq                = 2.702994e-10 targ= 1.013280e-08 trig= 9.862500e-09
ngspice 11 -> █

```

- Minimum $t_{\text{DQ}} = 0.270299$ ns
- Setup time = 0.1400 ns
- Clock-Q delay = 0.130299 ns