

Tutorial 3 report

EE5311 (Digital IC design)

- Amogh G. Okade (EP22B020)

Question 1

- In saturation, the PMOS current, $I_p = \frac{1}{2} k_p \text{cox}_p (W/L)_p (V_{DD} - V_{in} - V_{tp})^2$
- In saturation, the NMOS current, $I_n = \frac{1}{2} k_n \text{cox}_n (W/L)_n (V_{in} - V_{tn})^2$
- If the threshold voltage of the inverter, $V_{th} = V_{DD}/2$, then, at $V_{in} = V_{DD}/2$, $V_{out} = V_{DD}/2$ and the PMOS and NMOS will have equal saturation currents.
- Thus,

$$\frac{1}{2} k_p \left(\frac{V_{DD}}{2} - V_{tp} \right) = \frac{1}{2} k_n \left(\frac{V_{DD}}{2} - V_{tp} \right)$$

Therefore,

$$k_p = k_n$$

$$\mu_p \text{cox}_p \left(\frac{W}{L} \right)_p = \mu_n \text{cox}_n \left(\frac{W}{L} \right)_n$$


Setting $(W/L)_n = (0.42/0.15)$ and substituting the other known constants, we get

$$0.009 \times 8.16 \times \left(\frac{W}{L} \right)_p = \frac{0.025 \times 8.34 \times 0.42}{0.15}$$


Solving, we get

$$\left(\frac{W}{L} \right)_p = \frac{1.19}{0.15}$$

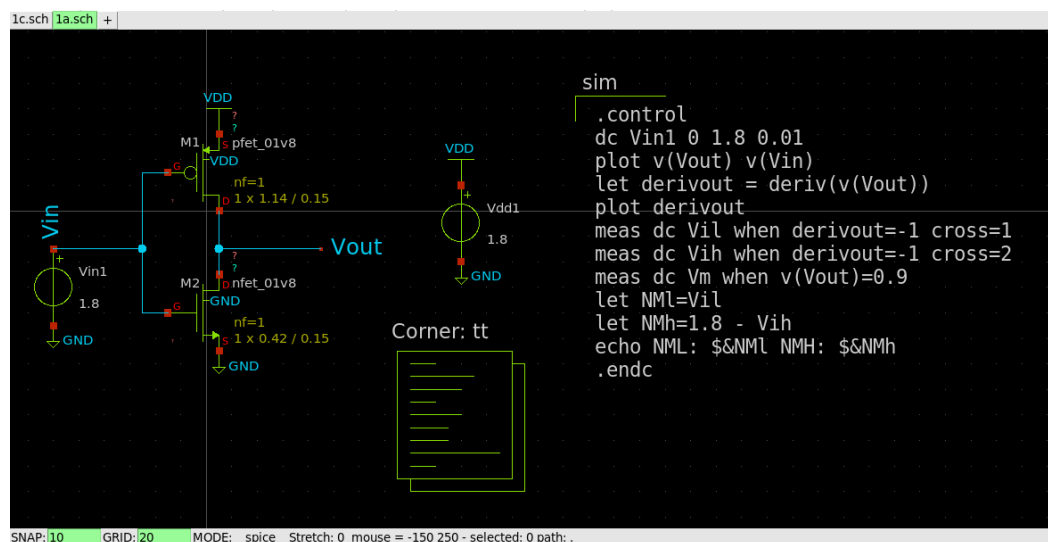However, for simulating with values around the calculated one, we may find that $(W/L)_p = (1.14/0.15)$ yields more accurate results for $V_{DD} = 1.8V$.




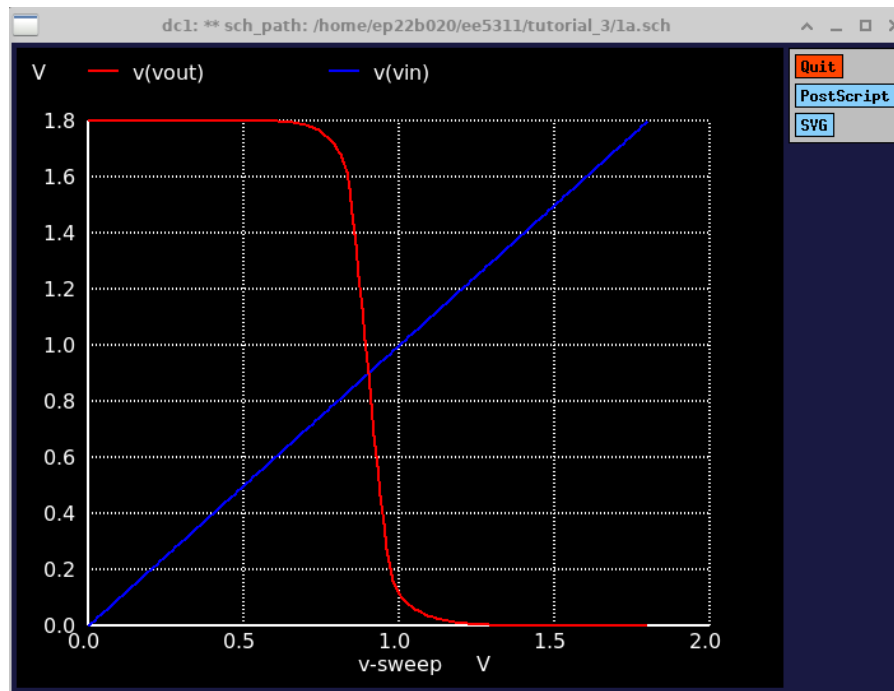- Plot of the DC transfer characteristics (V_{out} vs V_{in}):-



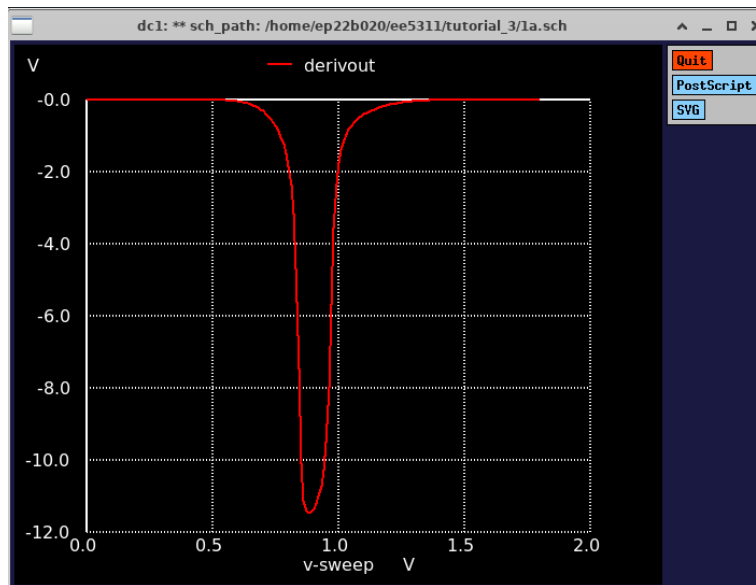Part a)

- Plot of the derivative of the output voltage vs V_{in} –



- Noise margins –
NML = 0.768, NMH = 0.773

```
Using SPARSE 1.3 as Direct Linear Solver
Reference value : 0.00000e+00
No. of Data Rows : 181
vil      = 7.680573e-01
vih      = 1.026838e+00
vm       = 9.002006e-01
NML: 0.768057 NMH: 0.773162
ngspice 6 -> []
```

Part b)


- From the equation balancing the saturation currents at $V_{in} = V_{th}$

$$k_p = k_n \frac{(V_{th} - V_{tp})}{(V_{DD} - V_{th} - V_{tp})}$$


we can clearly see that if $(W/L)_p$ is increased (k_p is increased), the inverter threshold V_{th} also increases, and vice-versa for when $(W/L)_p$ is decreased.

- When $(W/L)_p$ is increased, we also notice that NML increases, while NMH decreases. The converse can be said for the case where $(W/L)_p$ is decreased.

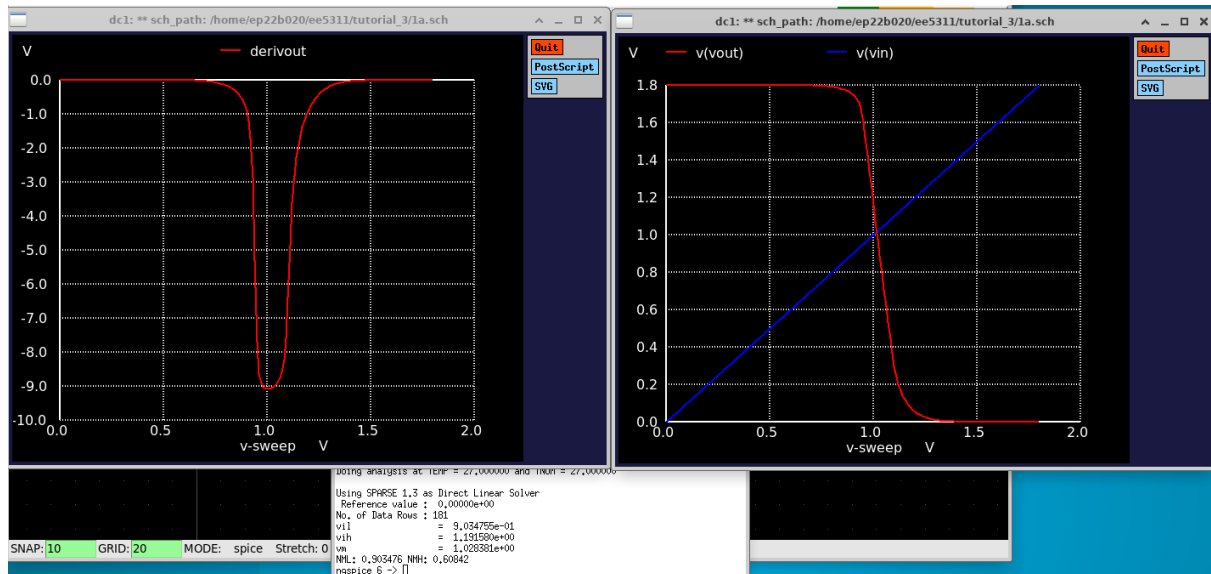
- Plot of the derivative of Vout and plot of Vout vs Vin when $(W/L)_p$ is increased by a factor of 10 (that is, $(W/L)_p = (11.4/0.15)$) –



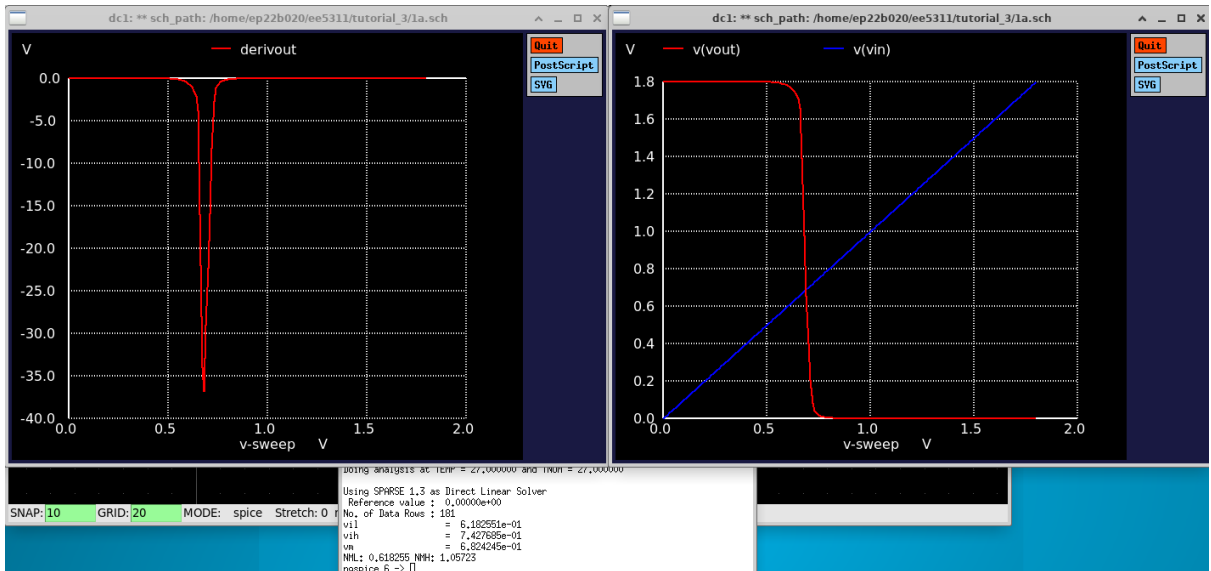
- Plot of the derivative of Vout and plot of Vout vs Vin when $(W/L)_p$ is decreased by a factor of 10 (that is, $(W/L)_p = (1.14/1.5)$) –




Part c)

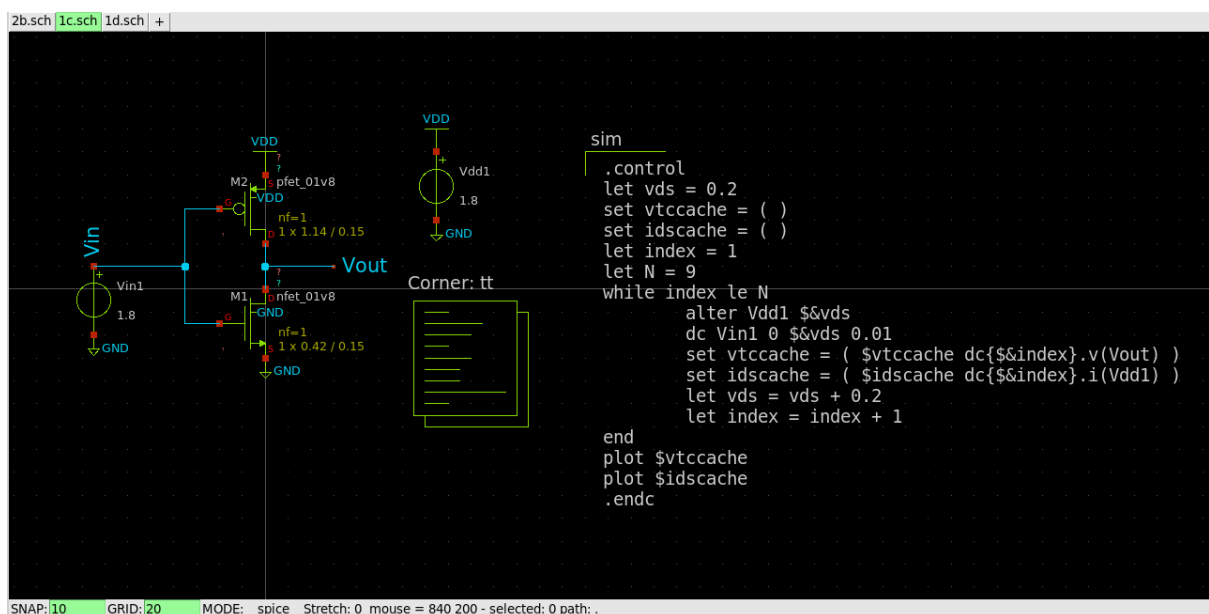

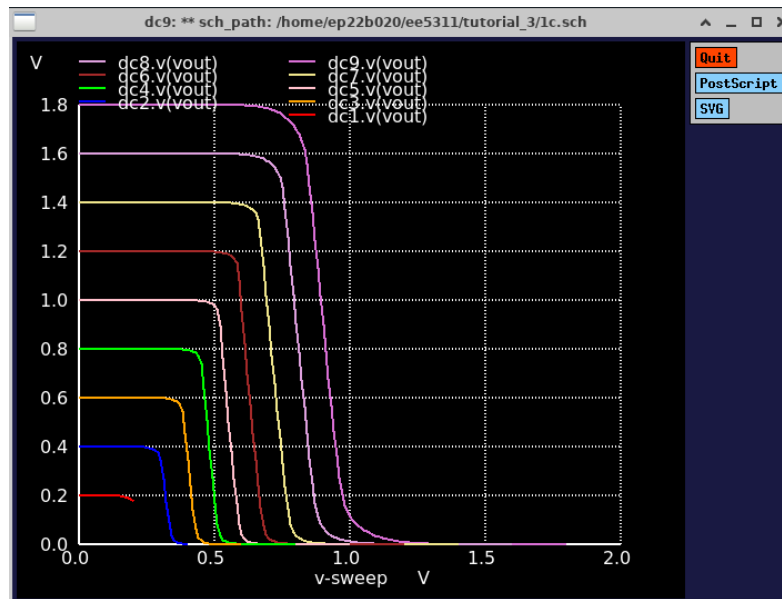
- Plot of the DC transfer characteristics (V_{out} vs V_{in}) for V_{DD} ranging from 0.2V to 1.8V –



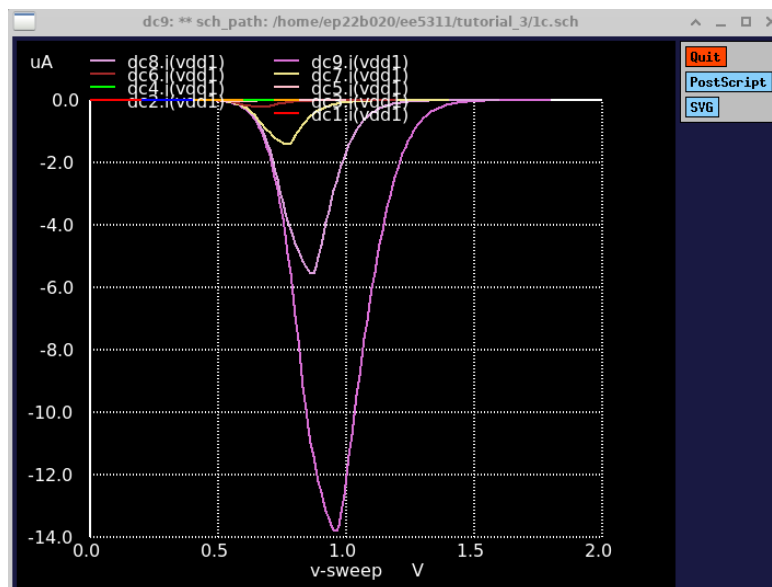
- Plot of I_{DS} vs V_{in} for V_{DD} ranging from 0.2V to 1.8V –



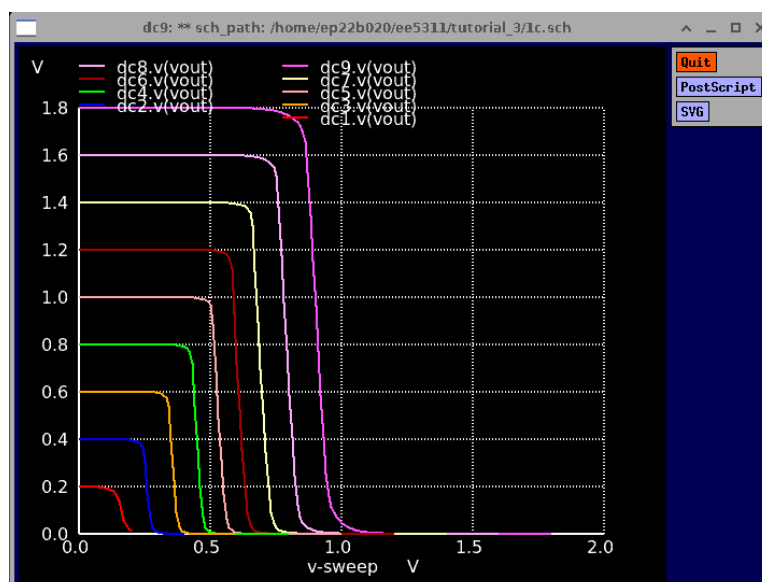
- For $V_{DD} = 0.2V$, it can't be used as an inverter.
The PMOS length can be increased slightly (and the width fine-tuned) to turn it into an inverter. For $(W/L)_p = (5/0.18)$, we get –



Part d)

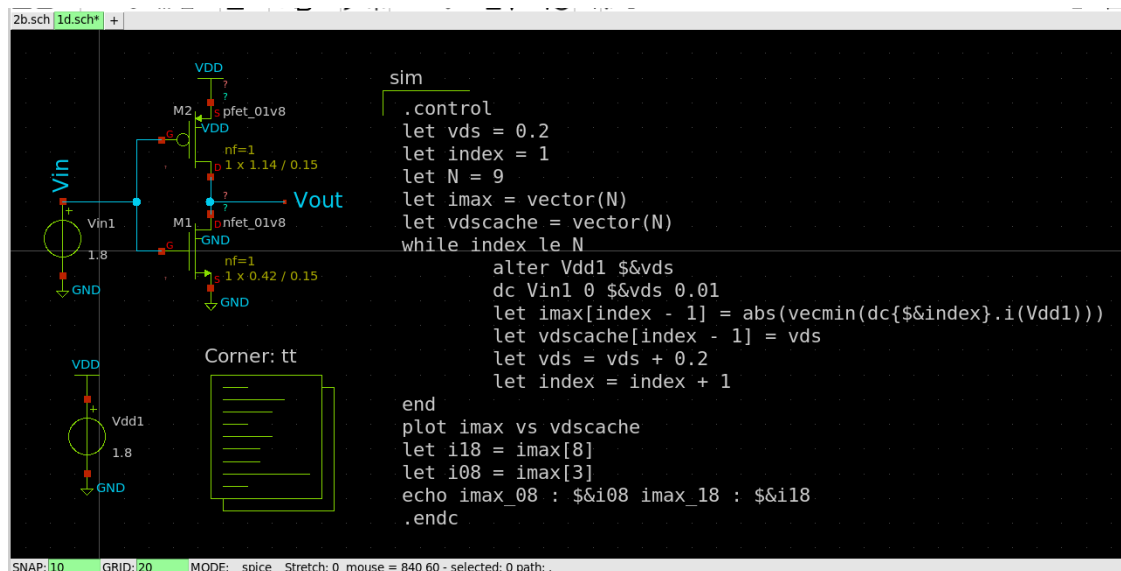

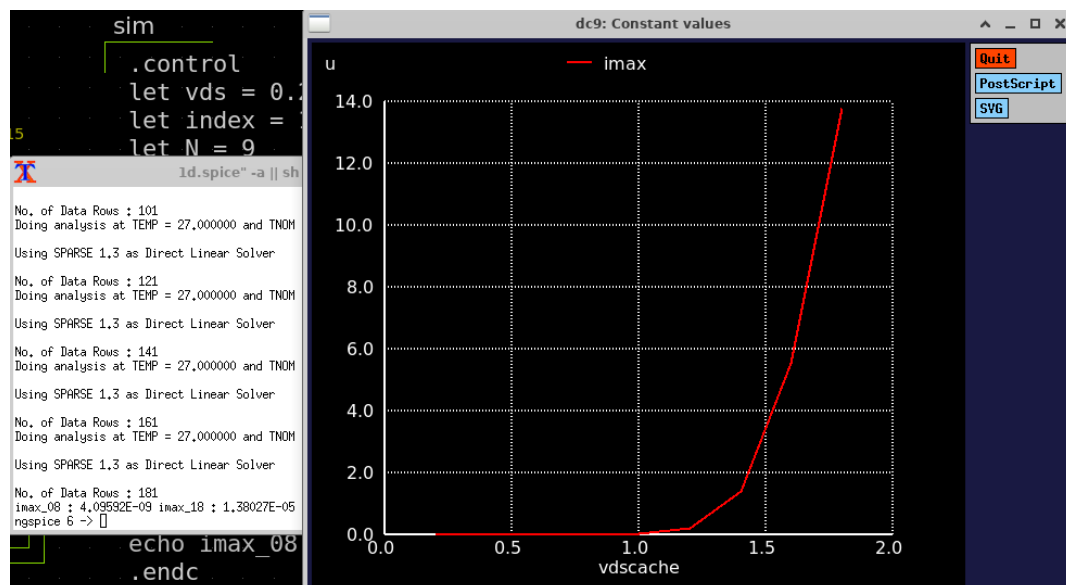- Plot of the peak I_{DS} for different values of V_{DD} –



- From the plot, peak $I_{DS} = 4.09\text{nA}$ for $V_{DD} = 0.8\text{V}$ and 13.8uA for $V_{DD} = 1.8\text{V}$.
- The analytical values are-
For $V_{DD} = 0.8\text{V}$, peak $I_{DS} = 0$, since both MOSFETs are cutoff at all times.
For $V_{DD} = 1.8\text{V}$, assuming that the peak I_{DS} occurs at $V_{in} = V_{out} = V_{th}$, we get (from the NMOS saturation current equation)

$$I_{ds, \text{peak}} = \frac{1}{2} k_n (0.9 - 0.7)^2 (1 + 0.2 \times 0.9) = 13.778\text{uA}$$

Question 2

- At $V_{in} = V_{DD}$, $V_{out} = V_{OL}$
- For these conditions (and assuming $V_{OL} = 0.1\text{V}$), we find that the PMOS is in triode and the NMOS is in saturation.
- Balancing the currents for the above conditions, we get

$$\frac{1}{2} k_p (V_{DD} - V_{tp})^2 = k_n \left(V_{DD} - V_{tn} - \frac{V_{OL}}{2} \right) V_{OL}$$

On solving further, we get

$$k_n \times V_{OL}^2 - V_{OL} \times 2k_n (V_{DD} - V_{tn}) + k_p \times (V_{DD} - V_{tp})^2 = 0$$

$$V_{OL} = V_{DD} - V_{tn} - \sqrt{(V_{DD} - V_{tn})^2 - \frac{k_p}{k_n} (V_{DD} - V_{tp})^2}$$

For $V_{OL} = 0.1V$, $V_{DD} = 1.8V$ and $V_{tn} = V_{tp} = 0.7V$, we get

$$\frac{k_p}{k_n} = \frac{0.21}{1.21}$$

$$\frac{\mu_p \text{COX}_p \left(\frac{W}{L}\right)_p}{\mu_n \text{COX}_n \left(\frac{W}{L}\right)_n} = \frac{0.21}{1.21}$$


Substituting for the known constants, we get

$$\frac{0.009 \times 8.16 \left(\frac{W}{L}\right)_p}{0.025 \times 8.34 \left(\frac{W}{L}\right)_n} = \frac{0.21}{1.21}$$


$$\left(\frac{W}{L}\right)_p = 0.4927 \times \left(\frac{W}{L}\right)_n$$

For $(W/L)_n = (0.42/0.15)$, we get
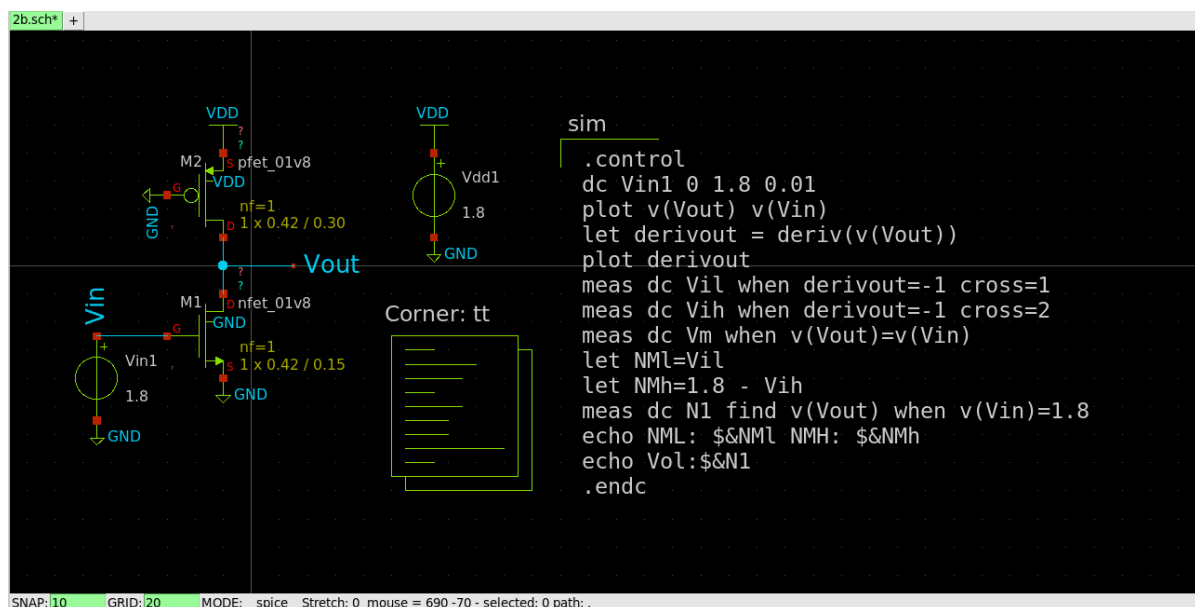
$$\left(\frac{W}{L}\right)_p = \frac{0.42}{0.3044}$$



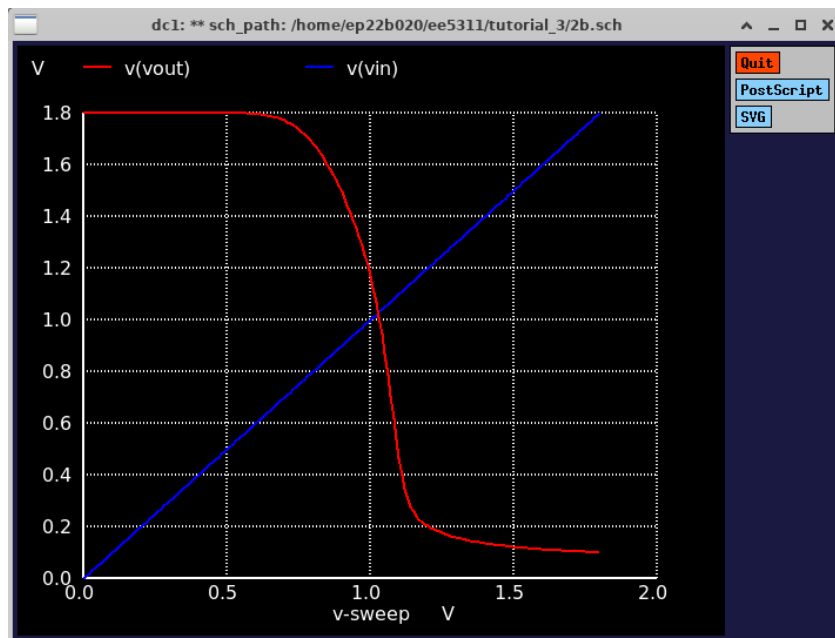- Plot of the DC transfer characteristics (Vout vs Vin) –




Part a)

- We see that the inverter threshold is 1.03V.

```
Using SPARSE 1.3 as Direct Linear Solver
Reference value : 0.00000e+00
No. of Data Rows : 181
vil          = 7.635257e-01
vih          = 1.177218e+00
vm          = 1.027268e+00
n1          = 1.001355e-01
NML: 0.763526 NMH: 0.622782
Vol:0.100136
ngspice 6 -> █
```

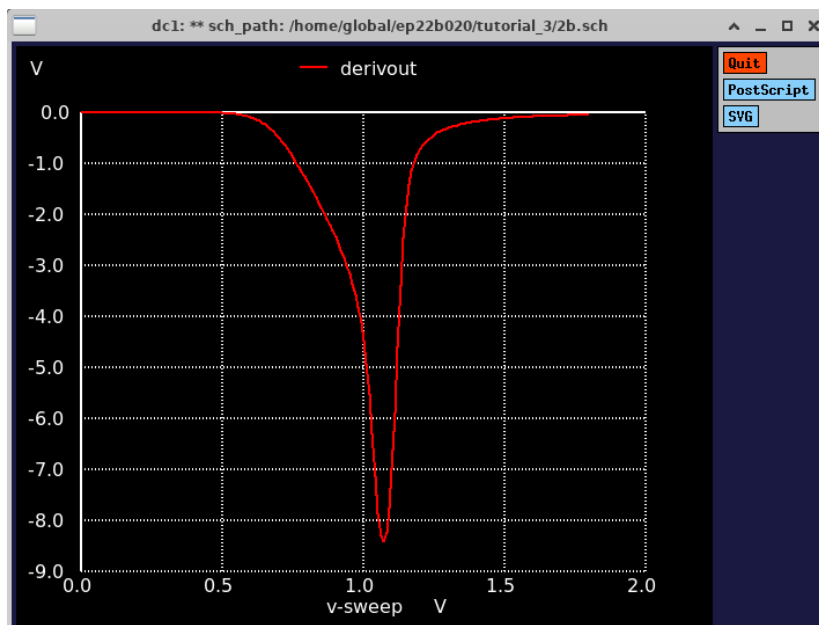Part b)

- Plot of the derivative of Vout vs Vin –



- Note that the value of Vout when Vin = 1.8V is 0.100136V, which is almost the desired 0.1V for the value of V_{OL} .
- $NML = 0.763V$, $NMH = 0.623V$.
- Analytically,

$$NML = VIL = V_{tn} + \frac{k_p}{k_n} (V_{out} - V_{tp})$$

Approximately,

$$NML = 0.7 + \frac{0.21}{1.21} (1.8 - 0.7) = 0.891V$$


Also,

$$NMH = VDD - V_{IH} = VDD - V_{tn} - \frac{2}{\sqrt{3}} \sqrt{\frac{k_p}{k_n}} (VDD - V_{tp})$$

Which approximately gives

$$NMH = 1.8 - 0.7 - \frac{2}{\sqrt{3}} \sqrt{\frac{0.21}{1.21}} (1.8 - 0.7) = 0.571V$$

Part c)

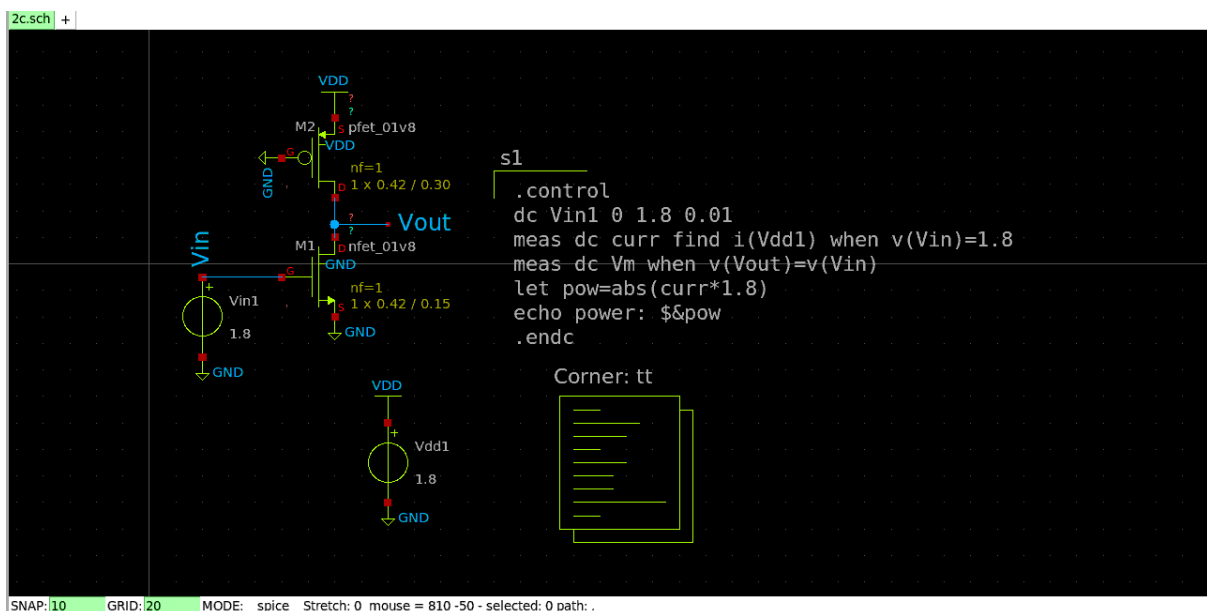

```
Using SPARSE 1.3 as Direct Linear Solver
Reference value : 0.00000e+00
No. of Data Rows : 181
curr              = -3.420985e-05
vm                = 1.027268e+00
power: 6.15777E-05
ngspice 6 -> █
```

- The simulated value of the power dissipated is 61.578uW.
- Analytically, considering the triode current through the NMOS, we get

$$I_{ds} = k_n \left(VDD - V_{tn} - \frac{V_{ds}}{2} \right) V_{ds} (1 + \lambda V_{ds}) = 64.05\mu A \quad (\text{for } V_{ds} = V_{ol} = 0.1V)$$

Thus, the power will be $I_{ds} \times 1.8 = 115.29\mu W$ (analytical).