

# Digital Systems

## Tutorial 11

March-June 2023

1. Investigation the transition table of the figure below and determine all race conditions and whether they are critical or non-critical.

| $x_1 x_2$ |    | 00 | 01 | 11 | 10 |
|-----------|----|----|----|----|----|
| $y_1 y_2$ | 00 | 00 | 11 | 10 | 01 |
|           | 01 | 10 | 01 | 10 | 11 |
|           | 11 | 11 | 11 | 10 | 10 |
|           | 10 | 11 | 01 | 10 | 10 |

### Solution:

(a) In row  $y_1 y_2 = 00$ , transition from  $x_1 x_2 = 00 \rightarrow x_1 x_2 = 01$ :

possible transitions

$00 \rightarrow 11$

$00 \rightarrow 10 \rightarrow 01$

$00 \rightarrow 01$

stable states are different  $\Rightarrow$  critical race condition

(b) In row  $y_1 y_2 = 01$ , transition from  $x_1 x_2 = 01 \rightarrow x_1 x_2 = 00$ :

possible transitions

$01 \rightarrow 10 \rightarrow 11$

$01 \rightarrow 00$

$01 \rightarrow 11$

stable states are different  $\Rightarrow$  critical race condition

(c) In row  $y_1 y_2 = 11$ , transition from  $x_1 x_2 = 01 \rightarrow x_1 x_2 = 11$ :

possible transitions

$01 \rightarrow 10$

$01 \rightarrow 00 \rightarrow 01$

$01 \rightarrow 11 \rightarrow 01$

stable states are same  $\Rightarrow$  non-critical race condition

(d) In row  $y_1 y_2 = 10$ , transition from  $x_1 x_2 = 11 \rightarrow x_1 x_2 = 01$ :

possible transitions

$10 \rightarrow 01$

$10 \rightarrow 00 \rightarrow 11$

$10 \rightarrow 11$

stable states are different  $\Rightarrow$  critical race condition

In following table, all races and type of races are shown.

| $x_1 x_2$ | 00 | 01 | 11 | 10 |                            |
|-----------|----|----|----|----|----------------------------|
| $y_1 y_2$ |    |    |    |    |                            |
| 00        | 00 | 11 | 10 | 01 | Critical                   |
| 01        | 10 | 01 | 10 | 11 | Critical Non-critical race |
| 11        | 11 | 11 | 10 | 10 |                            |
| 10        | 11 | 01 | 10 | 10 | Critical                   |

2. Determine all race conditions and are they critical or non-critical.

| $x_1 x_2$ | 00 | 01 | 11 | 10 |
|-----------|----|----|----|----|
| $y_1 y_2$ |    |    |    |    |
| 00        | 10 | 00 | 11 | 10 |
| 01        | 01 | 00 | 10 | 10 |
| 11        | 01 | 00 | 11 | 11 |
| 10        | 11 | 00 | 10 | 10 |

### Solution:

(a) In row  $y_1 y_2 = 00$ , transition from  $x_1 x_2 = 01 \rightarrow x_1 x_2 = 11$ :

possible transitions

$00 \rightarrow 11$

$00 \rightarrow 10$

$00 \rightarrow 01 \rightarrow 10$

stable states are different  $\Rightarrow$  critical race condition

(b) In row  $y_1 y_2 = 11$ , transition from  $x_1 x_2 = 11 \rightarrow x_1 x_2 = 01$ :

possible transitions

$11 \rightarrow 00$

$11 \rightarrow 10 \rightarrow 00$

$11 \rightarrow 01 \rightarrow 00$

stable states are same  $\Rightarrow$  non critical race condition

(c) In row  $y_1 y_2 = 01$ , transition from  $x_1 x_2 = 00 \rightarrow x_1 x_2 = 10$ :

possible transitions

$01 \rightarrow 10$

$01 \rightarrow 00 \rightarrow 10$


$01 \rightarrow 11 \rightarrow 11$

stable states are different  $\Rightarrow$  critical race condition


In the following table, all races and types of races are shown.

| $x_1 x_2$ | 00 | 01 | 11 | 10 |                   |
|-----------|----|----|----|----|-------------------|
| 00        | 10 | 00 | 11 | 10 | Critical race     |
| 01        | 01 | 00 | 10 | 10 | Critical race     |
| 11        | 01 | 00 | 11 | 11 | Non critical race |
| 10        | 11 | 00 | 10 | 10 |                   |

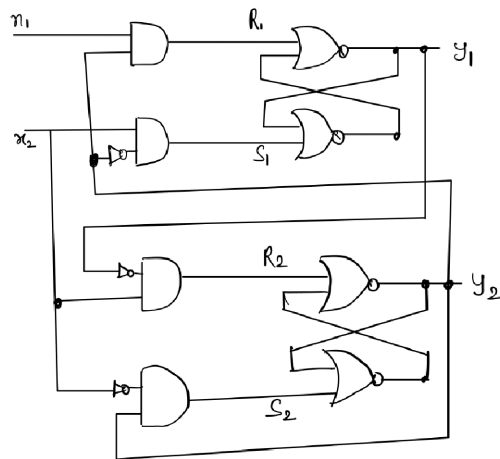3. Analyze the SR latch circuit and  
(a) derive the transition table (b) race condition



**Solution:**

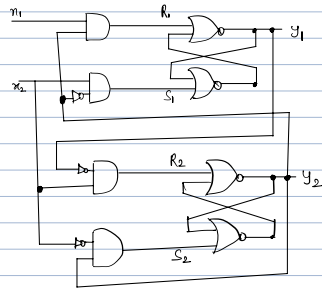

The boolean function of S and R inputs,

$$S_1 = x_2 y_2' \quad S_2 = x_1' y_2$$

$$R_1 = x_1 y_2 \quad R_2 = x_2 y_1'$$

We check the  $S_i R_i = 0$ , to ensure the proper operation of circuit,

$$S_1 R_1 = x_2 y_2' \cdot x_1 y_2 = 0$$

$$S_2 R_2 = x_1' y_2 \cdot x_2 y_1' = 0$$

The excitation function are derived from relation,

$$Y = S + R'Y'$$

$$Y_1 = x_2 y_2' + (x_1 y_2)' y_1$$

$$= x_2 y_2' + x_1' y_2 + y_2' y_1$$

$$Y_2 = x_1' y_2 + y_1 y_2$$

| $y_1 y_2$ \ $x_1 x_2$ | 00 | 01 | 11 | 10 |
|-----------------------|----|----|----|----|
| 00                    | 0  | 1  | 1  | 0  |
| 01                    | 0  | 0  | 0  | 0  |
| 11                    | 1  | 1  | 0  | 0  |
| 10                    | 1  | 1  | 1  | 1  |

Map for  $Y_1$

| $y_1 y_2$ \ $x_1 x_2$ | 00 | 01 | 11 | 10 |
|-----------------------|----|----|----|----|
| 00                    | 0  | 0  | 0  | 0  |
| 01                    | 1  | 0  | 0  | 1  |
| 11                    | 1  | 1  | 1  | 1  |
| 10                    | 0  | 0  | 0  | 0  |

Map for  $Y_2$

| $y_1 y_2$ \ $x_1 x_2$ | 00 | 01 | 11 | 10 |
|-----------------------|----|----|----|----|
| 00                    | 00 | 10 | 10 | 00 |
| 01                    | 01 | 00 | 00 | 01 |
| 11                    | 11 | 11 | 01 | 01 |
| 10                    | 10 | 10 | 10 | 10 |


Transition table

- There is no race

4. Find a circuit that has no static hazards and implements the boolean functions.  
 $F(A, B, C, D) = \Sigma(0, 2, 6, 7, 8, 10, 12)$ .

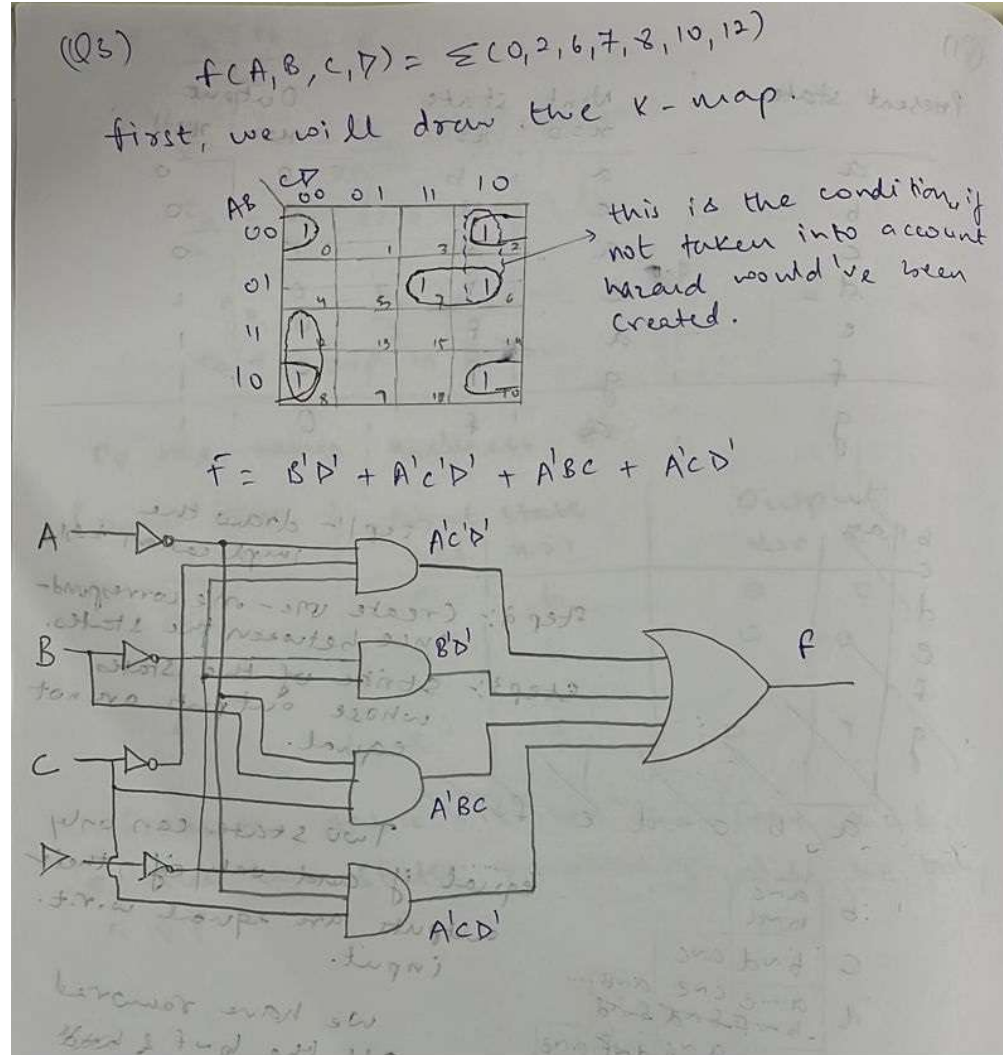**Solution:**


This is a static-1 hazard. Note: SOP = static-1 hazard, POS = static-0 hazards



5. Draw the logic diagram of the product of sums expression,  $Y = (x_1 + x_2')(x_2 + x_3)$ , find a way

to remove the hazard by adding one more OR gate.

**Solution:**

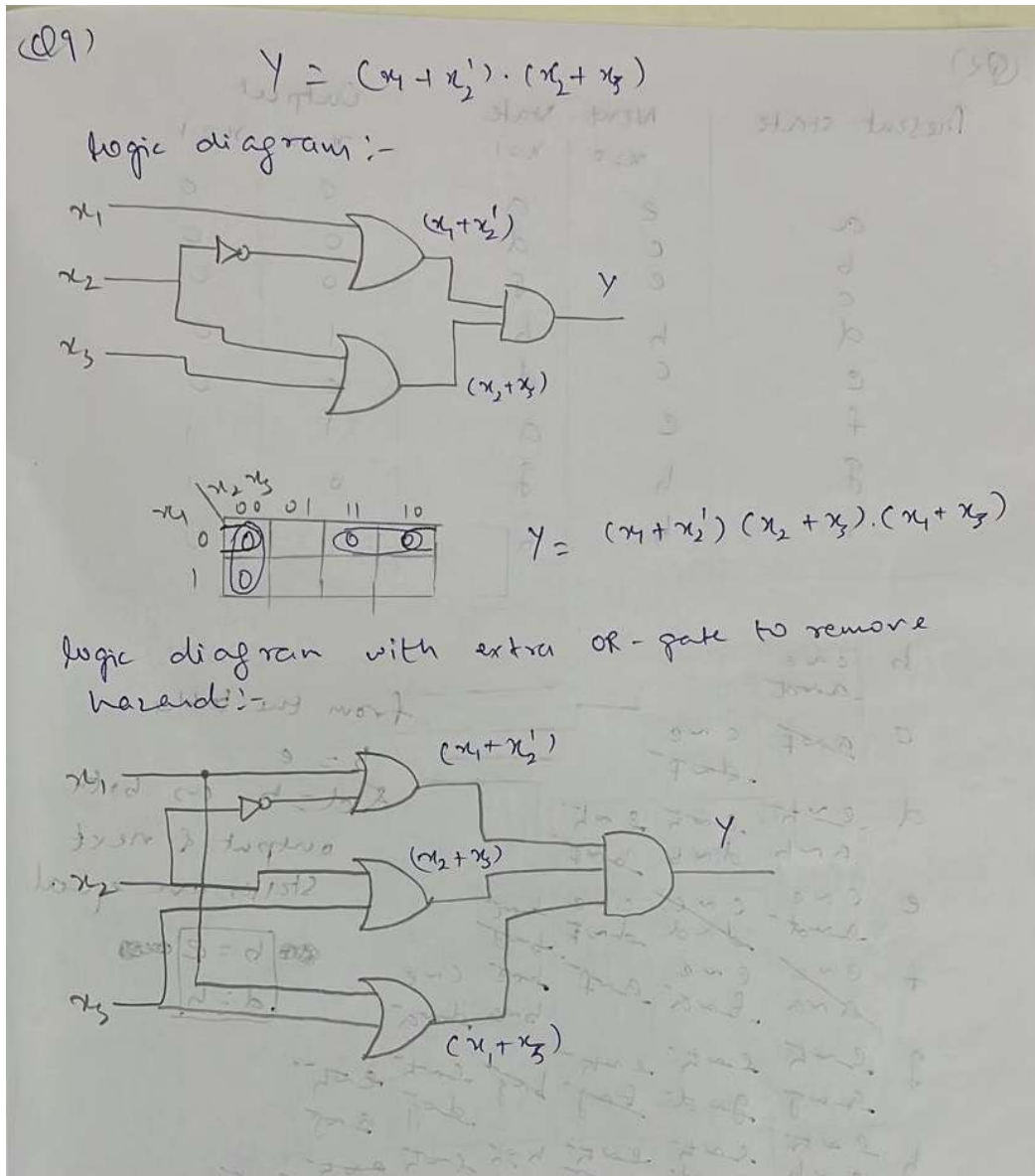

6. Obtain a primitive flow table for a circuit with two inputs,  $x_1$  and  $x_2$ , and one output,  $z$ , that satisfy the following two conditions:

- (a) The inputs  $x_1$  and  $x_2$  never changes simultaneously.
- (b) The output  $z$  is complemented if  $x_1 = 1$  and the  $x_2$  changes from 0 to 1. Otherwise, the output  $z$  remains unchanged under any other input condition.

**Solution:**

Given,

$x_1$  &  $x_2 \rightarrow$  inputs       $z \rightarrow$  output  
 $x_1 = 1$  &  $x_2 = 0 \rightarrow 1 \Rightarrow z = \bar{z}$  { Output is complemented  
 other i/p cond-n  $\Rightarrow z = z$  { No change  
 $x_1$  &  $x_2 =$  Not change simultaneously

• Specification of total state:-

| State | Input |       | Output | Comments             | Next state (NS) |
|-------|-------|-------|--------|----------------------|-----------------|
|       | $x_1$ | $x_2$ | $z$    |                      |                 |
| a     | 1     | 0     | 0      | Initial output $z=0$ | NS: e or b      |
| b     | 1     | 1     | 1      | After state a        | NS: h or c      |
| c     | 1     | 0     | 1      | Initial output $z=1$ | NS: g or d      |
| d     | 1     | 1     | 0      | After state c        | NS: f or a      |
| e     | 0     | 0     | 0      | After states a, f    | NS: f or a      |
| f     | 0     | 1     | 0      | After state d, e     | NS: e or d      |
| g     | 0     | 0     | 1      | After states c       | NS: h or c      |
| h     | 0     | 1     | 1      | After states b, g    | NS: g or b      |

• Primitive flow table:  
 $x_1, x_2$

|   | 00   | 01   | 11   | 10   |
|---|------|------|------|------|
| a | e, - | -, - | b, - | Ⓐ, 0 |
| b | -, - | h, - | Ⓑ, 1 | c, - |
| c | g, - | -, - | d, - | Ⓒ, 1 |
| d | -, - | f, - | Ⓓ, 0 | a, - |
| e | Ⓔ, 0 | f, - | -, - | a, - |
| f | e, - | Ⓕ, 0 | d, - | -, - |
| g | Ⓖ, 1 | h, - | -, - | c, - |
| h | g, - | Ⓖ, 1 | b, - | -, - |

7. Obtain a primitive flow table for a fundamental mode operated circuit meeting the following requirements:
- There are two inputs,  $x_1$  and  $x_2$ , and single output,  $z$ .
  - The output  $z$  is always 0, when  $x_1 = 0$ , independent of the  $x_2$  value.
  - The output  $z$  becomes 1 if  $x_2$  changes while  $x_1 = 1$  and it remains until  $x_1$  becomes 0 again.

**Solution:**



Given,

$x_1 \text{ \& } x_2 \rightarrow \text{inputs}$

$z \rightarrow \text{output}$

$x_1=0 \Rightarrow z=0$

$x_1=1 \text{ \& } x_2 = \begin{matrix} 0 \rightarrow 1 \\ \text{or} \\ 1 \rightarrow 0 \end{matrix} \Rightarrow z=1$

- Specification of total states:

| State | Input |       | Output | Comments                      | Next state (NS)      |
|-------|-------|-------|--------|-------------------------------|----------------------|
|       | $x_1$ | $x_2$ | $z$    |                               |                      |
| a     | 1     | 0     | 0      | Initial output $z=0$          | NS: d or b           |
| b     | 1     | 1     | 1      | After state a                 | NS: d or c           |
| c     | 1     | 0     | 1      | After state b <del>or a</del> | NS: For <del>b</del> |
| d     | 0     | 1     | 0      | After state b or a            | NS: For e            |
| e     | 1     | 1     | 0      | After state d                 | NS: d or c           |
| f     | 0     | 0     | 0      | After states d, c or e        | NS: d or a           |

- Primitive flow table:

$x_1 x_2$

|   | 00     | 01     | 11     | 10     |
|---|--------|--------|--------|--------|
| a | -/-    | d, -   | b, -   | (a), 0 |
| b | -/-    | d, -   | (b), 1 | c, -   |
| c | f, -   | -/-    | b, -   | (c), 1 |
| d | f, -   | (a), 0 | e, -   | -/-    |
| e | -/-    | d, -   | (e), 0 | c, -   |
| f | (f), 0 | d, -   | -/-    | a, -   |

8. Implement the following flow table using (1) gates, (2) SR latch

$x_1 x_2$

|   | 00  | 01  | 11  | 10  |
|---|-----|-----|-----|-----|
| a | (a) | c   | b   | (a) |
| b | a   | c   | (b) | (b) |
| c | a   | (c) | (c) | b   |
| d | a   | (d) | (d) | a   |

**Solution:**

(1) using gates

Given,  $x_1, x_2 \rightarrow$  inputs

$a, b, c, d \rightarrow$  states

$s \quad a=00 \quad c=11$   
 $b=01 \quad d=10$

$\rightarrow$  let  $y_1, y_2 \rightarrow$  internal states

Thus the transition table is given as:

| $y_1 y_2 \backslash x_1 x_2$ | 00 | 01 | 11 | 10 |
|------------------------------|----|----|----|----|
| 00                           | 00 | 11 | 01 | 00 |
| 01                           | 00 | 11 | 01 | 01 |
| 11                           | 00 | 11 | 11 | 01 |
| 10                           | 00 | 11 | 11 | 00 |

Transition table

| $y_1 y_2 \backslash x_1 x_2$ | 00 | 01 | 11 | 10 |
|------------------------------|----|----|----|----|
| 00                           | 0  | 1  | 0  | 0  |
| 01                           | 0  | 1  | 0  | 0  |
| 11                           | 0  | 1  | 1  | 0  |
| 10                           | 0  | 1  | 1  | 0  |

map for  $y_1$


| $y_1 y_2 \backslash x_1 x_2$ | 00 | 01 | 11 | 10 |
|------------------------------|----|----|----|----|
| 00                           | 0  | 1  | 1  | 0  |
| 01                           | 0  | 1  | 1  | 1  |
| 11                           | 0  | 1  | 1  | 1  |
| 10                           | 0  | 1  | 1  | 0  |

map for  $y_2$

$\rightarrow$  Thus,  $y_1 = \bar{x}_1 x_2 + y_1 x_2$

$\& \quad y_2 = x_2 + x_1 y_2$

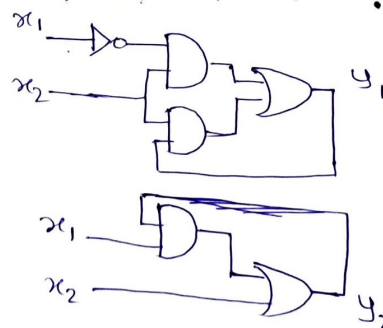$\rightarrow$  Thus implementation is given as:



(2) using SR latch

• Excitation table SR latch is :

→ Using the excitation table the  $y_1, y_2$  maps can be converted to SR as follows:

(NOR Gate S-R latch)

| $Q_n$ | $Q_n^+$ | S | R |
|-------|---------|---|---|
| 0     | 0       | 0 | x |
| 0     | 1       | 1 | 0 |
| 1     | 0       | 0 | 1 |
| 1     | 1       | x | 0 |

$S_1 = \overline{x_1} x_2$   
 $R_1 = \overline{x_2}$   
 $S_2 = x_2$   
 $R_2 = \overline{x_1} \overline{x_2}$


→ SR Implementation is:

9. Implement the following flow table using (1) gates, (2) D latch

|   |           |     |    |     |
|---|-----------|-----|----|-----|
|   | $x_1 x_2$ |     |    |     |
|   | 00        | 01  | 11 | 10  |
| a | (a)       | (a) | b  | d   |
| b | (b)       | c   | a  | d   |
| c | b         | (c) | d  | d   |
| d | a         | (d) | c  | (d) |

## Solution:


(1) using gates

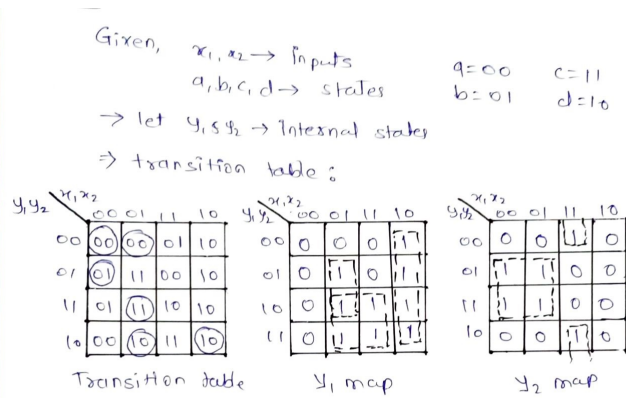

$$\Rightarrow y_1 = x_1 \bar{x}_2 + x_2 y_1 + y_2 x_2 \bar{x}_1$$

$$y_2 = \bar{x}_1 y_2 + \bar{y}_2 x_1 x_2$$

$\Rightarrow$  Circuit  $\rightarrow$

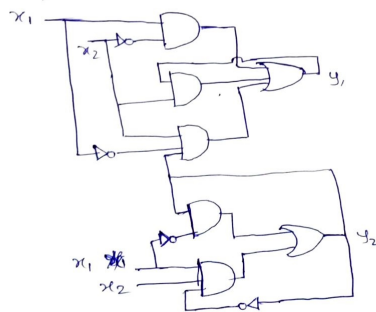

(2) using D latch

• Excitation table of D-latch is :

| $Q_n$ | $Q_{n+1}$ | D |
|-------|-----------|---|
| 0     | 0         | 0 |
| 0     | 1         | 1 |
| 1     | 0         | 0 |
| 1     | 1         | 1 |

→ Using the excitation table the  $y_1$  &  $y_2$  maps can be converted to  $D_1$  &  $D_2$  as follows:

$y_1, y_2$

|    |    |    |    |    |
|----|----|----|----|----|
|    | 00 | 01 | 11 | 10 |
| 00 | 0  | 0  | 0  | 1  |
| 01 | 0  | 1  | 0  | 1  |
| 11 | 0  | 1  | 1  | 1  |
| 10 | 0  | 1  | 1  | 1  |

$D_1$  map

$y_1, y_2$

|    |    |    |    |    |
|----|----|----|----|----|
|    | 00 | 01 | 11 | 10 |
| 00 | 0  | 0  | 1  | 0  |
| 01 | 1  | 1  | 0  | 0  |
| 11 | 1  | 1  | 0  | 0  |
| 10 | 0  | 0  | 1  | 0  |

$D_2$  map

⇒

$$D_1 = x_1 \bar{x}_2 + y_1 x_2 + y_2 \bar{x}_1 x_2$$

$$D_2 = y_2 \bar{x}_1 + \bar{y}_2 x_1 x_2$$

→ D latch implementation is

10. Design an asynchronous sequential circuit with two inputs ( $X_1$  and  $X_2$ ) and one output ( $Z$ ). Whenever the input  $X_2$  is 1, the input  $X_1$  is transferred to output  $Z$ . When  $X_2$  is 0; the output  $Z$  does not change for a change in  $X_1$ . Consider the fundamental mode of operation.

**Solution:**

Given,

$x_1, x_2 \rightarrow \text{inputs}$

$z \rightarrow \text{output}$

$x_2 = 1 \Rightarrow z = x_1$

$x_2 = 0 \Rightarrow z = z$

| States | Input |       | Output | Comments                           |
|--------|-------|-------|--------|------------------------------------|
|        | $x_1$ | $x_2$ | $z$    |                                    |
| a      | 0     | 0     | 0      | let initial cond <sup>n</sup> be a |
| b      | 0     | 1     | 0      | After <del>b</del> state a         |
| c      | 1     | 0     | 0      | After state a                      |
| d      | 1     | 1     | 1      | After states b, c                  |
| e      | 1     | 0     | 1      | After state d                      |
| f      | 0     | 0     | 1      | After state e                      |

• Specification of total states

→ Thus the primitive flow table can be drawn as:

|   | $x_1, x_2$ |        |        |        |
|---|------------|--------|--------|--------|
|   | 00         | 01     | 11     | 10     |
| a | (a), 0     | b, -   | - , -  | c, -   |
| b | a, -       | (b), 0 | d, -   | - , -  |
| c | a, -       | - , -  | d, -   | c, 0   |
| d | - , -      | b, -   | (d), 1 | e, -   |
| e | f, -       | - , -  | d, -   | (e), 1 |
| f | (f), 1     | b, -   | - , -  | e, -   |

→ The obtained flow table can be reduced to two variables by grouping similar states:

|             | 00         | 01         | 11         | 10         |
|-------------|------------|------------|------------|------------|
| $s_0 = abc$ | $(s_0, 0)$ | $(s_1, 0)$ | $(s_1, -)$ | $(s_0, 0)$ |
| $s_1 = def$ | $(s_1, 1)$ | $(s_0, -)$ | $(s_1, 1)$ | $(s_1, 1)$ |



→ Now assigning binary values to state

• transition diagrams

→ No extra states are needed (race-free)



→ The transition table & output map be written as


| S | $x_1 x_2$ |    |    |    |
|---|-----------|----|----|----|
|   | 00        | 01 | 11 | 10 |
| 0 | 0         | 0  | 1  | 0  |
| 1 | 1         | 0  | 1  | 1  |

| Z | $x_1 x_2$ |    |    |    |
|---|-----------|----|----|----|
|   | 00        | 01 | 11 | 10 |
| 0 | 0         | 0  | *  | 0  |
| 1 | 1         | *  | 1  | 1  |

$$S^+ = x_1 x_2 + S \bar{x}_2$$

$$Z = S \quad \text{(output)}$$

→ Implementation using gates

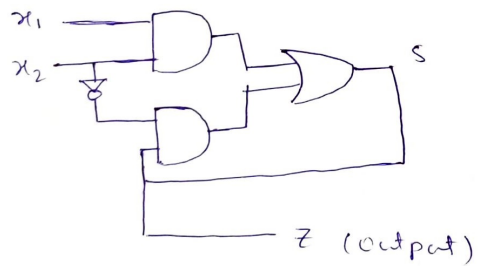

## Practice problems

11. Use the implication-table method, to reduce the state table.

| Present State | Next State |     | Output |     |
|---------------|------------|-----|--------|-----|
|               | X=0        | X=1 | X=0    | X=1 |
| a             | a          | b   | 0      | 0   |
| b             | c          | d   | 0      | 0   |
| c             | a          | d   | 0      | 0   |
| d             | e          | f   | 0      | 1   |
| e             | a          | f   | 0      | 1   |
| f             | g          | f   | 0      | 1   |
| g             | a          | f   | 0      | 1   |

Solution:

(81)

| Present state | Next state |       | Output |       |
|---------------|------------|-------|--------|-------|
|               | $x=0$      | $x=1$ | $x=0$  | $x=1$ |
| a             | a          | b     | 0      | 0     |
| b             | c          | d     | 0      | 0     |
| c             | a          | d     | 0      | 0     |
| d             | e          | f     | 0      | 1     |
| e             | a          | f     | 0      | 1     |
| f             | g          | f     | 0      | 1     |
| g             | a          | f     | 0      | 1     |

~~b~~ / ~~a~~  
~~c~~  
~~d~~  
~~e~~  
~~f~~  
~~g~~

Step 1:- draw the implication table

Step 2:- Create one-one correspondence between the states.

Step 3:- Strike off the states whose outputs are not equal.

Two states can only equal if and only if, their outputs are equal w.r.t. input.

We have removed all the b-f & b-d f-d correspondences.

Hence the remaining states, which are equal,

$$a = c = g = e$$

$$\& b = d$$

|   |                |                |                |     |       |
|---|----------------|----------------|----------------|-----|-------|
| b | anc            |                |                |     |       |
|   | bnd            |                |                |     |       |
| c | bnd            | anc            |                |     |       |
|   | anc            | cne            | ane            |     |       |
| d | <del>bnd</del> | <del>fnd</del> | <del>fnd</del> |     |       |
|   | <del>bnd</del> | anc            | dof            | ane |       |
| e | <del>bnd</del> | <del>fnd</del> | <del>dof</del> |     |       |
|   | ang            | cng            | ang            | eng | ang   |
| f | <del>bnd</del> | <del>dnd</del> | <del>dof</del> |     |       |
| g | <del>bnd</del> | anc            | dof            | ane | X ang |
|   | <del>fnd</del> |                |                |     |       |
| a | b              | c              | d              | e   | f     |

12. Reduce the number of states in the state table. Use implication table.

| Present State | Next State |     | Output |     |
|---------------|------------|-----|--------|-----|
|               | X=0        | X=1 | X=0    | X=1 |
| a             | e          | a   | 0      | 0   |
| b             | c          | d   | 0      | 0   |
| c             | e          | f   | 0      | 0   |
| d             | h          | b   | 1      | 0   |
| e             | c          | d   | 0      | 0   |
| f             | e          | a   | 1      | 1   |
| g             | h          | g   | 0      | 1   |
| h             | h          | b   | 1      | 0   |

**Solution:**

(Q2)

| Present state | Next state |       | Output |       |
|---------------|------------|-------|--------|-------|
|               | $x=0$      | $x=1$ | $x=0$  | $x=1$ |
| a             | e          | a     | 0      | 0     |
| b             | c          | d     | 0      | 0     |
| c             | e          | f     | 0      | 0     |
| d             | h          | b     | 1      | 0     |
| e             | c          | d     | 0      | 0     |
| f             | e          | a     | 1      | 1     |
| g             | h          | g     | 0      | 1     |
| h             | h          | b     | 1      | 0     |

from the table

$b = e$   
 $d = h$  as both output & next states are equal.

|   |                                  |                                  |                                  |                                  |                                   |                                  |
|---|----------------------------------|----------------------------------|----------------------------------|----------------------------------|-----------------------------------|----------------------------------|
| b | <del>cne</del><br><del>and</del> |                                  |                                  |                                  |                                   |                                  |
| c | <del>anf</del>                   | <del>cne</del><br><del>dnf</del> |                                  |                                  |                                   |                                  |
| d | <del>ent</del><br><del>anb</del> | <del>ent</del><br><del>dnb</del> | <del>ent</del><br><del>bnt</del> |                                  |                                   |                                  |
| e | <del>cne</del><br><del>and</del> | <del>cne</del><br><del>dnf</del> | <del>cne</del><br><del>dnf</del> | <del>ent</del><br><del>bnt</del> |                                   |                                  |
| f | <del>enf</del><br><del>ana</del> | <del>cne</del><br><del>fna</del> | <del>anf</del>                   | <del>ent</del><br><del>bna</del> | <del>cne</del><br><del>dnna</del> |                                  |
| g | <del>ent</del><br><del>gag</del> | <del>ent</del><br><del>gat</del> | <del>ent</del><br><del>fgg</del> | <del>ent</del><br><del>dog</del> | <del>ent</del><br><del>ang</del>  |                                  |
| h | <del>ent</del><br><del>anb</del> | <del>ent</del><br><del>bnd</del> | <del>ent</del><br><del>bnt</del> | <del>ent</del><br><del>bnd</del> | <del>ent</del><br><del>anb</del>  | <del>ent</del><br><del>205</del> |
|   | a                                | b                                | c                                | d                                | e                                 | f                                |

13. Merge each of the primitive flow tables shown below. Proceed as follows:

|   | 00  | 01  | 11  | 10  |
|---|-----|-----|-----|-----|
| a | 0,0 | b,- | -,- | e,- |
| b | a,- | 0,0 | c,- | -,- |
| c | -,- | d,- | 0,0 | h,- |
| d | a,- | 0,1 | -,- | -,- |
| e | a,- | -,- | f,- | 0,0 |
| f | -,- | g,- | 0,0 | h,- |
| g | a,- | 0,0 | -,- | -,- |
| h | a,- | -,- | -,- | 0,0 |

(I)

|   | 00  | 01  | 11  | 10  |
|---|-----|-----|-----|-----|
| a | -,- | d,- | b,- | 0,0 |
| b | -,- | d,- | 0,1 | c,- |
| c | f,- | -,- | b,- | 0,1 |
| d | f,- | 0,0 | e,- | -,- |
| e | -,- | d,- | 0,0 | c,- |
| f | 0,0 | d,- | -,- | a,- |

(II)

- Find all compatible pairs by means of an implication table.
- Find the maximal compatibles by means of a merger diagram.
- Find a minimal set of compatibles that covers all the states and is closed

### Solution:


① Implication table

|   | a         | b     | c         | d     | e  | f | g |
|---|-----------|-------|-----------|-------|----|---|---|
| b | ✓         |       |           |       |    |   |   |
| c | bd, eh, X | bd, X |           |       |    |   |   |
| d | X         | X     | ✓         |       |    |   |   |
| e | ✓         | cf, X | ef, X     | he, X | ✓  |   |   |
| f | bg, eh, X | bg, X | dg, cf, X | dg, X | eh |   |   |
| g | bg        | bg    | dg, X     | X     | ✓  | ✓ |   |
| h | eh        | ✓     | ✓         | ✓     | eh | ✓ | ✓ |

→ Hence, compatible pairs are:

ab, ac, ad, ae, af, ag, ah, bg, bh, cd, ch, ef, eg, eh, fg, fh, gh

• Merger diagram:

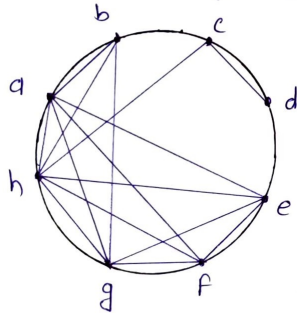

→ Maximal compatibles are: ab, cd, ch, efgh

• closure table:

|                |    |    |    |      |
|----------------|----|----|----|------|
| Compatibles    | ab | cd | ch | efgh |
| Implied states | -  | -  | -  | eh   |

→ implied state 'eh' already included in maximal compatible  
Hence, minimal set of compatibles are:  
ab, cd, ch, efgh


② Implication table:-

|   |                 |     |     |   |     |
|---|-----------------|-----|-----|---|-----|
| b | ae              |     |     |   |     |
|   | x               |     |     |   |     |
| c | acx             | ✓   |     |   |     |
|   |                 |     |     |   |     |
| d | bex             | bex | bex |   |     |
|   |                 |     |     |   |     |
| e | be <sub>x</sub> | X   | bex | ✓ |     |
|   | ac              |     |     |   |     |
| f | ✓               | acx | acx | ✓ | acx |
|   |                 |     |     |   |     |
|   | a               | b   | c   | d | e   |

→ Thus the all compatible pairs are: df, af, de, cb

→ Hence the minimal collection of compatibles is also the maximal compatible set.

Merger diagram

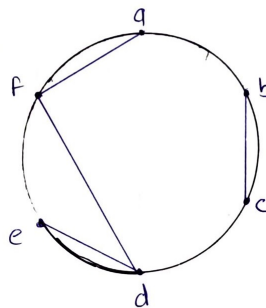


→ Maximum compatibles are: bc, de, af

14. Find a critical race-free state assignment for the reduced flow table shown below:

|   | 00 | 01 | 11 | 10 |
|---|----|----|----|----|
| a | a  | d  | a  | c  |
| b | a  | b  | b  | d  |
| c | d  | c  | b  | c  |
| d | d  | d  | e  | d  |
| e | f  | c  | e  | c  |
| f | f  | b  | a  | f  |

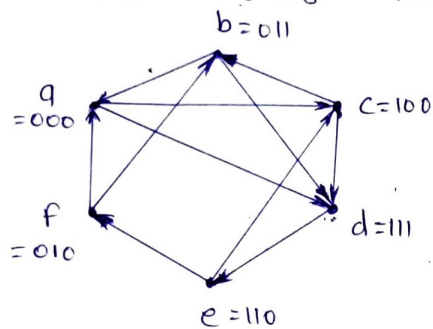**Solution:**

- Transition diagram for given flow table is :



- Transition diagram for the given flow table

→ Two extra states (g=001 & h=101) can be utilized for race free assignment  
 → Hence the binary assignment table is given

|   | 00 | 01 | 11 | 10 |
|---|----|----|----|----|
| 0 | a  | g  | b  | f  |
| 1 | c  | h  | d  | e  |

15. Consider the reduced flow table shown in below Fig.




|          | 00       | 01       | 11       | 10       |
|----------|----------|----------|----------|----------|
| <i>a</i> | <i>a</i> | <i>c</i> | <i>a</i> | <i>d</i> |
| <i>b</i> | <i>a</i> | <i>b</i> | <i>c</i> | <i>b</i> |
| <i>c</i> | <i>c</i> | <i>c</i> | <i>c</i> | <i>d</i> |
| <i>d</i> | <i>d</i> | <i>b</i> | <i>a</i> | <i>d</i> |

- Obtain the transition diagram, and show that three state variables are needed for a race-free binary state assignment.
- Obtain the expanded flow table using the multiple-row method of assignment.
- Obtain the expanded flow table using the four-row method of assignment.
- Compare the number of states required in (b) and (c)

**Solution:**

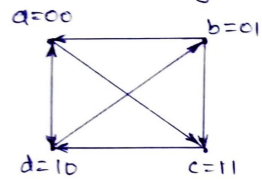- (a) • Transition diagram for given flow table is



→ The transitions from state a to c & d to b requires two bits change, which can arise race condition

→ To avoid it, extra states need to be added

→ Thus three-state variables are needed for the race-free binary state assignment.

- (b) • Multiple-row method:-

Let,  $a_1 = 000$   $b_1 = 001$   $c_1 = 011$   $d_1 = 010$   
 $a_2 = 111$   $b_2 = 110$   $c_2 = 100$   $d_2 = 101$

→ Binary state assignment table is given as,

| $a_1$ | $b_1$ | $c_1$ | $d_1$ |
|-------|-------|-------|-------|
| $a_2$ | $b_2$ | $c_2$ | $d_2$ |

→ This expanded flow table is given as

|       | 00    | 01    | 11    | 10    |
|-------|-------|-------|-------|-------|
| $a_1$ | $a_1$ | $c_2$ | $a_1$ | $d_1$ |
| $a_2$ | $a_2$ | $c_1$ | $a_2$ | $d_2$ |
| $b_1$ | $a_1$ | $b_1$ | $c_1$ | $b_1$ |
| $b_2$ | $a_2$ | $b_2$ | $c_2$ | $b_2$ |
| $c_1$ | $c_1$ | $c_1$ | $c_1$ | $d_1$ |
| $c_2$ | $c_2$ | $c_2$ | $c_2$ | $d_2$ |
| $d_1$ | $d_1$ | $b_2$ | $a_1$ | $d_1$ |
| $d_2$ | $d_2$ | $b_1$ | $a_2$ | $d_2$ |

→ Total 8-states are required

(C) Four-row method:


let  $a=000$   $b=001$   $c=011$  &  $d=101$

Three extra states  $e=100$ ,  $f=010$  &  $g=111$

→ Thus the binary state assignment table is given as,

|   |       |       |    |    |    |    |
|---|-------|-------|----|----|----|----|
|   | $q_3$ | $q_2$ | 00 | 01 | 11 | 10 |
| 0 |       |       | a  | b  | c  | f  |
| 1 |       |       | e  | d  | g  |    |

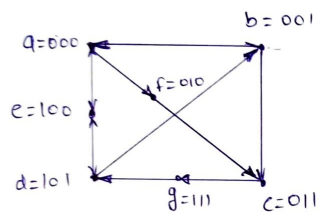→ The modified transition diagram can be given as



→ Thus the expanded flow table is given as

|   |     |     |     |     |    |
|---|-----|-----|-----|-----|----|
|   |     | 00  | 01  | 11  | 10 |
| a | (a) | f   | (a) | e   |    |
| b | a   | (b) | c   | (b) |    |
| c | (c) | (c) | (c) | g   |    |
| d | (d) | b   | e   | (d) |    |
| e | -   | -   | a   | d   |    |
| f | -   | c   | -   | -   |    |
| g | -   | -   | -   | d   |    |

→ Total 7-states are required

(d) 7-states are required in Four-row method compared to 8-states in multiple row method.

16. Design an asynchronous sequential circuit using SR latch with two inputs ( $X_1$  and  $X_2$ ) and one output ( $Z$ ), satisfying the following conditions:

(a) The inputs  $X_1$  and  $X_2$  never change simultaneously.

(b) The output  $z$  is 1 if  $X_1 = 1$  and the  $X_2$  changes from 0 to 1. Otherwise, the output  $z$  remains unchanged under any other input condition.

**Solution:**

Given,  $x_1, x_2 \rightarrow \text{inputs}$   $z \rightarrow \text{output}$

$$x_1 = 1 \text{ \& } x_2 = 0 \rightarrow 1 \Rightarrow z = 1$$

• Specification of total states:


| States | Input |       | Output | Comments             |
|--------|-------|-------|--------|----------------------|
|        | $x_1$ | $x_2$ | $z$    |                      |
| a      | 1     | 0     | 0      | Initial output $z=0$ |
| b      | 1     | 1     | 1      | After state a        |
| c      | 0     | 0     | 0      | After state a        |
| d      | 0     | 1     | 1      | After state b        |
| e      | 1     | 0     | 1      | After state b        |
| f      | 0     | 1     | 0      | After state c        |
| g      | 0     | 0     | 1      | After state d        |
| h      | 1     | 1     | 0      | After state f        |

→ The primitive flow table obtained as:

|   | $x_1, x_2$ |        |        |        |
|---|------------|--------|--------|--------|
|   | 00         | 01     | 11     | 10     |
| a | c, -       | -1-    | b, -   | (a), 0 |
| b | -1-        | d, -   | (b), 1 | e, -   |
| c | (c), 0     | f, -   | -1-    | a, -   |
| d | g, -       | (d), 1 | b, -   | -1-    |
| e | g, -       | -1-    | b, -   | (e), 1 |
| f | c, -       | (f), 0 | h, -   | -1-    |
| g | (g), 1     | d, -   | -1-    | e, -   |
| h | -1-        | f, -   | (h), 0 | a, -   |

→ Implication table:-

|   |    |    |    |    |    |    |   |
|---|----|----|----|----|----|----|---|
| b | ae |    |    |    |    |    |   |
| c | ✓  | df |    |    |    |    |   |
| d | cg | ✓  | df |    |    |    |   |
| e | ✓  | cg | df | ✓  |    |    |   |
| f | bh | df | ✓  | cg | ✓  |    |   |
| g | cg | ✓  | df | ✓  | bh | ✓  |   |
| h | bh | ✓  | df | ✓  | cg | df | ✓ |
| a | b  | c  | d  | e  | f  | g  |   |

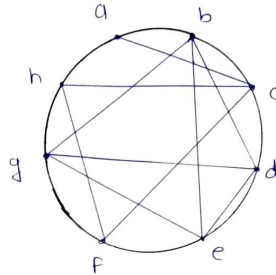


→ Compatible pairs are:  
ac, db, be, bg, cf, ch, de, dg,  
eg, fh

→ maximal compatibles  
are: ac, cfh, bdeg

→ The minimal set of compatibles is also the  
maximal compatible set because covering & closed  
condition are satisfied.

→ Hence the reduced flow table can be given as:

|        |      |      |      |      |
|--------|------|------|------|------|
|        | 00   | 01   | 11   | 10   |
| A=ac   | (A)0 | B,-  | C,-  | (A)0 |
| B=cfh  | (B)0 | (B)0 | (B)0 | A,-  |
| C=bdeg | (C)1 | (C)1 | (C)1 | (C)1 |

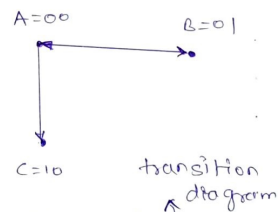

• State Assignment:-

→ Transition diagram can be given as,

• transition table :- let  $y_1, y_2 \rightarrow$  internal state

| $y_1 y_2 \backslash x_1 x_2$ | 00 | 01 | 11 | 10 |
|------------------------------|----|----|----|----|
| 00                           | 00 | 01 | 10 | 00 |
| 01                           | 01 | 01 | 01 | 00 |
| 11                           | xx | xx | xx | xx |
| 10                           | 10 | 10 | 10 | 10 |

Transition table

| $y_1 y_2 \backslash x_1 x_2$ | 00 | 01 | 11 | 10 |
|------------------------------|----|----|----|----|
| 00                           | 0  | 0  | 1  | 0  |
| 01                           | 0  | 0  | 0  | 0  |
| 11                           | x  | x  | x  | x  |
| 10                           | 1  | 1  | 1  | 1  |

$y_1$  map

| $y_1 y_2 \backslash x_1 x_2$ | 00 | 01 | 11 | 10 |
|------------------------------|----|----|----|----|
| 00                           | 0  | 1  | 0  | 0  |
| 01                           | 1  | 1  | 1  | 0  |
| 11                           | x  | x  | x  | x  |
| 10                           | 0  | 0  | 0  | 0  |

$y_2$  map

| $y_1 y_2 \backslash x_1 x_2$ | 00 | 01 | 10 | 11 |
|------------------------------|----|----|----|----|
| 00                           | 0  | x  | x  | 0  |
| 01                           | 0  | 0  | 0  | x  |
| 11                           | x  | x  | x  | x  |
| 10                           | 1  | 1  | 1  | 1  |

output z map

$$y_1 = y_1 + \overline{y_2} x_1 x_2$$

$$\Rightarrow y_2 = \overline{y_1} \overline{x_1} x_2 + y_2 \overline{x_1} + y_2 x_2$$

$$z = y_1$$

| $Q_n$ | $Q_n^+$ | S | R |
|-------|---------|---|---|
| 0     | 0       | 0 | x |
| 0     | 1       | 1 | 0 |
| 1     | 0       | 0 | 1 |
| 1     | 1       | x | 0 |

→ Implementation using SR latch:

| $y_1 y_2 \backslash x_1 x_2$ | 00 | 01 | 11 | 10 |
|------------------------------|----|----|----|----|
| 00                           | 0  | 0  | 1  | 0  |
| 01                           | 0  | 0  | 0  | 0  |
| 11                           | x  | x  | x  | x  |
| 10                           | x  | x  | x  | x  |

$S_1$

| $y_1 y_2 \backslash x_1 x_2$ | 00 | 01 | 11 | 10 |
|------------------------------|----|----|----|----|
| 00                           | x  | x  | 0  | x  |
| 01                           | x  | x  | x  | x  |
| 11                           | x  | x  | x  | x  |
| 10                           | 0  | 0  | 0  | 0  |

$R_1$

$$S_1 = \overline{y_2} x_1 x_2$$

$$\Rightarrow R_1 = 0$$

| $y_1 y_2 \backslash x_1 x_2$ | 00 | 01 | 11 | 10 |
|------------------------------|----|----|----|----|
| 00                           | 0  | 1  | 0  | 0  |
| 01                           | x  | x  | x  | 0  |
| 11                           | x  | x  | x  | x  |
| 10                           | 0  | 0  | 0  | 0  |

$S_2$


| $y_1 y_2 \backslash x_1 x_2$ | 00 | 01 | 11 | 10 |
|------------------------------|----|----|----|----|
| 00                           | x  | 0  | x  | x  |
| 01                           | 0  | 0  | 0  | 1  |
| 11                           | x  | x  | x  | x  |
| 10                           | x  | x  | x  | x  |

$R_2$

$$S_2 = \overline{y_1} \overline{x_1} x_2$$

$$R_2 = x_1 \overline{x_2}$$

$$z = y_1$$

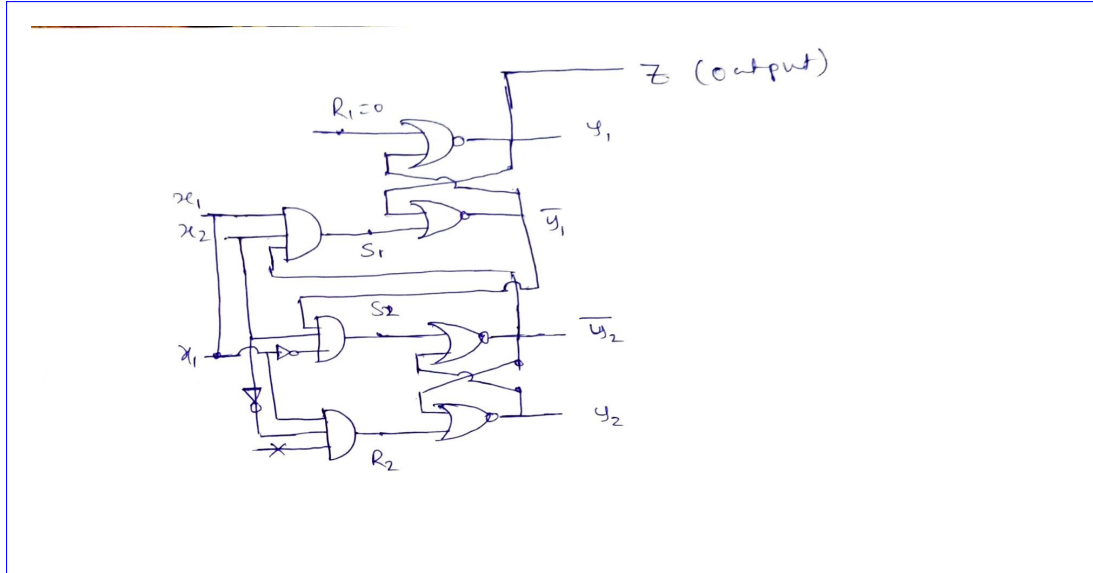


17. A traffic light is installed at the junction of a railroad and a road. The light is controlled by two switches in the rails placed 1 mile apart on either side of the junction. A switch is turned on when the train is over it and is turned off otherwise. The traffic light changes from green (logic 0) to red (logic 1) when the beginning of the train is 1 mile from the junction. The light changes back to green when the end of the train is 1 mile away from the junction. Assume that the length of the train is less than 2 miles. Consider the fundamental mode of operation.
- Obtain a primitive flow table for the circuit.
  - Show that the flow table can be reduced to four rows.
  - Complete the design of the circuit using D latch

**Solution:**

Q1

Soln:-

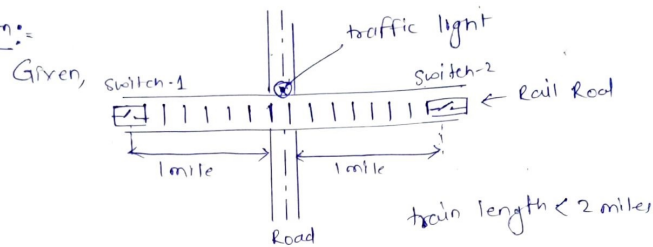

let  $x_1 \rightarrow$  Switch-1 } Inputs  $z \rightarrow$  light } output  
 $x_2 \rightarrow$  Switch-2

① before & end of passing of train  $\Rightarrow x_1, x_2 = 00 \Rightarrow z = 0$

② train over the switches  $\Rightarrow x_1, x_2 = 10$  or  $\Rightarrow z = 1$   
 or  $= 01$

③ train between the switches  $\Rightarrow x_1, x_2 = 00 \Rightarrow z = 1$

④ train may come from right or left side:

⑤  $x_1, x_2 = 11$  Not Possible  $\Leftarrow$  train length < 2 miles

$\rightarrow$  • Specifications of the states:

| States | Input |       | Output | Comments                               |
|--------|-------|-------|--------|----------------------------------------|
|        | $x_1$ | $x_2$ | $z$    |                                        |
| a      | 0     | 0     | 0      | No train, End of train                 |
| b      | 1     | 0     | 1      | train over sw-1, After a               |
| c      | 0     | 1     | 1      | train over sw-2, After a               |
| d      | 0     | 0     | 1      | train bet <sup>n</sup> sws, After b, c |
| e      | 0     | 1     | 1      | train over sw-2, After d               |
| f      | 1     | 0     | 1      | train over sw-1, After d               |




→ Primitive flow table:

|   | $x_1x_2$ |        |     |        |
|---|----------|--------|-----|--------|
|   | 00       | 01     | 11  | 10     |
| a | (A, 0)   | c, -   | -/- | b, -   |
| b | d, -     | -/-    | -/- | (B, 1) |
| c | d, -     | (C, 1) | -/- | -/-    |
| d | (D, 1)   | e, -   | -/- | f, -   |
| e | a, -     | (E, 1) | -/- | -/-    |
| f | a, -     | -/-    | -/- | (F, 1) |

→ This flow table can be reduced further:

|   |    |    |    |    |   |
|---|----|----|----|----|---|
| b | ad |    |    |    |   |
| c | ad | ✓  |    |    |   |
| d | X  | bf | ce |    |   |
| e | ce | ad | ad | ad |   |
| f | bf | ad | ad | ad | ✓ |
|   | a  | b  | c  | d  | e |

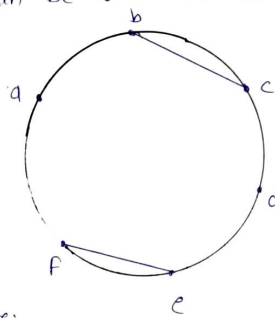

→ compatible pairs are:

a, bc, d, ef

→ maximal compatibles are: a, bc, d, ef


→ minimal set of compatibles = maximal compatibles

← both covering & closed cond's satisfied

→ The reduced flow table is:-

|        | $x_1x_2$ |        |     |        |
|--------|----------|--------|-----|--------|
|        | 00       | 01     | 11  | 10     |
| A = a  | (A, 0)   | B, -   | -/- | B, -   |
| B = bc | C, -     | (C, 1) | -/- | (D, 1) |
| C = d  | (C, 1)   | D, -   | -/- | D, -   |
| D = ef | A, -     | (D, 1) | -/- | (D, 1) |

⇒ transition diagram ⇒

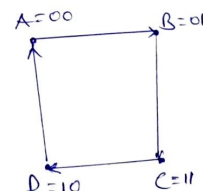

→ Transition table:-

| $y_1 y_2 \backslash x_1 x_2$ | 00 | 01 | 11 | 10 |
|------------------------------|----|----|----|----|
| 00                           | 00 | 01 | xx | 01 |
| 01                           | 11 | 01 | xx | 01 |
| 11                           | 11 | 10 | xx | 10 |
| 10                           | 00 | 10 | xx | 10 |

transition table

| $y_1 y_2 \backslash x_1 x_2$ | 00 | 01 | 11 | 10 |
|------------------------------|----|----|----|----|
| 00                           | 0  | 0  | x  | 0  |
| 01                           | 1  | 0  | x  | 0  |
| 11                           | 1  | 1  | x  | 1  |
| 10                           | 0  | 1  | x  | 1  |

$y_1$  map

| $y_1 y_2 \backslash x_1 x_2$ | 00 | 01 | 11 | 10 |
|------------------------------|----|----|----|----|
| 00                           | 0  | 1  | x  | 1  |
| 01                           | 1  | 1  | x  | 1  |
| 11                           | 1  | 0  | x  | 0  |
| 10                           | 0  | 0  | x  | 0  |

$y_2$  map

| $y_1 y_2 \backslash x_1 x_2$ | 00 | 01 | 11 | 10 |
|------------------------------|----|----|----|----|
| 00                           | 0  | x  | x  | x  |
| 01                           | x  | 1  | x  | 1  |
| 11                           | 1  | x  | x  | x  |
| 10                           | x  | 1  | x  | 1  |

output map

| $y_1 y_2 \backslash x_1 x_2$ | 00 | 01 | 11 | 10 |
|------------------------------|----|----|----|----|
| 00                           | 0  | 0  | x  | 0  |
| 01                           | 1  | 0  | x  | 0  |
| 11                           | 1  | 1  | x  | 1  |
| 10                           | 0  | 1  | x  | 1  |

$D_1$  map

| $y_1 y_2 \backslash x_1 x_2$ | 00 | 01 | 11 | 10 |
|------------------------------|----|----|----|----|
| 00                           | 0  | 1  | x  | 1  |
| 01                           | 1  | 1  | x  | 1  |
| 11                           | 1  | 0  | x  | 0  |
| 10                           | 0  | 0  | x  | 0  |

$D_2$  map

→ Equations:

$$D_1 = y_2 \bar{x}_1 \bar{x}_2 + y_1 x_2 + y_1 x_1$$

$$D_2 = y_2 \bar{x}_1 \bar{x}_2 + \bar{y}_1 x_2 + \bar{y}_1 x_1$$

$$Z = y_1 + y_2$$

→ Implementation:

