
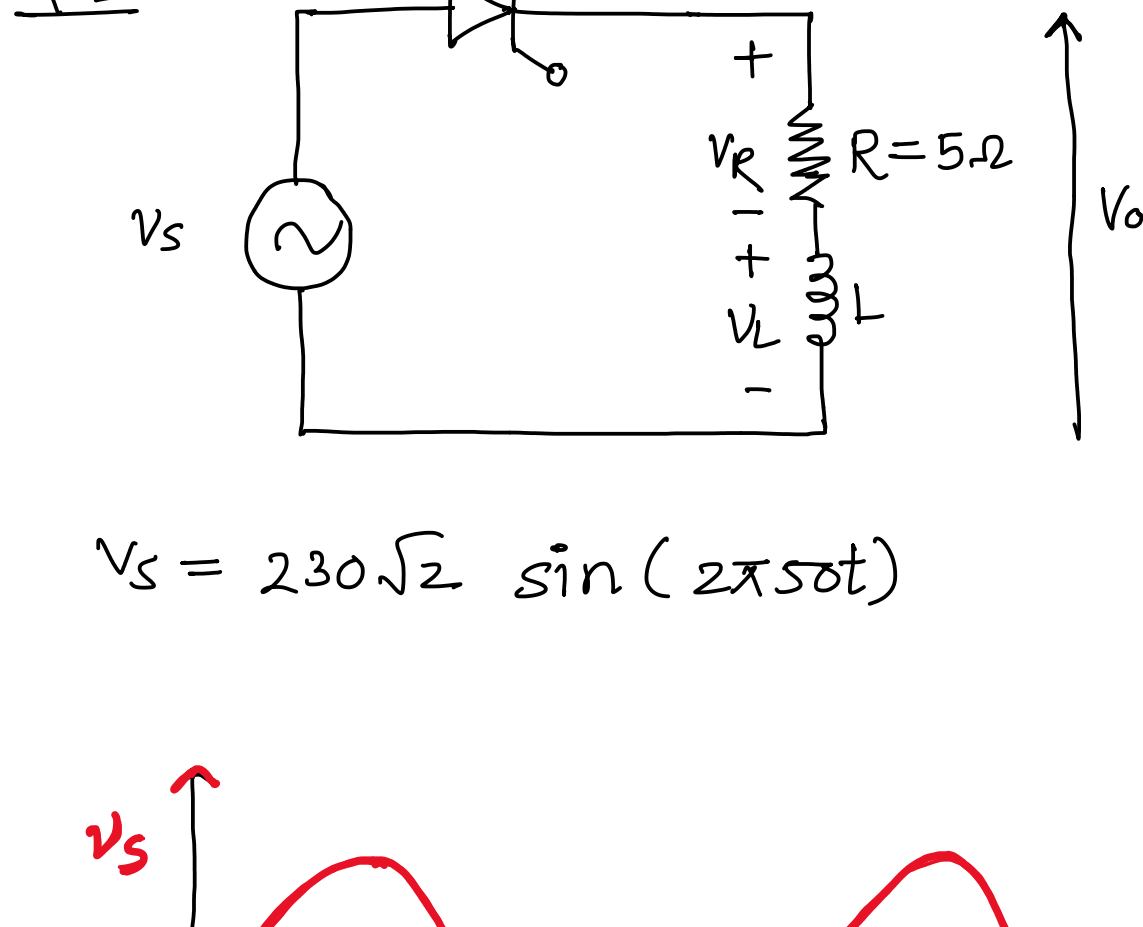


Tutorial 3 Solution Sheet

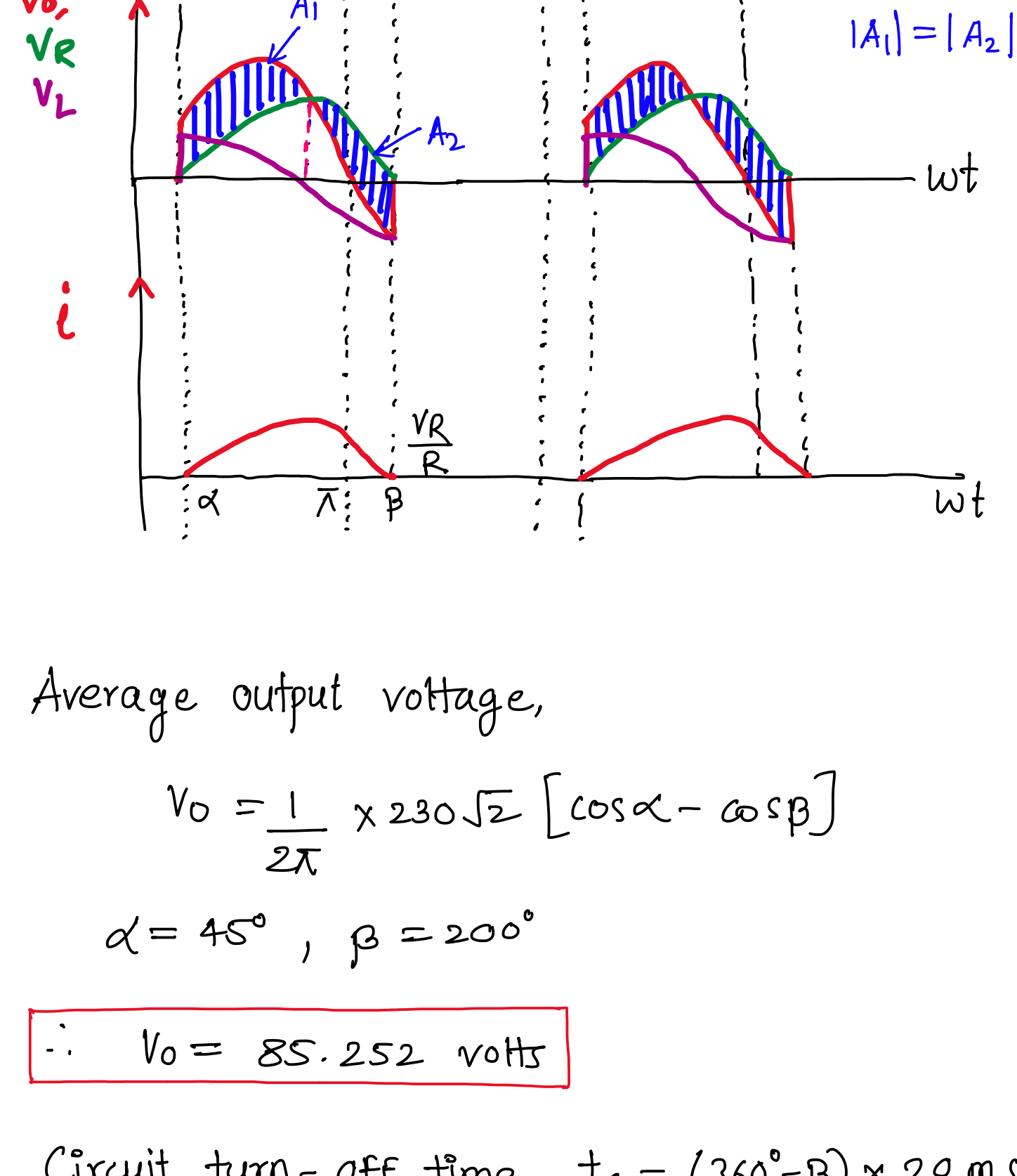

$$V_s = 230\sqrt{2} \sin(2\pi 50t)$$



Average output voltage,

$$V_o = \frac{1}{2\pi} \times 230\sqrt{2} [\cos\alpha - \cos\beta]$$

$$\alpha = 45^\circ, \beta = 200^\circ$$


$$\therefore V_o = 85.252 \text{ volts}$$

$$\text{Circuit turn-off time, } t_c = (360^\circ - \beta) \times \frac{20 \text{ ms}}{360}$$

$$\therefore t_c = 18.89 \text{ ms}$$


$$\text{Average load current, } I_o = \frac{V_o}{R} = 17.050 \text{ A}$$

Q.2

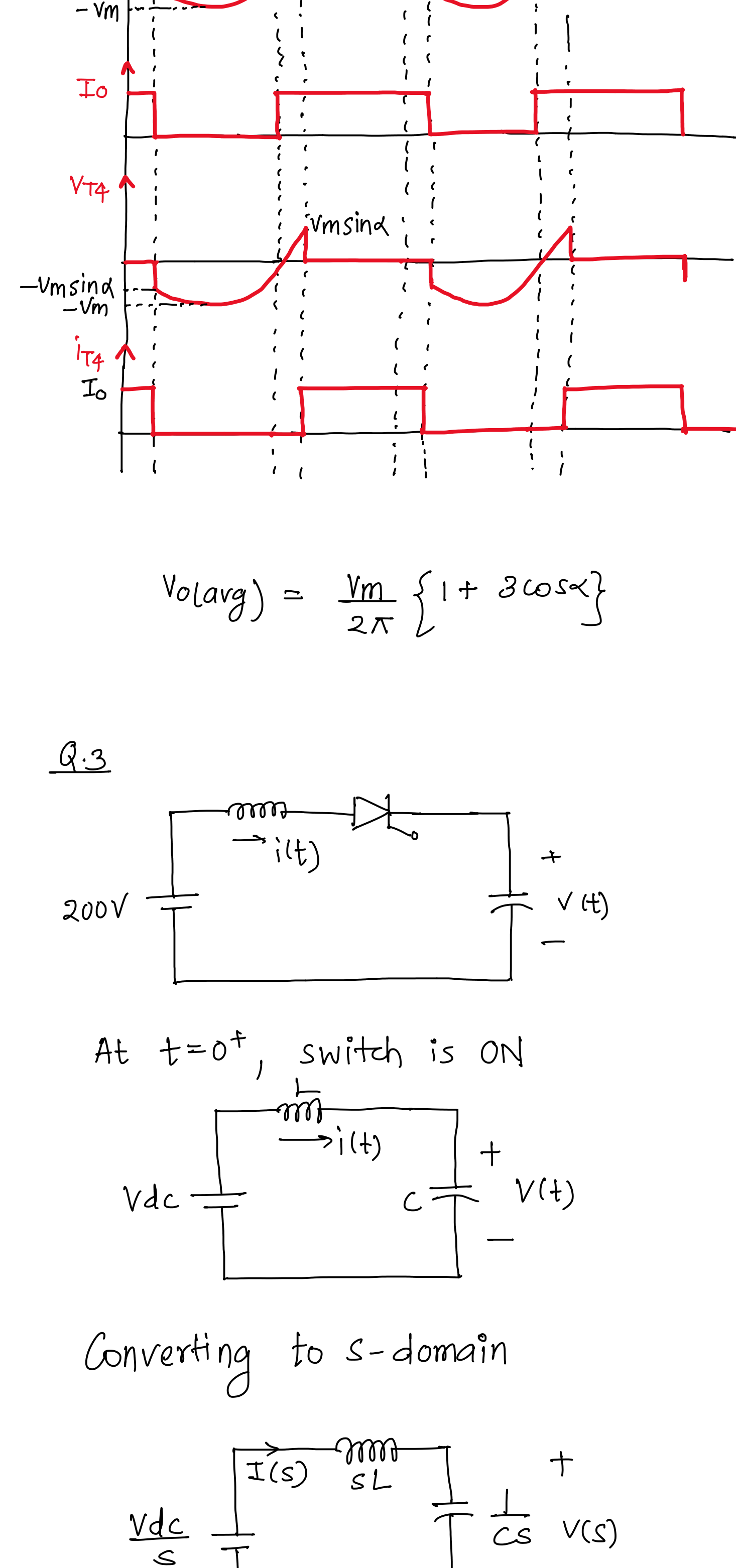


$$V_o(\text{avg}) = \frac{V_m}{2\pi} \{1 + 3\cos\alpha\}$$


Q.3

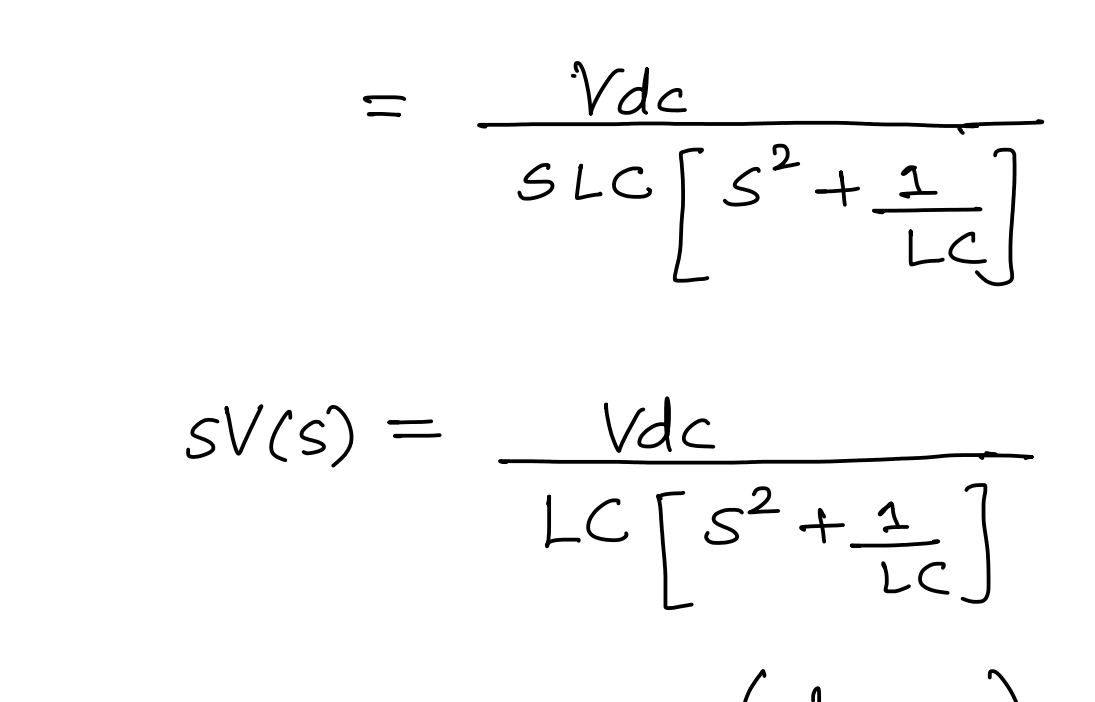

At $t=0^+$, switch is ON

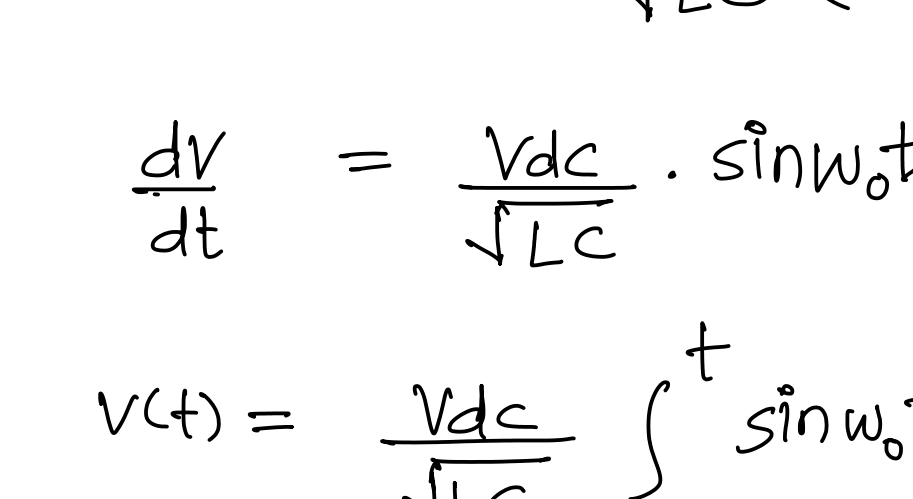

Converting to s-domain

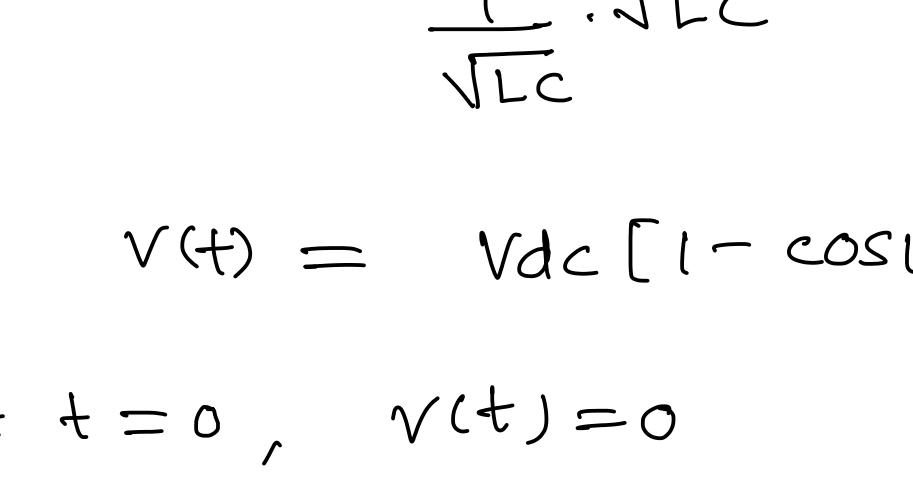

$$V(s) = \frac{V_{dc}}{s} \left[\frac{1}{cs} \right]$$

$$= \frac{V_{dc}}{s \left[s^2 LC + 1 \right]}$$

$$= \frac{V_{dc}}{s LC \left[s^2 + \frac{1}{LC} \right]}$$

$$sV(s) = \frac{V_{dc}}{LC \left[s^2 + \frac{1}{LC} \right]}$$

$$= \frac{V_{dc} \left(\frac{1}{\sqrt{LC}} \right)}{LC \cdot \frac{1}{\sqrt{LC}} \left(s^2 + \left(\frac{1}{\sqrt{LC}} \right)^2 \right)}$$

$$\frac{dV}{dt} = \frac{V_{dc}}{\sqrt{LC}} \cdot \sin \omega_0 t, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\therefore V(t) = \frac{V_{dc}}{\sqrt{LC}} \int_0^t \sin \omega_0 t \, dt$$

$$= \frac{-V_{dc}}{\frac{1}{\sqrt{LC}} \cdot \sqrt{LC}} [\cos \omega_0 t - 1] + k$$

$$V(t) = V_{dc} [1 - \cos \omega_0 t] + k$$

$$\text{At } t=0, \quad V(t)=0$$

$$\therefore k=0$$

$$\therefore V(t) = V_{dc} [1 - \cos \omega_0 t]$$



$$\therefore I(s) = \frac{V_{dc}/s}{sL + \frac{1}{Cs}} = \frac{C V_{dc}}{s^2 LC + 1}$$

$$I(s) = \frac{C V_{dc}}{s^2 LC + 1} = \frac{C}{LC} \frac{V_{dc}}{\left(s^2 + \frac{1}{LC} \right)}$$

$$\therefore I(s) = \frac{V_{dc} \times \frac{1}{\sqrt{LC}}}{\frac{1}{\sqrt{LC}} \cdot L \cdot \left(s^2 + \left(\frac{1}{\sqrt{LC}} \right)^2 \right)}$$

$$\therefore i(t) = V_{dc} \sqrt{\frac{C}{L}} \sin \omega_0 t; \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

b)

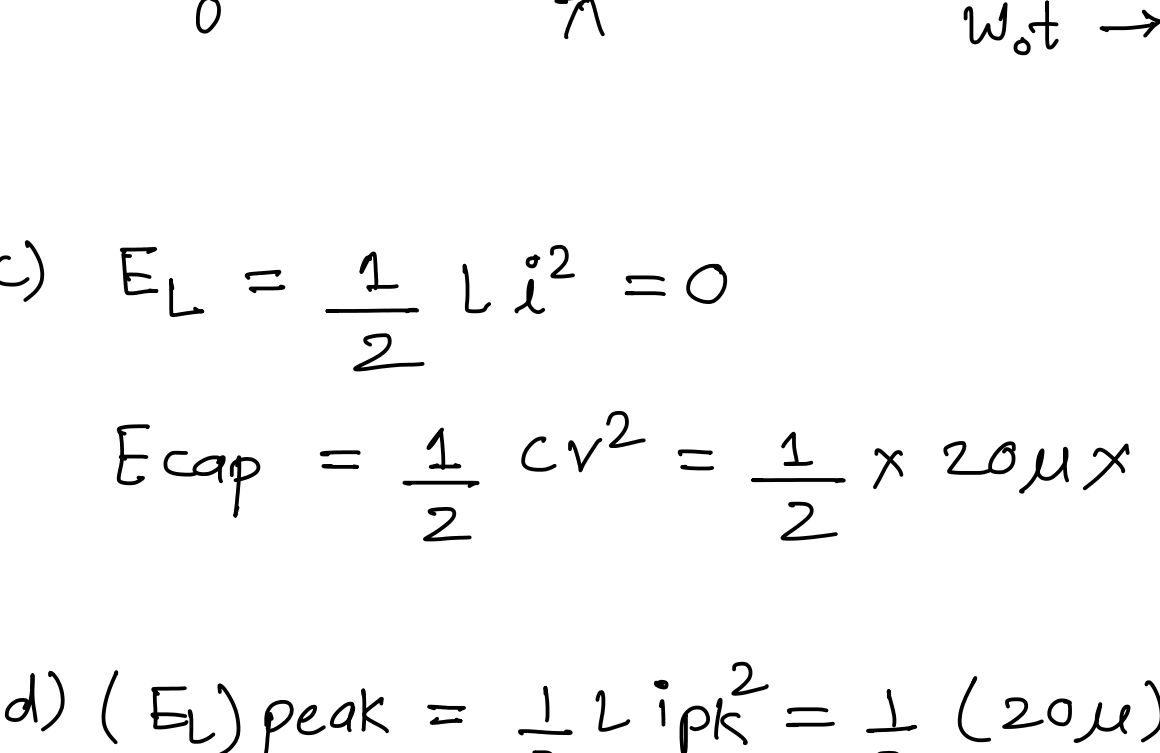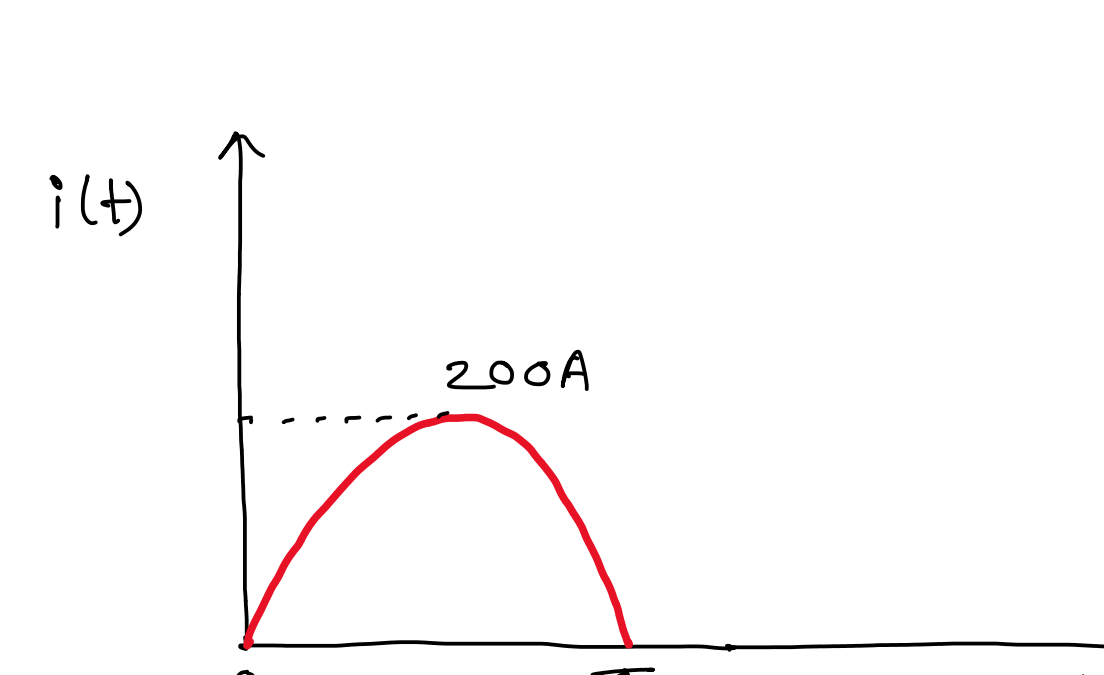

$$c) E_L = \frac{1}{2} L i^2 = 0$$

$$E_{cap} = \frac{1}{2} C v^2 = \frac{1}{2} \times 20 \mu \times 400^2 = 1.6 \text{ J}$$

$$d) (E_L)_{\text{peak}} = \frac{1}{2} L i_{pk}^2 = \frac{1}{2} (20 \mu)(200)^2 = 0.4 \text{ J}$$

$$(E_{cap})_{\text{peak}} = 1.6 \text{ J}$$

$$e) E_{\text{source}} = \left(\int V_{dc} i(t) \, dt \right)$$

$$= \left(\int_0^\pi 200 (200) \sin \omega_0 t \, d(\omega_0 t) \right) / \omega_0$$

$$= \left(200 \times 200 \times [-\cos \omega_0 t]_0^\pi \right) / \omega_0$$

$$= \frac{200 \times 200 \times 2}{\omega_0} = 200 \times 200 \times 2 \times 20 \mu$$

$$= 1.6 \text{ J}$$


$$\therefore \text{Energy balance: } E_{\text{source}} = 1.6 \text{ J}$$

$$\therefore E_L + E_C = 0 + 1.6 \text{ J} = 1.6 \text{ J}$$

$$f) \text{ Peak Conducting Current stress} = I_{pk} = 200 \text{ A}$$

$$\text{Peak blocking voltage stress} = 200 \text{ V}$$

Q.4

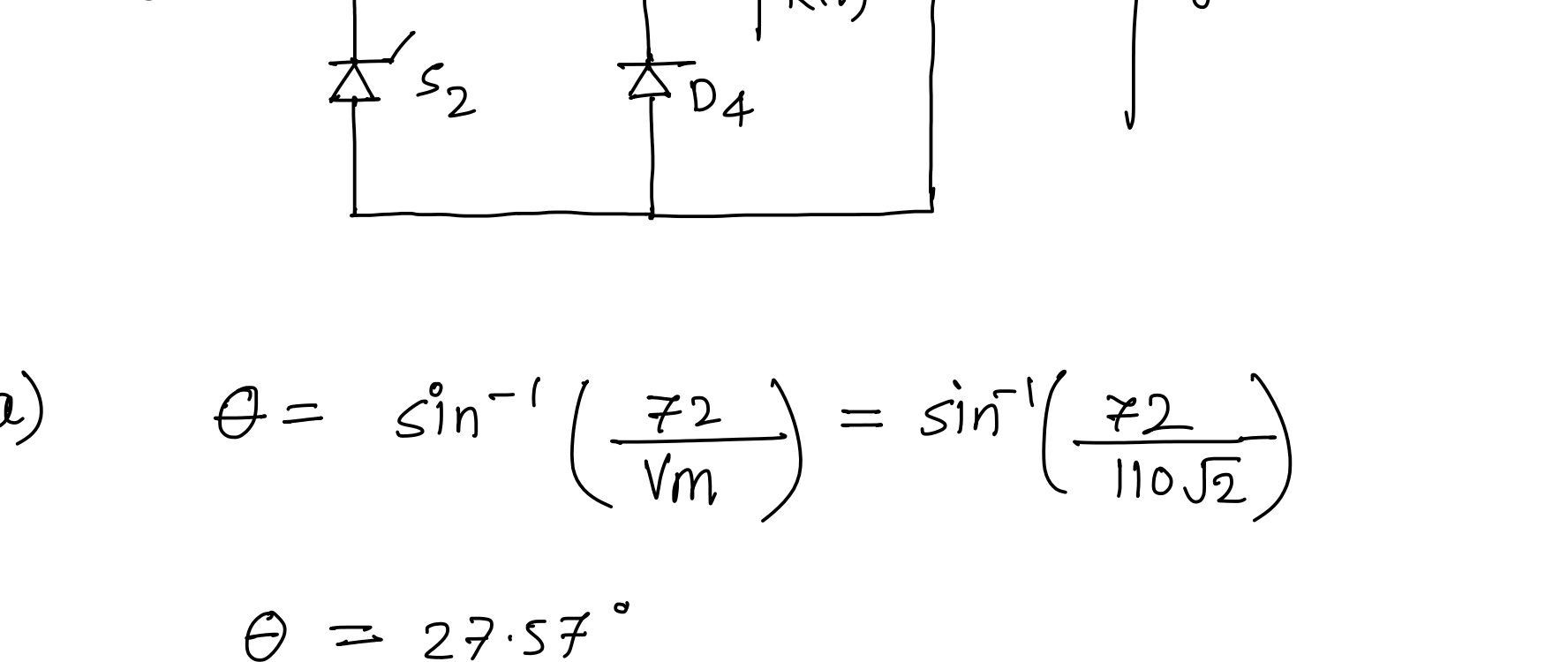

$$a) \quad \theta = \sin^{-1} \left(\frac{72}{V_m} \right) = \sin^{-1} \left(\frac{72}{110\sqrt{2}} \right)$$

$$\theta = 27.57^\circ$$


$$\therefore (V_R)_{\text{avg}} = 72 \text{ V}$$

$$\therefore 72 = \frac{V_m}{\pi} [1 + \cos\alpha]$$

$$\frac{72 \times \pi}{110\sqrt{2}} - 1 = \cos\alpha$$

$$\therefore \alpha = 63^\circ$$

b)

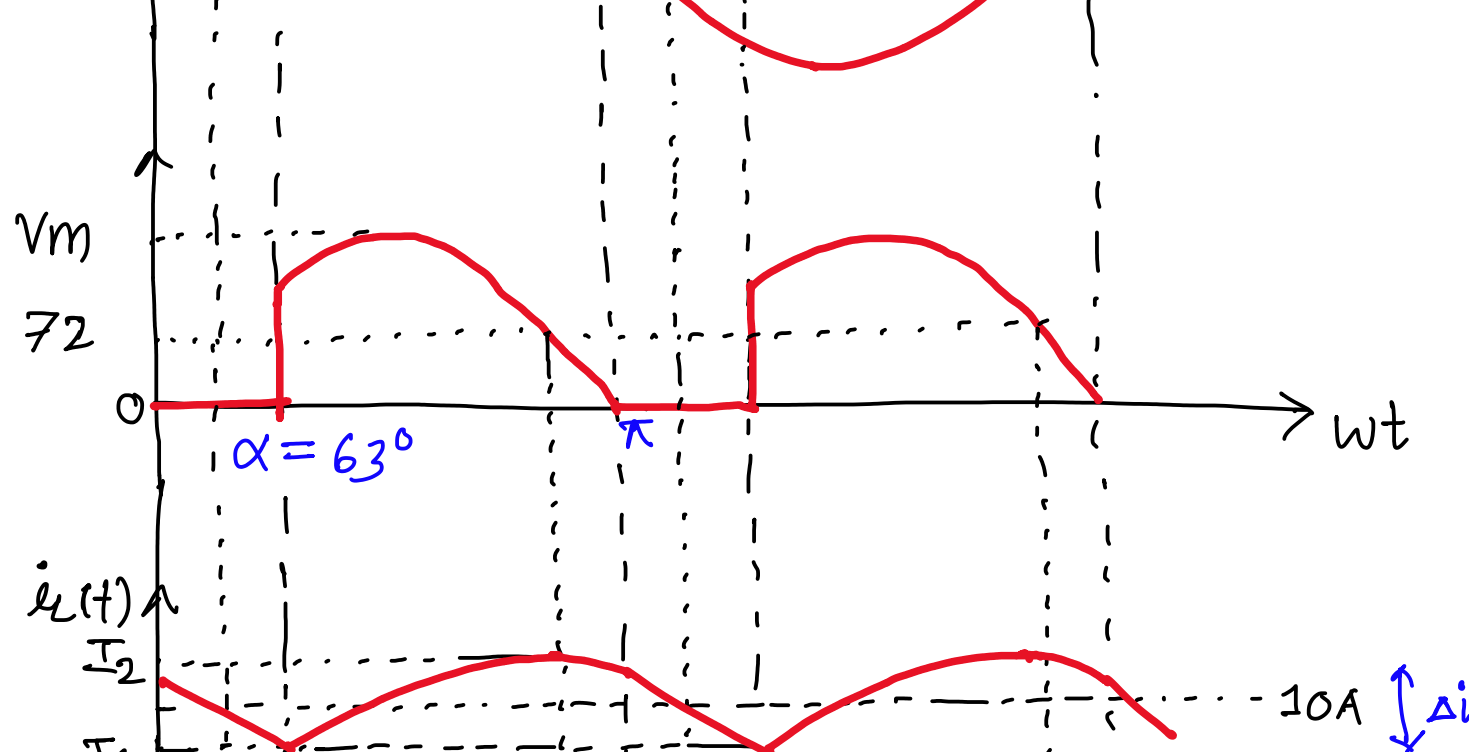

c) The current reaches maximum at ' $\pi - \theta$ ' and minimum at ' $\pi + \alpha$ '.

From $\pi - \theta$ to π , the voltage across inductor is

$$V_L = V_m \sin \omega t - E$$

From π to $\pi + \alpha$, the free-wheeling happens. & the voltage across inductor is

$$V_L = -E$$

$$V_L = L \frac{di_o}{dt}$$

$$\Rightarrow V_L dt = L di_o$$

$$\Rightarrow V_L d\omega t = \omega L di_o$$

$$\Rightarrow \int_{\pi - \theta}^{\pi + \alpha} V_L d\omega t = \int_{I_2}^{I_1} \omega L di_o$$

$$\Rightarrow \int_{\pi - \theta}^{\pi} (V_m \sin \omega t - E) d\omega t + \int_{\pi}^{\pi + \alpha} -E d\omega t = \omega L (I_1 - I_2)$$

$$\Rightarrow V_m (-\cos \omega t)_{\pi - \theta}^{\pi} - E (\omega t)_{\pi - \theta}^{\pi} - E (\omega t)_{\pi}^{\pi + \alpha} = -\omega L \Delta I_o$$

$$\Rightarrow V_m (1 - \cos \theta) - E (\alpha + \theta) = -\omega L \Delta I_o$$

$$\Rightarrow L = \frac{E (\alpha + \theta) - V_m (1 - \cos \theta)}{\omega \cdot \Delta I_o}$$

$$\Rightarrow L = \frac{72 (63^\circ + 27.57^\circ) \times \frac{\pi}{180} - 110\sqrt{2} (1 - \cos 27.57^\circ)}{2\pi \times 50 \times 1}$$

$$\therefore L = 306.05 \text{ mH}$$