
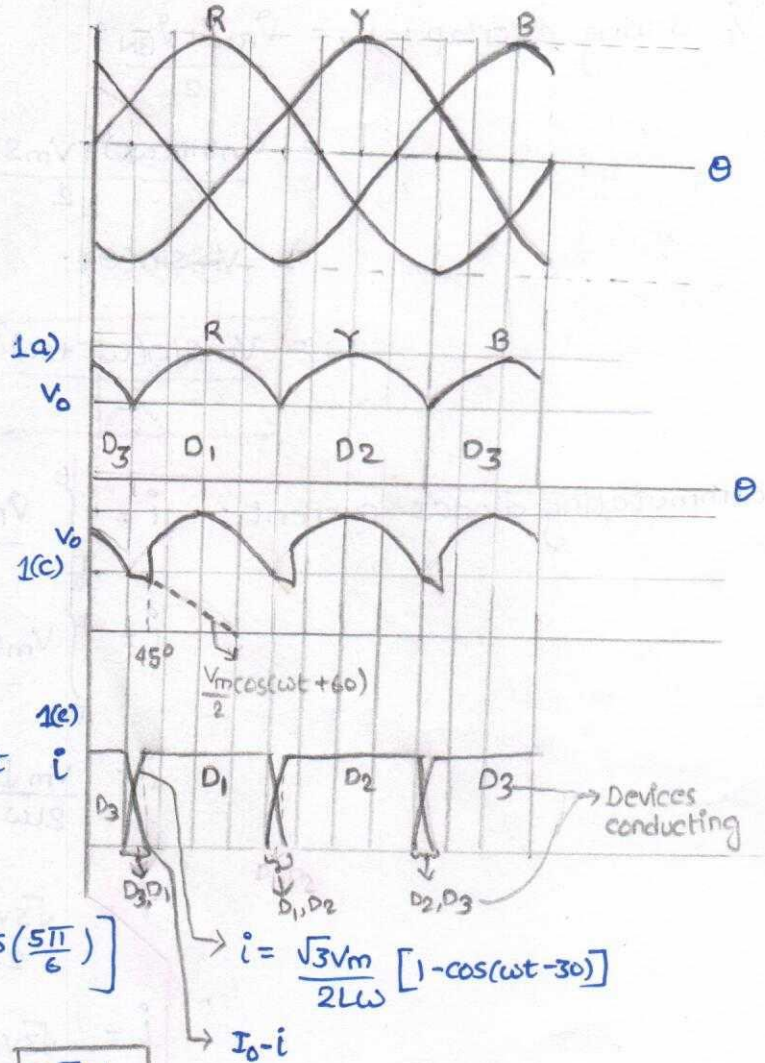



Three phase Rectifiers solutions

1

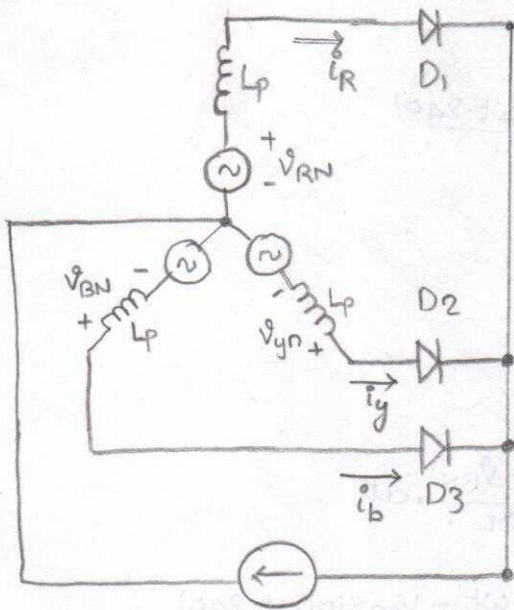

$$\begin{aligned}
 1b) \langle V_0 \rangle &= \frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} V_m \sin(\omega t) d\omega t \\
 &= \frac{3V_m}{2\pi} \left[\cos(\pi/6) - \cos(5\pi/6) \right] \\
 &= \frac{3V_m}{2\pi} \left[\frac{\sqrt{3}}{2} - \left(-\frac{\sqrt{3}}{2}\right) \right] = \boxed{\frac{3\sqrt{3}V_m}{2\pi}}
 \end{aligned}$$

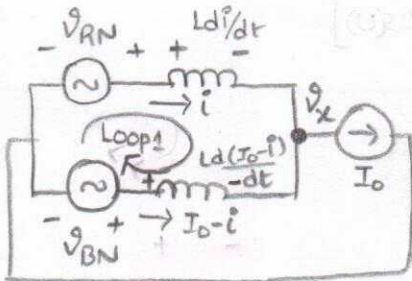1c) $L_p \neq 0$ @ $\theta = 30^\circ$ (current commutation between R & B phases)



KVL in loop 1:

$$-V_{RN} + L \frac{di}{dt} - L \frac{d(I_0 - i)}{dt} + V_{BN} = 0$$

$$\boxed{\frac{L di}{dt} = \frac{V_{RN} - V_{BN}}{2}}$$

$$V_x = V_{RN} - \frac{L di}{dt}$$

$$\boxed{V_x = \frac{V_{RN} + V_{BN}}{2}}$$

$$\begin{aligned}
 V_o \text{ during overlap: } V_x &= \frac{V_{RN} + V_{BN}}{2} \\
 &= \frac{V_m \sin(\omega t) + V_m \sin(\omega t - 240^\circ)}{2} \\
 &= V_m \sin(\theta) \\
 &= \boxed{\frac{V_m \sin(\omega t + 60^\circ)}{2}}
 \end{aligned}$$

$$\begin{aligned}
 \text{commutating diode's current: } i &= \int_{\frac{\pi}{12}}^t \frac{V_{RN} - V_{BN}}{2L} \cdot dt \\
 i &= \int_{\frac{\pi}{12}}^t \frac{V_m \sin \omega t - V_m \sin(\omega t - 240^\circ)}{2L} \cdot dt \\
 i &= \frac{V_m \sqrt{3}}{2L\omega} \int_{30^\circ}^{\omega t} \sin(\omega t - 30^\circ) \cdot d\omega t \\
 i &= \frac{\sqrt{3}V_m}{2L\omega} \left[\cos(30^\circ - 30^\circ) - \cos(\omega t - 30^\circ) \right] \\
 i &= \frac{\sqrt{3}V_m}{2L\omega} \left[1 - \underbrace{\cos(\omega t - 30^\circ)}_u \right]
 \end{aligned}$$

$$\text{Given } u = 15^\circ \Rightarrow \omega t = 15 + 30 = 45^\circ$$


$$\left. \begin{aligned} i &= 0 \text{ @ } \omega t = 30^\circ \\ i &= I_o \text{ @ } \omega t = 45^\circ \end{aligned} \right\} \Rightarrow I_o = \frac{\sqrt{3}V_m}{2L\omega} [1 - \cos(u)]$$

1d) Average output voltage:

$$\begin{aligned}
 \langle V_o \rangle &= \frac{3}{2\pi} \left[\int_{\frac{\pi}{6}}^{\frac{\pi}{6}+u} \frac{V_m}{2} \sin(\omega t + 60^\circ) \cdot d\omega t + \int_{\frac{\pi}{6}+u}^{\frac{5\pi}{6}} V_m \sin \omega t \cdot d\omega t \right] \\
 &= \frac{3V_m}{2\pi} \left[\frac{\cos(30^\circ + 60^\circ)}{2} - \frac{\cos(30^\circ + u + 60^\circ)}{2} + \cos(30^\circ + u) - \cos(150^\circ) \right]
 \end{aligned}$$


$$\begin{aligned}
 &= \frac{3V_m}{2\pi} \left[+\sin u + \cos(30^\circ + u) - \left(-\frac{\sqrt{3}}{2}\right) \right] = \boxed{\frac{3V_m}{2\pi} \left[\frac{\sqrt{3}}{2} + \cos(30^\circ - u) \right]} \\
 &u = \cos^{-1} \left[1 - \frac{2I_o L \omega}{\sqrt{3} V_m} \right]
 \end{aligned}$$

2

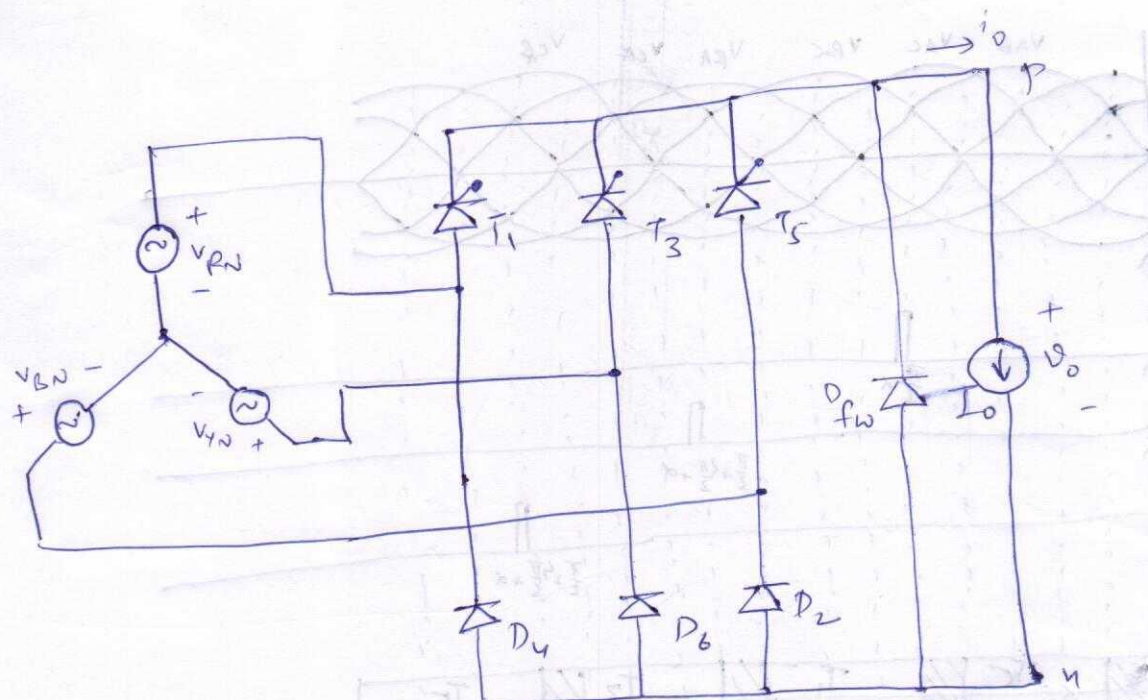


a) The range of firing angle is $0 < \alpha < 2\pi/3$.

b) for $\alpha = 30^\circ$,

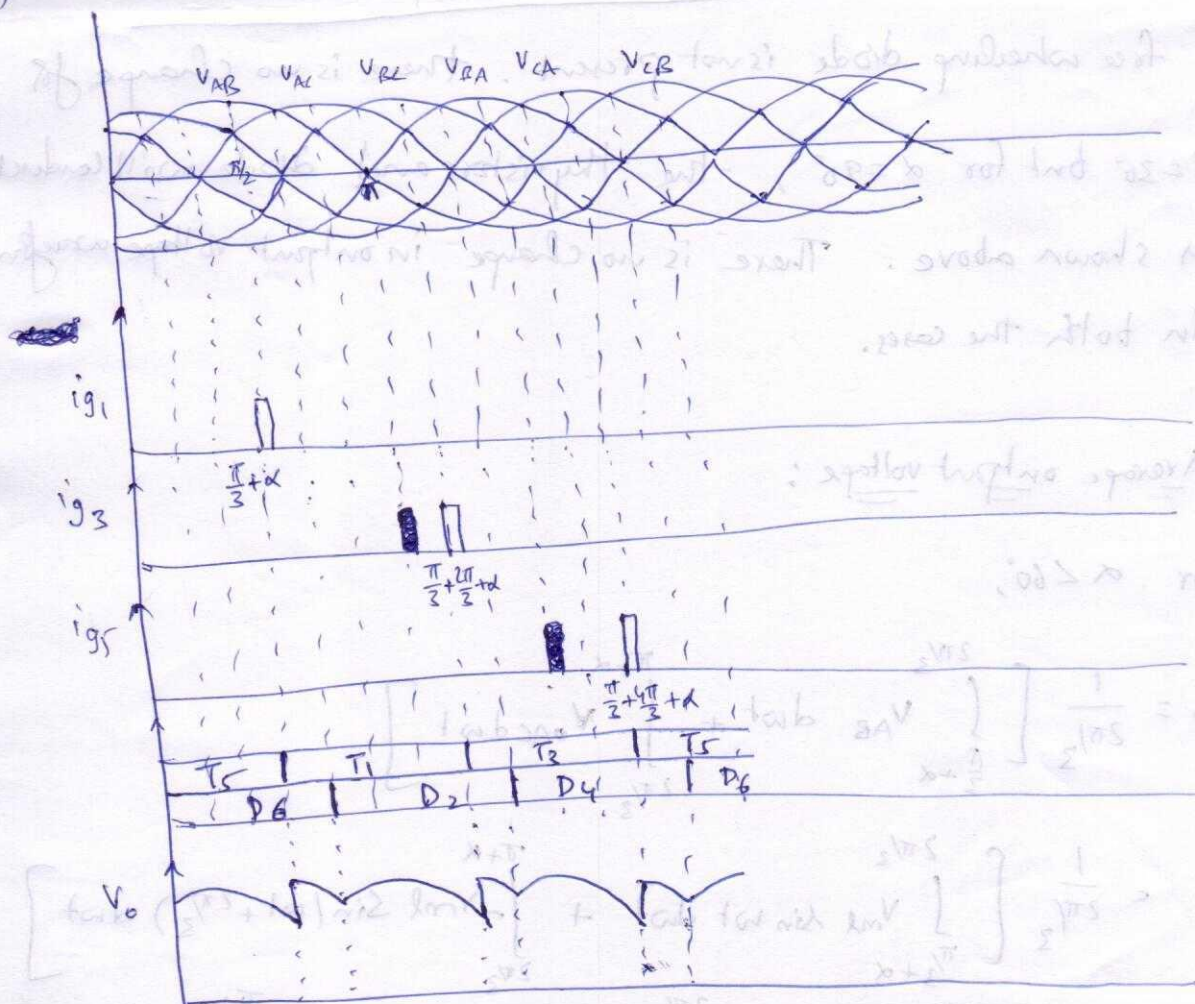

$$\alpha = 90^\circ$$

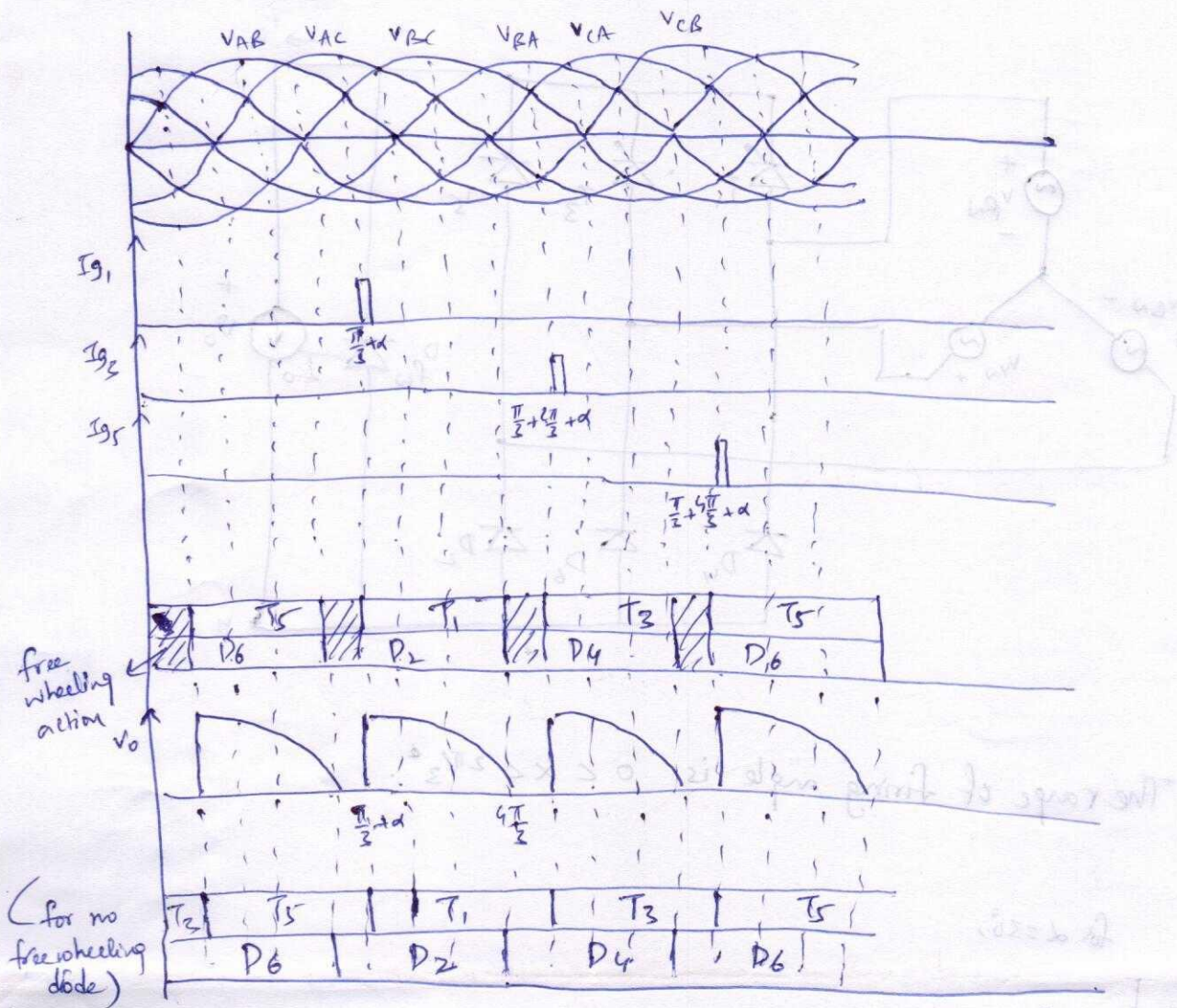

If free wheeling diode is not present, there is no change for $\alpha = 30^\circ$ but for $\alpha = 90^\circ$, the thyristors and diode will conduct as shown above. There is no change in output voltage waveform in both the cases.

c) Average output voltage :

for $\alpha < 60^\circ$,

$$V_o = \frac{1}{2\pi/3} \left[\int_{\pi/3+\alpha}^{2\pi/3} V_{AB} d\omega t + \int_{2\pi/3}^{\pi+\alpha} V_{AC} d\omega t \right]$$

$$= \frac{1}{2\pi/3} \left[\int_{\pi/3+\alpha}^{2\pi/3} V_{ml} \sin \omega t d\omega t + \int_{2\pi/3}^{\pi+\alpha} -V_{ml} \sin(\omega t + 2\pi/3) d\omega t \right]$$

$$= \frac{3V_{ml}}{2\pi} \left[\cos\left(\frac{\pi}{3} + \alpha\right) - \cos\left(2\pi/3\right) + \cos\left(\frac{2\pi}{3} + \pi + \alpha\right) - \cos\left(\frac{2\pi}{3} + \frac{2\pi}{3}\right) \right]$$

$$= \frac{3V_{ml}}{2\pi} \left[\frac{1}{2} \cos \alpha - \frac{\sqrt{3}}{2} \sin \alpha + \frac{1}{2} + \frac{1}{2} \cos \alpha - \left(-\frac{\sqrt{3}}{2} \sin \alpha\right) - \left(-\frac{1}{2}\right) \right]$$

$$= \frac{3V_{ml}}{2\pi} \left[\cos \alpha - \frac{\sqrt{3}}{2} \sin \alpha + \frac{\sqrt{3}}{2} \sin \alpha + 1 \right]$$

$$\boxed{V_o = \frac{3V_{ml}}{2\pi} (1 + \cos \alpha)}$$

$$(V_{ml} = \sqrt{3} V_{m(ph)})$$

When $\alpha > 60^\circ$,

$$V_o = \frac{1}{2\pi/3} \int_{\pi/3 + \alpha}^{4\pi/3} V_{ml} \sin \omega t \, d\omega t$$

$$= \frac{1}{2\pi/3} \int_{\pi/3 + \alpha}^{4\pi/3} -V_{ml} \sin(\omega t + 2\pi/3) \, d\omega t$$

$$= \frac{3V_{ml}}{2\pi} \left[\cos(\omega t + 2\pi/3) \right]_{\pi/3 + \alpha}^{4\pi/3}$$

$$= \frac{3V_{ml}}{2\pi} \left[\cos 2\pi - \cos(\pi + \alpha) \right]$$

$$\boxed{V_o = \frac{3V_{ml}}{2\pi} (1 + \cos \alpha)}$$

$$(V_{ml} = \sqrt{3} V_{m(ph)})$$

$$\left[\left(\frac{1}{2} + \frac{1}{2} \right) \cos - \left(\lambda + \pi + \frac{\pi}{2} \right) \cos + \left(\frac{1}{2} \right) \cos - \left(\lambda + \frac{\pi}{2} \right) \cos \right] \frac{\ln V S}{\pi S}$$

$$\left[\left(\frac{1}{2} \right) - \left(\lambda + \frac{\pi}{2} \right) - \lambda \cos \frac{1}{S} + \frac{1}{S} + \lambda \cos \frac{2V}{S} - \lambda \cos \frac{1}{S} \right] \frac{\ln V S}{\pi S} =$$

$$\left[1 + \lambda \cos \frac{2V}{S} + \lambda \cos \frac{2V}{S} - \lambda \cos \frac{1}{S} \right] \frac{\ln V S}{\pi S} =$$

$$(\ln V S) = \ln V$$

$$\boxed{(\lambda \cos + 1) \frac{\ln V S}{\pi S} = V}$$

id < 2nd

$$\left. \begin{array}{l} \frac{1}{2} \cos \\ \cos \end{array} \right\} \frac{1}{2} = V$$

$$\cos \left(\frac{1}{2} \cos + \cos \right) \ln V = \left[\frac{1}{2} \cos \right]$$

$$\left[\left(\frac{1}{2} \cos + \cos \right) \cos \right] \frac{\ln V S}{\pi S} =$$

$$\left[(\lambda + \pi) \cos - \pi \cos \right] \frac{\ln V S}{\pi S} =$$

$$(\ln V S) = \ln V$$

$$\boxed{(\lambda \cos + 1) \frac{\ln V S}{\pi S} = V}$$