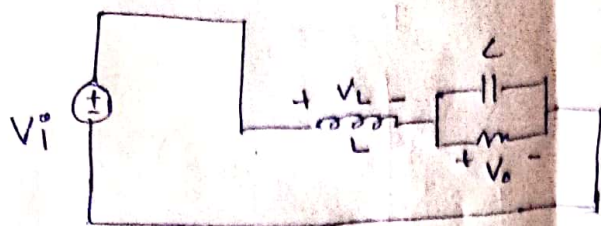



1) When switch is in position 1. for duration DT_s .



$$V_i - V_L - V_o = 0$$

$$V_L = V_i - V_o \rightarrow (1)$$

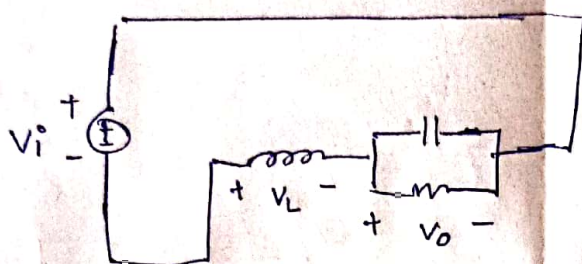When switch is in position 2. for duration $(1-D)T_s$.



$$V_i + V_L + V_o = 0$$

$$V_L = -V_o - V_i \rightarrow (2)$$

Applying volt-second balance for a cycle.


$$(V_i - V_o)DT_s + (-V_o - V_i)(1-D)T_s = 0$$

$$(V_i - V_o)DT_s + (-V_o - V_i)(1-D)T_s = 0$$

$$\Rightarrow V_o = V_i(2D-1)$$

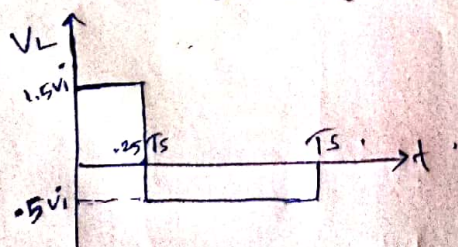
b) Voltage across inductor when $D = 0.25$

$$V_o = V_i(2 \times 0.25 - 1) = -0.5 V_i$$



position ① $\Rightarrow V_L = 1.5 V_i$
position ② $\Rightarrow V_L = -0.5 V_i$


(c) $V_o = V_i(2D-1)$

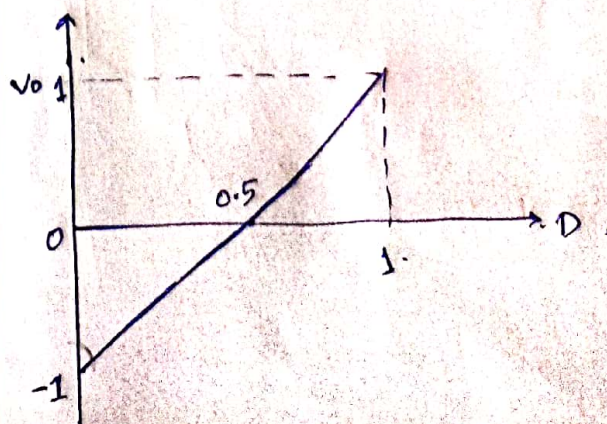


2.

(a)

During Position 1
circuit;

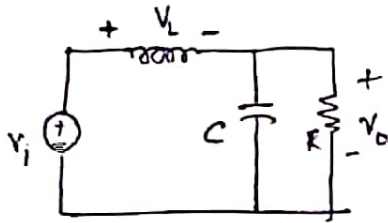

During Position 2
circuit:

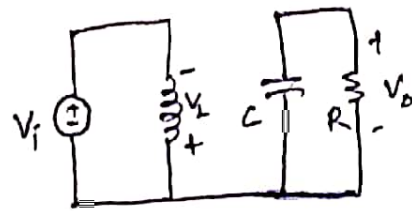

Applying volt-sec balance:

$$(V_i - V_o)DT_s + (-V_i)(1-D)T_s = 0$$

$$\frac{V_o}{V_i} = \frac{2D-1}{D}$$


(b) voltage across Inductor, when $D=0.25$

$$V_o = V_i \left(\frac{2D-1}{D} \right)$$

$$V_o = -2V_i$$


when switch in posⁿ 1, $V_L = V_i - V_o = 3V_i$

" posⁿ 2, $V_L = -V_i$

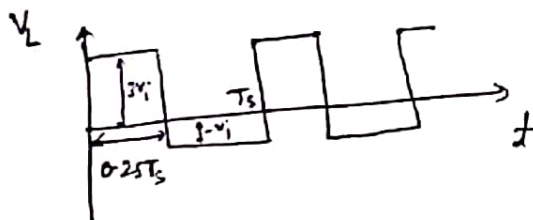


(c) $V_o = \left(\frac{2D-1}{D} \right) V_i$

for $0 \leq D \leq 1$

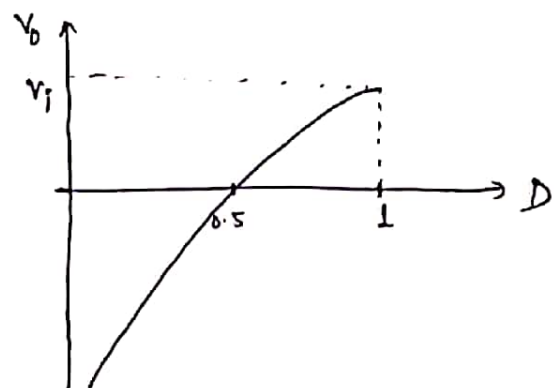

3.


(a). Switch in position ① (DT_s)

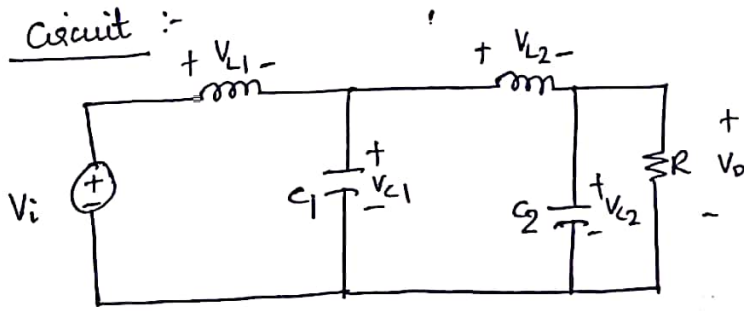

$$V_{L1} = V_i - V_{C1} \quad \text{--- ①}$$

$$V_{L2} = V_{C1} - V_o \quad \text{--- ②}$$

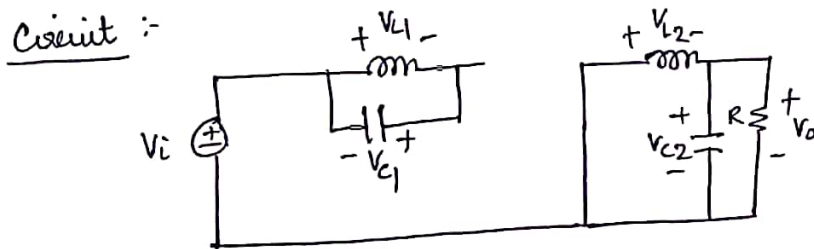Switch in position ② ($D'T_s$) $[D' = 1 - D]$



$$V_{L1} = -V_{C1} \quad \text{--- ③}$$

$$V_{L2} = -V_o \quad \text{--- ④}$$

Applying volt-sec balance in L_1 ,

eqn: ① and ③ $\Rightarrow \langle V_{L1} \rangle = 0 \Rightarrow (V_i - V_{C1})D - V_{C1}D' = 0$

$$V_i D - V_{C1}(D + D') = 0$$

$V_{C1} = V_i D$

Volt-sec balance in L_2 ,

eqn: ② and ④, $(V_{C1} - V_o)D - V_o D' = 0$

$$V_o = V_{C1} D$$

$V_o = D^2 V_i$

⑥

In DTs

$$V_{L1} = V_i - V_{C1} = V_i - DV_i = V_i(1-D)$$


$$V_{L2} = V_{C1} - V_o = DV_i - D^2V_i = V_iD(1-D)$$

$$D = 0.25$$

In D'Ts

$$V_{L1} = -V_{C1} = -DV_i$$

$$V_{L2} = -V_o = -D^2V_i$$

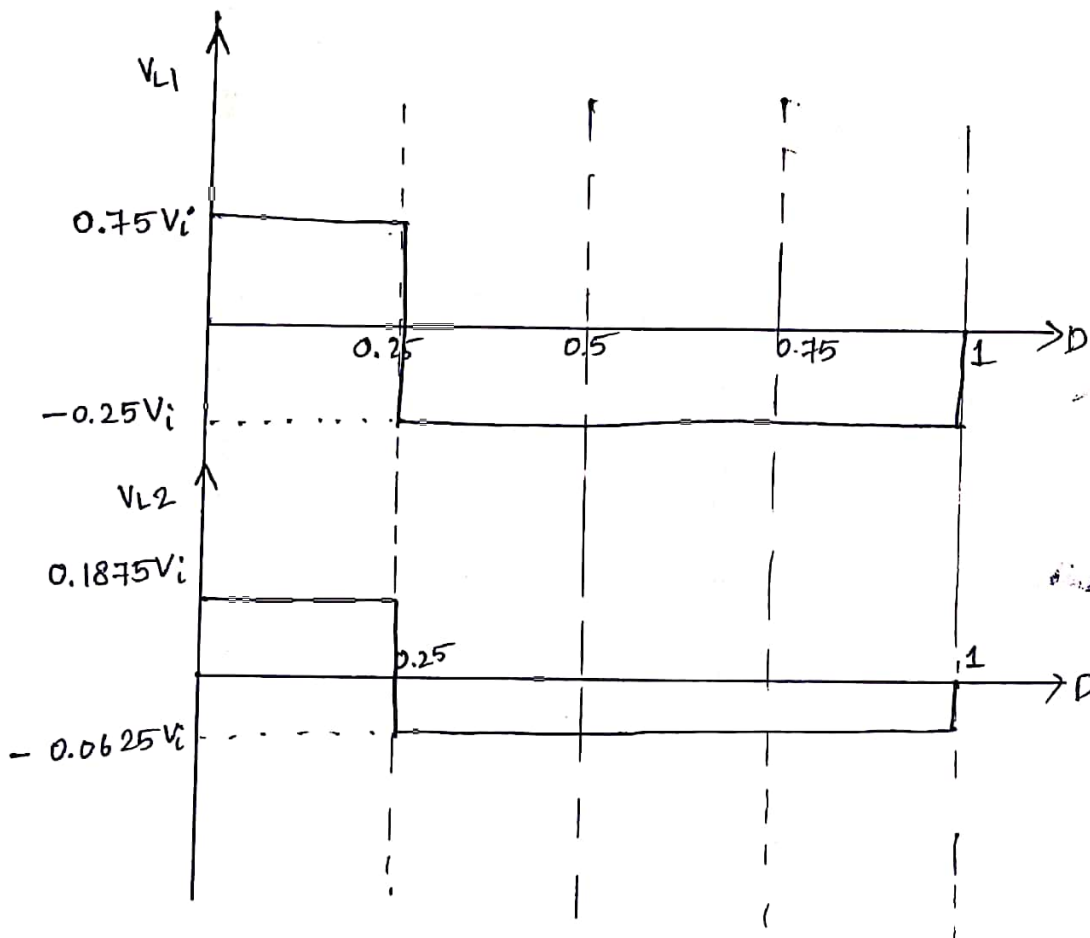

⑦

