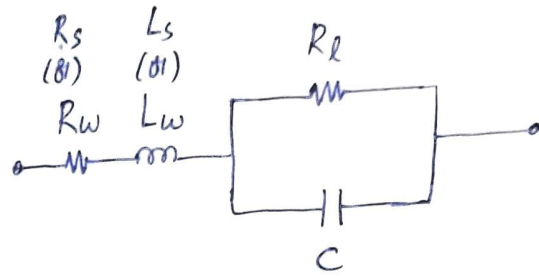


EE6203 : ASSIGNMENT - 4

(Q1)

(1)

R_s / R_w = resistance due to leads / wires.




L_s / L_w = inductance due to leads / wires.

R_l = insulation leakage resistance.

C = capacitance.

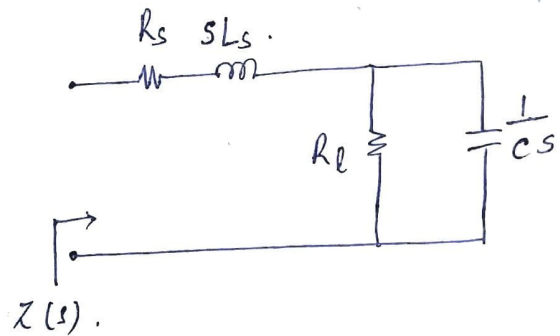(2)

$$Z(s) = R_s + sL_s + \frac{R_l \cdot \frac{1}{sC}}{R_l + \frac{1}{sC}}$$



Simplifying it results as,

$$Z(s) = \frac{(R_s + R_l) \left[s^2 \left(\frac{L_s R_l C}{R_s + R_l} \right) + s \left(\frac{L_s + R_s R_l C}{R_s + R_l} \right) + 1 \right]}{1 + \frac{s}{R_l C}}$$

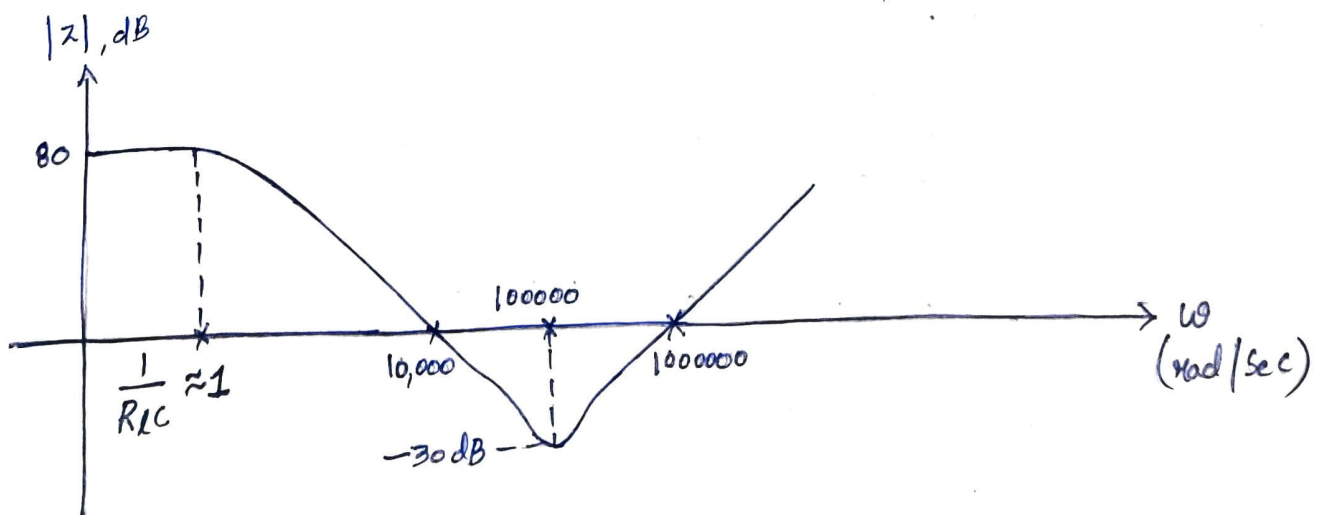


Fig (1)

Magnitude plot of $Z(s)$ is shown in Fig (1).

$$\omega < \frac{1}{R_L C} \Rightarrow |Z| = R_s + R_L$$

$$|Z| \approx R_L \quad (\because R_L \gg R_s)$$

$$\therefore 20 \log |Z| = 80$$

$$|Z| = 10^4$$


$$\therefore R_L = 10 \text{ k}\Omega$$

From the plot $\frac{1}{R_L C} \approx 1$

$$\therefore C = \frac{1}{R_L} = \frac{1}{10,000}$$

$$\therefore C = 100 \mu\text{F}$$

Fig (2) shows the standard model of the capacitor, where

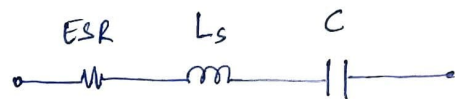

Fig(2)

$$ESR = R_s + \frac{1}{\omega^2 R_L C^2} \longrightarrow \textcircled{1}$$

From Fig (1) at $\omega = 10^5 \text{ rad/sec}$ $|Z| = ESR$.

$$\therefore 20 \log |Z| = -30$$

$$|Z| = 0.0316$$

$$\therefore ESR = 31.6 \text{ m}\Omega$$

From (1) $R_s + \frac{1}{\omega^2 R_L C^2} = 31.6 \times 10^{-3}$


$$R_s + \frac{1}{(10^5)^2 \times 10 \times 10^3 \times (100 \times 10^{-6})^2} = 31.6 \times 10^{-3}$$

$$R_s = 31.599 \text{ m}\Omega$$

From Fig (1) at $\omega = 10^5 \text{ rad/sec}$, network behaves as pure reactive.


$$\therefore \omega = \frac{1}{\sqrt{L_s C}} \Rightarrow 10^5 = \frac{1}{\sqrt{L_s \cdot 100 \times 10^{-6}}}$$

$$\therefore L_s = 1 \mu\text{H}$$

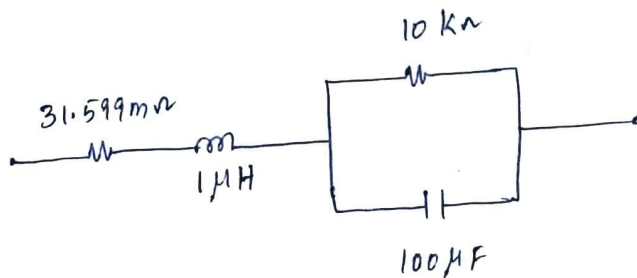

(Q2)

Given

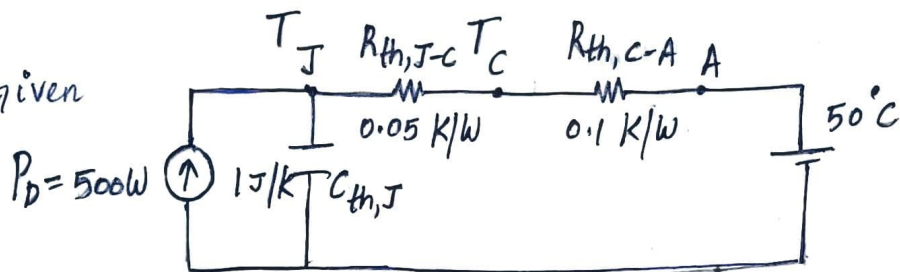

(A) To find steady state temperatures of junction and case.

Case temperature T_C :

$$P_D = \frac{T_C - T_A}{R_{th,C-A}}$$

$$500 = \frac{T_C - 50}{0.1}$$

$$\therefore T_C = 50^\circ\text{C}$$

Junction temperature T_J :

$$P_D = \frac{T_J - T_C}{R_{th,J-C}} \Rightarrow 500 = \frac{T_J - 50}{0.05}$$

$$\therefore T_J = 125^\circ\text{C}$$

(B)

Transient thermal impedance, $Z_{th} = R_{th} (1 - e^{-t/\tau}) = 0.15 (1 - e^{-t/0.15})$

$$\tau = (R_{th,J-C} + R_{th,C-A}) C = (0.05 + 0.1)(1) = 0.15$$

$$\therefore Z_{th}|_{t=0.15} = (0.15) \left[1 - e^{-0.1/0.15} \right]$$


$$Z_{th}|_{t=0.15} = 0.073 \text{ K/W}$$

(C) $\Delta T_J = P_{\text{excess}} Z_{th}$

$$P_{\text{excess}} = \frac{T_{J,\text{max}} - T_{J,\text{ini}}}{Z_{th}}$$

$$= \frac{150^\circ - 125^\circ}{0.073}$$
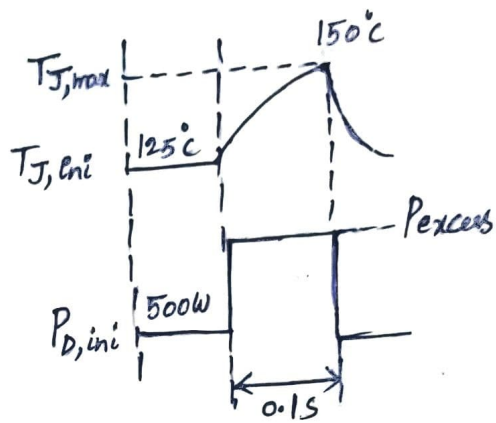
$$P_{\text{excess}} = 342.465 \text{ W}$$



(A)
(Q3) Device - D :-

Average calculation :- $I_{D,\text{avg}}$.

$$I_{D,\text{avg}} = \frac{1}{T} \int_0^T I_m \sin \omega t \, dt$$


$$= \frac{1}{T} \int_0^t I_m \sin \omega t \, dt$$

$$= \frac{1}{200 \times 10^{-6}} \int_0^{50 \times 10^{-6}} 20 \sin \omega t \, dt$$

$$= \frac{20}{200 \times 10^{-6}} \times \frac{1}{\omega} \left[-\cos \omega t \right]_0^t$$

$$= \frac{20}{200 \times 10^{-6} \times 2 \times \pi \times 5000} \left[-\cos(2 \times \pi \times 5000 \times 50 \times 10^{-6}) + 1 \right]$$
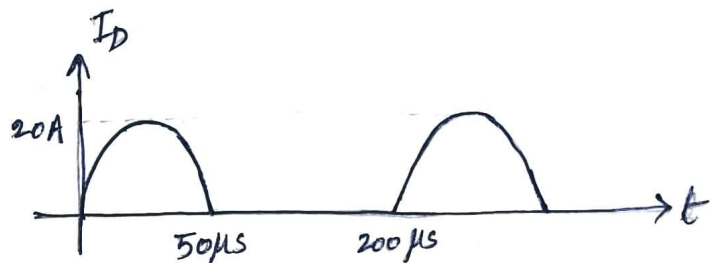
$$\therefore I_{D,\text{avg}} = 3.183 \text{ A}$$



RMS calculation: $I_{D,rms}$

$$I_{D,rms}^2 = \frac{1}{T} \int_0^t I_m^2 \sin^2 \omega t \, dt$$

$$= \frac{I_m^2}{T} \int_0^t \frac{1 - \cos 2\omega t}{2} \, dt$$

$$= \frac{I_m^2}{2T} \left[\int_0^t dt - \int_0^t \cos 2\omega t \, dt \right]$$

$$= \frac{I_m^2}{2T} \left[t - \frac{1}{2\omega} (\sin 2\omega t)_0^t \right]$$

$$= \frac{I_m^2}{2T} \left[t - \frac{\sin 2\omega t}{2\omega} \right]$$


$$= \frac{(20)^2}{2 \times 200 \times 10^{-6}} \left[50 \times 10^{-6} - \frac{\sin(2 \times 2\pi \times 5000 \times 50 \times 10^{-6})}{2 \times 2\pi \times 5000} \right]$$

$$I_{D,rms}^2 = 50$$

$$\therefore I_{D,rms} = 7.071 \, A$$

Device M:

Average Calculation: $I_{M,avg}$

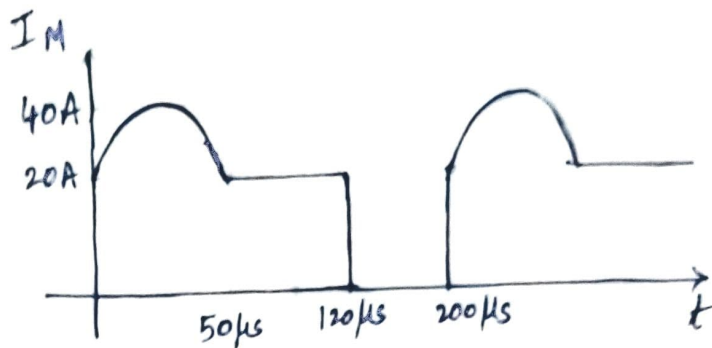

$$I_{M,avg} = \frac{1}{T} \left[\int_0^{50 \times 10^{-6}} (20 + 20 \sin \omega t) dt + \int_{50 \times 10^{-6}}^{120 \times 10^{-6}} 20 dt \right]$$
$$= \frac{1}{T} \left[\int_0^{50 \times 10^{-6}} 20 dt + \int_0^{50 \times 10^{-6}} 20 \sin \omega t dt + \int_{50 \times 10^{-6}}^{120 \times 10^{-6}} 20 dt \right] \quad T = 200 \times 10^{-6}$$

Solving the above integration results in

$$\boxed{I_{M,avg} = 15.183 \text{ A}}$$

RMS Calculation: $I_{M,rms}$


$$I_{M,rms}^2 = \frac{1}{T} \left[\int_0^{50 \times 10^{-6}} (20 + 20 \sin \omega t)^2 dt + \int_{50 \times 10^{-6}}^{120 \times 10^{-6}} (20)^2 dt \right]$$
$$= \frac{1}{200 \times 10^{-6}} \left[\int_0^{50 \times 10^{-6}} 400 dt + \int_0^{50 \times 10^{-6}} 400 \sin^2 \omega t dt + \int_0^{50 \times 10^{-6}} 800 \sin \omega t dt + \int_{50 \times 10^{-6}}^{120 \times 10^{-6}} 400 dt \right]$$

Solving the above integration

$$\boxed{I_{M,rms} = 20.37 \text{ A}}$$

Device A :-

Average Calculation: $I_{A,avg}$

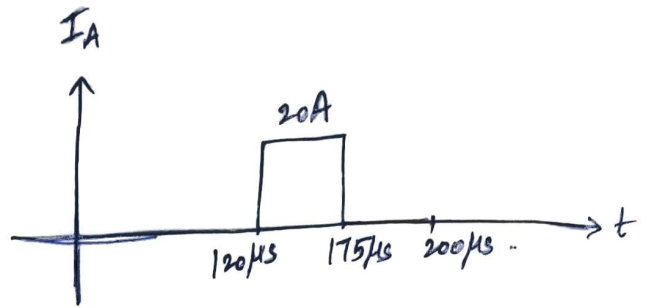

$$I_{A,avg} = \frac{1}{T} \int_0^T i_A(t) dt$$
$$= \frac{1}{200 \times 10^{-6}} \left[\int_{120 \times 10^{-6}}^{175 \times 10^{-6}} 20 dt + \int_{175 \times 10^{-6}}^{200 \times 10^{-6}} 0 dt \right]$$

$$\therefore I_{A,avg} = 5.5 \text{ A}$$


RMS Calculation: $I_{A,rms}$

$$I_{A,rms}^2 = \frac{1}{T} \int_0^T i_A^2(t) dt$$
$$= \frac{1}{200 \times 10^{-6}} \int_{120 \times 10^{-6}}^{175 \times 10^{-6}} (20)^2 dt$$

$$I_{A,rms} = 10.488 \text{ A}$$

(B) To calculate average power loss:-


Device M:-

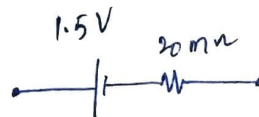

$$P_M = I_{M,avg} (1.5) + I_{M,rms}^2 (20 \times 10^{-3})$$
$$= (15.183) (1.5) + (20.37)^2 (20 \times 10^{-3})$$

$$\therefore P_M = 31.072 \text{ W}$$

Device A:-

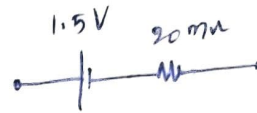


$$P_A = I_{A,avg} (1.5) + I_{A,rms}^2 (20 \times 10^{-3})$$

$$= (5.5) (1.5) + (10.488)^2 (20 \times 10^{-3})$$

$$P_A = 10.449 \text{ W}$$

Device D

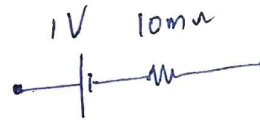



$$P_D = I_{D,avg} (1) + I_{D,rms}^2 (10 \times 10^{-3})$$

$$= (3.183) (1) + (7.071)^2 (10 \times 10^{-3})$$

$$P_D = 3.6829 \text{ W}$$

(Q4)

(A)

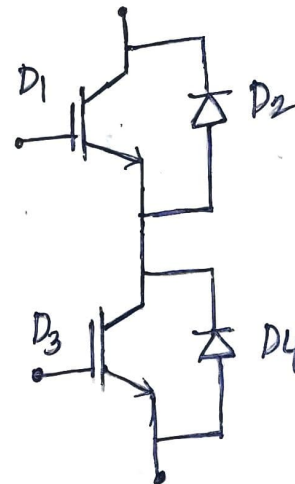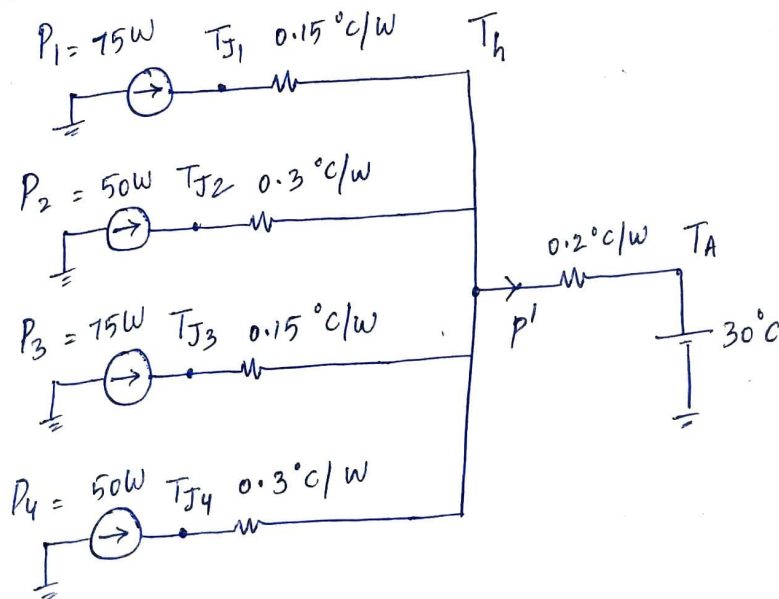

(B) To find heat sink temperature :-

From above figure $P = P_1 + P_2 + P_3 + P_4 = 250W$

$$P = \frac{T_h - T_A}{R_{th, h-A}}$$

$$250 = \frac{T_h - 30}{0.2}$$

$$\boxed{T_h = 80^\circ C}$$

To find junction temperatures :-

Device - 1 :- $P_1 = \frac{T_{J1} - T_h}{R_{th, J-h}} \Rightarrow 75 = \frac{T_{J1} - 80}{0.15}$

$$\boxed{\therefore T_{J1} = 91.25^\circ C}$$

Device - 2 $P_2 = \frac{T_{J2} - T_h}{R_{th, J-h}} \Rightarrow \frac{T_{J2} - 80}{0.3} = 50$

$$\boxed{T_{J2} = 95^\circ C}$$

Device - 3 $P_3 = \frac{T_{J3} - T_h}{R_{th, J-h}} \Rightarrow 75 = \frac{T_{J3} - 80}{0.15}$

$$\boxed{\therefore T_{J3} = 91.25^\circ C}$$

Device - 4 :- $P_4 = \frac{T_{J4} - T_h}{R_{th, J-h}} \Rightarrow 50 = \frac{T_{J4} - 80}{0.3}$

$$\boxed{T_{J4} = 95^\circ C}$$