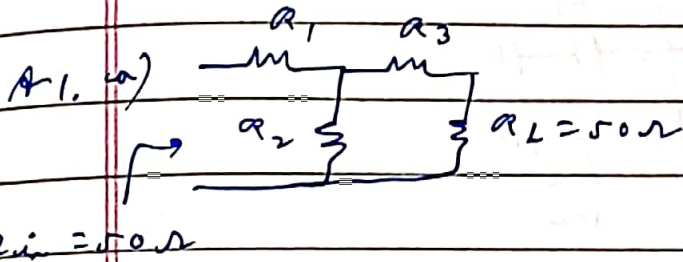


RZIC

24.3.26


Assignment - 1



$$\therefore 50 = R_1 + (R_2 \parallel R_3 + 50)$$


$$\therefore (50 - R_1)(R_2 + R_3 + 50)$$
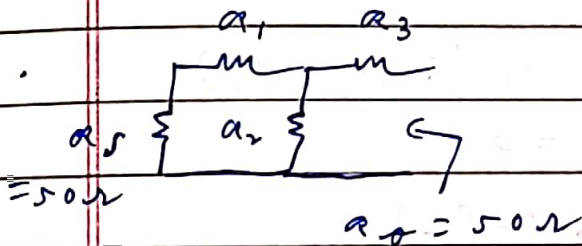
$$= R_2 \times (R_3 + 50) \quad \text{--- (1)}$$



$$\therefore 50 = R_3 + (R_2 \parallel R_1 + 50)$$
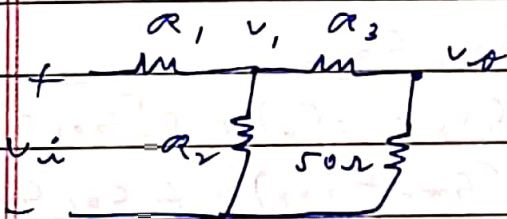
$$(50 - R_3)(R_2 + R_1 + 50) = R_2 \times (R_1 + 50) \quad \text{--- (2)}$$



$$\frac{v_i - v_1}{R_1} = \frac{v_i}{50} \quad (\because R_{in} = 50)$$

$$\therefore v_1 = R_1 v_i \left(\frac{1}{R_1} - \frac{1}{50} \right)$$

$$\frac{v_1}{R_3 + 50} = \frac{v_o}{50} \Rightarrow \left(\frac{R_3 + 50}{50} \right) v_o = R_1 v_i \left(\frac{1}{R_1} - \frac{1}{50} \right)$$

$$\therefore \frac{v_o}{v_i} = \frac{50 R_1}{R_3 + 50} \left(\frac{1}{R_1} - \frac{1}{50} \right) = -6 \text{ dB} = \frac{1}{2} \quad \text{--- (3)}$$

$$\therefore R_3 + 50 = 100 - 2R_1$$

$$R_3 = 50 - 2R_1 \quad \text{--- (4)}$$

Substituting (4) in (1) and (2) :-

$$(50 - R_1)(R_2 + 100 - 2R_1) = R_2 \times (100 - 2R_1)$$

$$\therefore 2R_1^2 - 200R_1 + R_1 R_2 - 50R_2 + 5000 \quad \text{--- (5)}$$

$$2\alpha_1 (\alpha_1 + \alpha_2 + 50) = \alpha_2 (\alpha_1 + 50)$$

$$\therefore 2\alpha_1^2 + \alpha_1 \alpha_2 + 100\alpha_1 - 50\alpha_2 = 0 \quad \text{--- (6)}$$

$$\text{(5) - (6) :- } -300\alpha_1 + 5000 = 0$$


$$\therefore \alpha_1 = \frac{50}{3} \Omega$$

$$\alpha_3 = 50 - \frac{100}{3} = \frac{50}{3} \Omega$$

$$\text{From (6) :- } \alpha_2 (50 - \alpha_1) = 2\alpha_1 (\alpha_1 + 50)$$

$$\alpha_2 \times \frac{100}{3} = \frac{100}{3} \times \frac{200}{3}$$
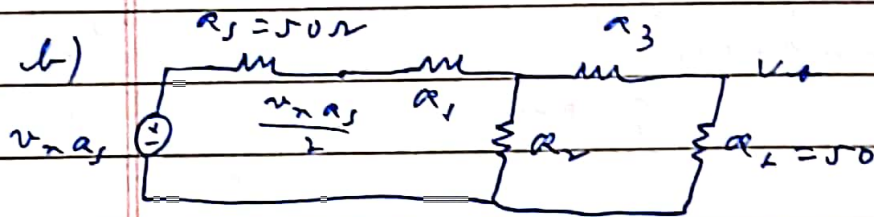
$$\therefore \alpha_2 = \frac{200}{3} \Omega$$



$$\frac{v_{na_s}}{2} = 2v_o \Rightarrow v_o = \frac{v_{na_s}}{4}$$

$$\therefore 5v_{na_s} = \frac{27\alpha_1}{4} = \frac{50 \times 7}{4}$$

$$\text{c) } \alpha_1 \text{ :- Same as (b) as } v_{na_s}$$

$$\therefore 5v_{na_s} = \frac{27\alpha_1}{4} = \frac{50 \times 7}{12}$$




$$i_{n2} = \frac{V}{\alpha_2} + \frac{2V}{\alpha_2 + 50} \quad \left\{ \frac{V}{\alpha_2 + 50} = \frac{V_{th}}{50} \Rightarrow V = V_{th} \frac{(\alpha_2 + 50)}{50} \right.$$

$$\therefore i_{n2} = \frac{V_{th} (\alpha_2 + 50)}{50} \left(\frac{1}{\alpha_2} + \frac{2}{\alpha_2 + 50} \right)$$

$$\therefore V_{th} = \frac{50 \alpha_2 i_{n2}}{\alpha_2 + 50 + 2 \alpha_2} = \frac{50 \times 200 \times i_{n2}}{\frac{400 + 150 \alpha_2 + 50}{3}}$$

$$V_{th} = \frac{50 \times 200}{600} i_{n2} = \frac{50}{3} i_{n2}$$
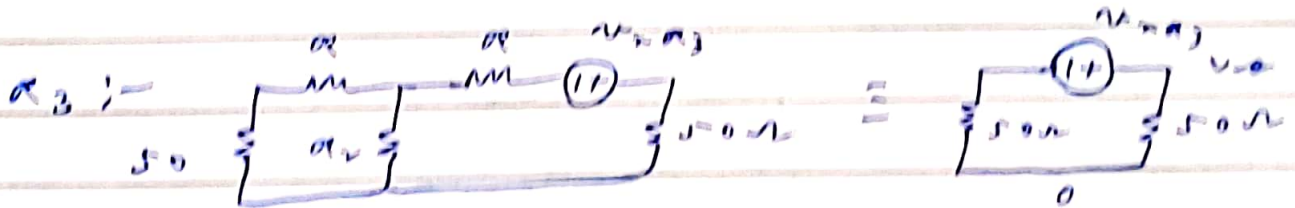
$$\therefore 5 V_{th} = \frac{2500}{1} \times \frac{477}{\alpha_2} = \frac{50}{3} \times 27$$




$$\therefore V_{th} = \frac{V_{th} \alpha_3}{2} \Rightarrow 5 V_{th} = 27 \alpha_3$$

$$5 V_{th} = \frac{50}{3} \times 27$$

$$d) \quad 7 = 1 + \frac{27 \left(\frac{50}{12} + \frac{50}{3} + \frac{50}{3} \right)}{27 \times \frac{50}{4}} = 1 + \frac{1}{3} + \frac{8}{3} = 1 + 3 = 4$$
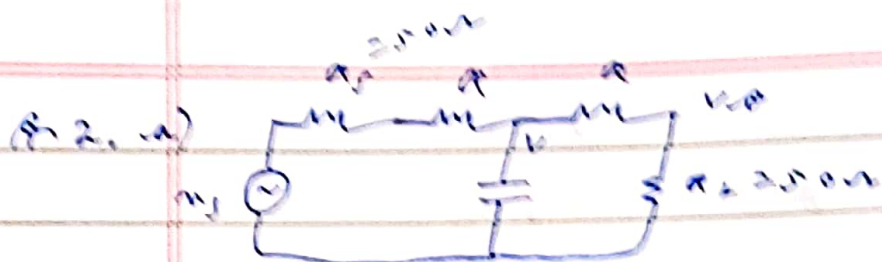
$$\therefore NF = 10 \log_{10}(4) = 6.02 \text{ dB}$$



$$\text{At } s=0, \quad i = \frac{V_s}{2\pi + 100}$$

$$v_o = 50i = \frac{50V_s}{2\pi + 100} \quad \Rightarrow \quad \frac{v_o}{V_s} = \frac{25}{\pi + 50}$$

-12 dB $\Rightarrow$ 4 times attenuation

$$\therefore \frac{1}{4} = \frac{25}{\pi + 50} \quad \Rightarrow \quad \pi = 50$$

$$\frac{V - V_s}{\pi + 50} + V s C + \frac{V}{\pi + 50} = 0 \quad \left\{ \frac{V}{\pi + 50} = \frac{v_o}{50} \right.$$

$$\therefore \frac{V_s}{\pi + 50} = \frac{(\pi + 50)}{50} v_o \left(sC + \frac{2}{\pi + 50} \right)$$

$$\therefore \frac{v_o}{V_s} = \left(\frac{50}{\pi + 50} \right) \times \frac{1}{2 + sC(\pi + 50)}$$

$$\frac{v_o}{V_s} = H(s) = \frac{1}{4[1 + 50sC]}$$

$$\omega - 3 \text{ dB} = f_{\text{ole}} = \frac{1}{50C} = 2\pi \times 10^4$$

$$\therefore C = \frac{10^{-4}}{\pi} \text{ F} = \frac{10}{\pi} \mu\text{F} = 3.183 \mu\text{F}$$


$$b) H(s) = \frac{0.25}{1 + j100\pi f C} = \frac{0.25}{1 + j \frac{f}{10^9}}$$

$$c) v_o = v_{na1} \times H(s)$$

$$\therefore 5v_{na1} = \frac{50 \times 7}{16 [1 + (f \times 10^{-9})^2]} = \frac{50 \times 7}{4 [1 + (f \times 10^{-9})^2]}$$

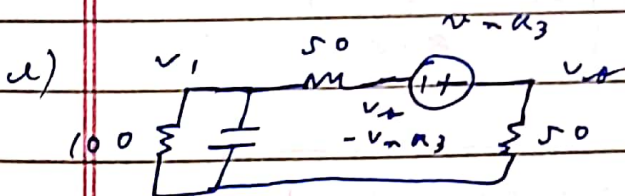d) Same transfer function as a_1 , and $a_1 = a_1$

$$\therefore 5v_{na1} = \frac{50 \times 7}{4 [1 + (f \times 10^{-9})^2]}$$



$$\frac{v_1 - (v_o - v_{na3})}{50} = \frac{v_o}{50}$$

$$\therefore v_1 = 2v_o - v_{na3}$$

$$\frac{-v_o}{50} = \frac{v_1}{100} + v_1 s C = (2v_o - v_{na3}) \left(\frac{1 + 100sC}{100} \right)$$

$$v_{na3} (1 + 100sC) = 2v_o (2 + 100sC)$$

$$v_o = \frac{v_{na3}}{4} \left(\frac{1 + 100sC}{1 + 50sC} \right)$$

$$\therefore 5v_{na3} = \frac{7 \times 50}{4} \left[\frac{1 + (200\pi f C)^2}{1 + (100\pi f C)^2} \right]$$

$$f) \quad Z = 1 + \frac{50 \times 7}{4} \left[1 + 1 + (2 \times 10^{-9})^2 \right] \times \frac{1}{1 + (2 \times 10^{-9})^2}$$

$$\frac{50 \times 7}{4} \times \frac{1}{1 + (2 \times 10^{-9})^2}$$

$$Z = 1 + 2 + 4 \times 10^{-18} = 3 + 4 \times 10^{-18}$$

$$N Z = 10 \log_{10} [3 + 4 \times 10^{-18}]$$

$$g) \quad f = 0.5 \text{ kHz} :- \quad N Z = 10 \log_{10} (3 + 1) = 6.02 \text{ dB}$$

$$f = 1 \text{ kHz} :- \quad N Z = 10 \log_{10} (3 + 4) = 8.45 \text{ dB}$$

$$f = 2 \text{ kHz} :- \quad N Z = 10 \log_{10} (3 + 16) = 12.79 \text{ dB}$$

$$Q3. a) \omega_0 = 2\pi \times 10^9 = \frac{1}{\sqrt{LC}}$$

$$Q_{induct} = 25 \text{ @ } \omega_0$$


$$\therefore 25 = \frac{\omega_0 L}{R}$$

$$\text{At } \omega_0, |H(s)| = Q_{net} = 0.5 = \frac{\omega_0 L}{R + 50}$$

$$\therefore \frac{25}{0.5} = \frac{R + 50}{R} \Rightarrow R = \frac{50}{49} \Omega = 1.02 \Omega$$

$$25 = \frac{2\pi \times 10^9 \times L}{50/49} \Rightarrow L = 4.06 \mu H$$
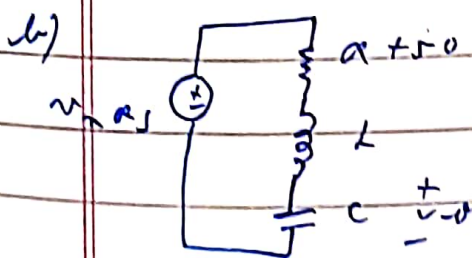
$$C = \frac{1}{L \times 4\pi^2 \times 10^{18}} = 0.24 \mu F$$



$$R_{net} = (R + 50) + sL + \frac{1}{sC}$$

$$i = \frac{v_m \sin \omega_s t}{R_{net}} \Rightarrow v_o = i \times \frac{1}{sC}$$

$$\therefore v_o = v_m \sin \omega_s t \times \frac{1}{s^2 LC + sC(R + 50) + 1}$$

$$\therefore s v_o = \frac{4 \pi \times 10^9}{(1 - \omega^2 LC)^2 + \omega^2 C^2 (R + 50)^2}$$

1) Same $H(s)$ from a as from a_s :-

$$v_o = v_{na}$$

$$1 - \omega^2 LC + j\omega C(R + 50)$$

$$\therefore S_{v_{na}} = \frac{4\pi^2 R}{(1 - \omega^2 LC)^2 + \omega^2 C^2 (R + 50)^2}$$

$$d) \quad Z = 1 + \frac{4\pi^2 R}{4\pi^2 R_s} = 1 + \frac{1}{49} = \frac{50}{49}$$

$$NF = 10 \log_{10} Z = 0.087 \text{ dB}$$


e) Q index doubles $\Rightarrow R$ halves (for same L, ω)

$$\therefore R_{\text{new}} = \frac{25}{49}$$

$$\therefore Z_{\text{new}} = 1 + \frac{25}{50 \times 49} = 1 + \frac{1}{98} = \frac{99}{98}$$


$$\therefore NF_{\text{new}} = 10 \log_{10} Z_{\text{new}} = 0.044 \text{ dB}$$

A 4.

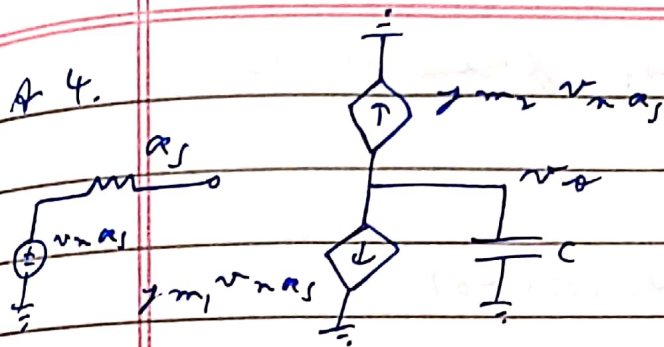

$$\therefore v_{ds} = - \frac{(g_{m1} + g_{m2}) v_{gs}}{sC}$$
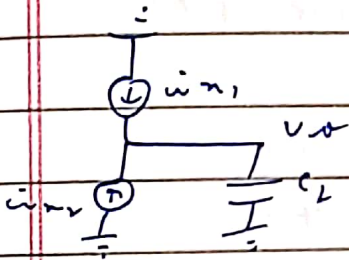
$$\therefore s v_{ds} = \frac{(g_{m1} + g_{m2})^2 \times 4 \times 7 \times R_S}{2\pi f C}$$




$$v_{ds} \times sC_L = i_{n1} + i_{n2}$$

$$\therefore s v_{ds} = \frac{8 \times 7 \times (g_{m1} + g_{m2})}{3 (2\pi f C)^2}$$

$$\therefore \mathcal{F} = 1 + \frac{8 \times 7 \times (g_{m1} + g_{m2}) \times (2\pi f C)^2}{(g_{m1} + g_{m2})^2 \times 4 \times 7 \times R_S (2\pi f C)^2}$$

$$\mathcal{F} = 1 + \frac{2}{3 R_S (g_{m1} + g_{m2})} \quad \left\{ \text{NF} = 10 \log_{10} \mathcal{F} \right.$$


A 5.

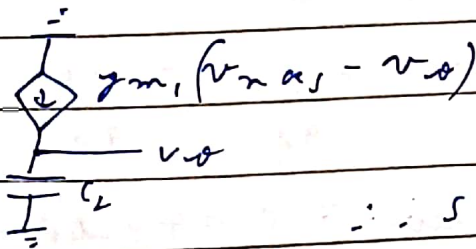

$$\therefore g_{m1} (v_{gs} - v_{ds}) = v_{ds} sC$$


$$v_{ds} (sC + g_{m1}) = g_{m1} v_{gs}$$
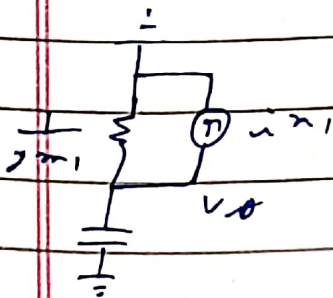
$$\therefore s v_{ds} = \frac{g_{m1}^2}{g_{m1}^2 + (2\pi f C)^2} \times 4 \times 7 \times R_S$$



$$-i_{n1} = v_{ds} (g_{m1} + sC)$$
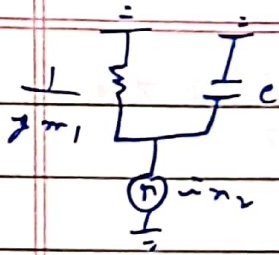
$$\therefore s v_{ds} = \frac{1}{g_{m1}^2 + (2\pi f C)^2} \times \frac{8 \times 7 \times g_{m1}}{3}$$




$$i_{n1} = v_o (g_{m1} + sC)$$

$$\therefore S V_{n_{th}} = \frac{1}{g_{m1}^2 + (2\pi f C)^2} \times \frac{8 k T g_{m1}}{3}$$

$$F = 1 + \frac{\frac{8}{3} k T (g_{m1} + g_{m2})}{4 k T \alpha_s g_{m1}^2}$$

$$F = 1 + \frac{2}{3} \left(\frac{g_{m1} + g_{m2}}{g_{m1}^2 \alpha_s} \right) \quad \left. \vphantom{\frac{2}{3}} \right\} NF = 10 \log_{10} F$$

A 6.

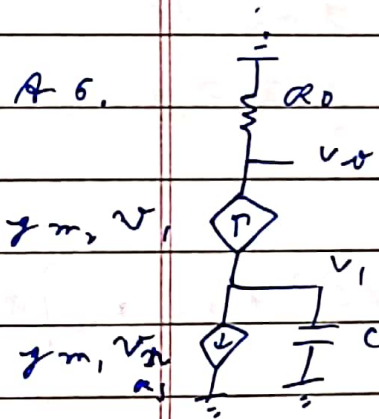


$$g_{m2} v_1 + g_{m1} v_{n1} + v_1 sC = 0$$

$$\therefore v_1 = \frac{-g_{m1} v_{n1} \alpha_s}{g_{m2} + sC}$$


$$v_o = g_{m2} \alpha_o v_1$$
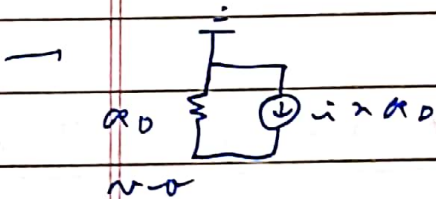
$$\therefore S V_{n_{th}} = \frac{(g_{m1} g_{m2} \alpha_o)^2}{g_{m2}^2 + (2\pi f C)^2} \quad 4 k T \alpha_s$$



$$v_o = i_{n1} \alpha_o \times \alpha_o$$
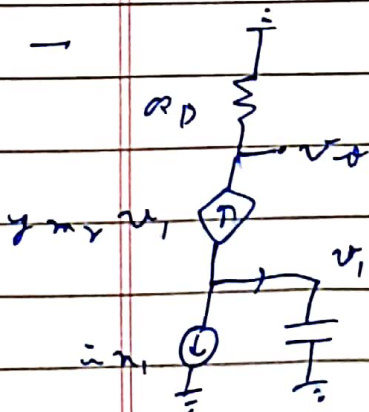
$$\therefore S V_{n_{th}} = 4 k T \alpha_o$$



$$g_{m2} v_1 + i_{n1} + v_1 sC = 0$$


$$v_1 = \frac{-i_{n1}}{g_{m2} + sC}$$

$$v_o = -g_{m2} \alpha_o i_{n1}$$

$$v_o = -g_{m2} \alpha_o i_{n1}$$

$$g_{m2} + sC$$
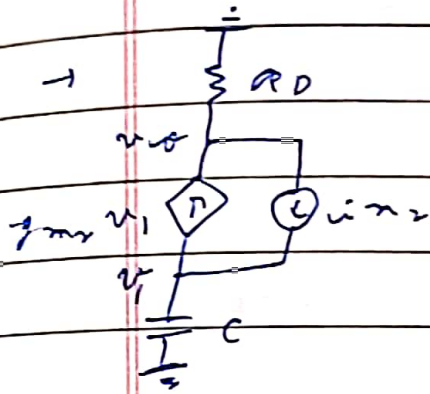
$$S V_{n+2} = \frac{(g_{m2} R_D)^2}{g_{m2}^2 + (2\pi f C)^2} \times \frac{8}{3} kT g_{m1}$$



$$g_{m1} v_1 + v_1 s C = i_{n2}$$

$$v_1 = \frac{i_{n2}}{g_{m1} + s C}$$

$$g_{m1} + s C$$

$$\frac{v_o}{R_D} = -v_1 s C \Rightarrow v_o = -\frac{s C R_D}{g_{m1} + s C} i_{n2}$$

$$\therefore S V_{n+3} = \frac{(2\pi f C R_D)^2}{g_{m1}^2 + (2\pi f C)^2} \times \frac{8}{3} kT g_{m1}$$

$$F = 1 + 4 kT R_D + \frac{8}{3} kT g_{m1} \left[\frac{(2\pi f C)^2 + g_{m1}^2}{g_{m1}^2 + (2\pi f C)^2} \right] R_D^2$$

$$\frac{(g_{m1} g_{m2} R_D)^2 \times 4 kT R_D}{g_{m1}^2 + (2\pi f C)^2}$$

$$F = 1 + \frac{g_{m2}^2 \left(1 + \frac{2}{3} R_D g_{m1} \right) + (2\pi f C)^2 \left(1 + \frac{2}{3} R_D g_{m1} \right)}{(g_{m1} g_{m2})^2 R_D R_S}$$

$$NF = 10 \log_{10} F$$