

$$① \quad f(t) = DV_{in} + \sum_{n=1}^{\infty} \frac{2V_{in}}{n\pi} \sin(n\pi D) \cos(n\omega_s t - n\pi D)$$

$$\text{where, } \omega_s = \frac{2\pi}{T_s}$$

$\Rightarrow$ when, $D = \frac{1}{2}$, all the even harmonics vanishes.

$$② \quad \frac{V_{out}(s)}{V_{sw}(s)} = \frac{\frac{1}{LC}}{s^2 + \frac{1}{R_L C}s + \frac{1}{LC}} = \frac{\omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

$$\Rightarrow \text{natural frequency of oscillations} = \omega_n = \frac{1}{\sqrt{LC}} = 16,939.90892 \text{ rad/sec.}$$

$$\Rightarrow \text{damped frequency of oscillations} = \omega_d = \omega_n \sqrt{1-\xi^2} = 16939.34891 \text{ rad/sec.}$$

$\hookrightarrow$ for $R_L = 5\Omega$

$$\Rightarrow \text{frequency at which } \left| \frac{V_{out}(s)}{V_{sw}(s)} \right| \text{ peak occurs} = \omega \Big|_{\text{Mpeak}} = \omega_n \sqrt{1-2\xi^2} = 16938.78889 \text{ rad/sec}$$


$\hookrightarrow$ for $R_L = 5\Omega$

$$\Rightarrow \text{Resonant frequency is a frequency at which the circuit behaves purely resistive} = \omega_{res} = \sqrt{\frac{1}{LC} \left[1 - \frac{1}{R^2 C} \right]} = 16937.66878 \text{ rad/sec}$$

$\hookrightarrow$ for $R_L = 5\Omega$

$$③ \quad \text{attenuation @ } 200\text{kHz} \text{ is } \underline{\underline{-74.8135 \text{ dB}}}$$

③

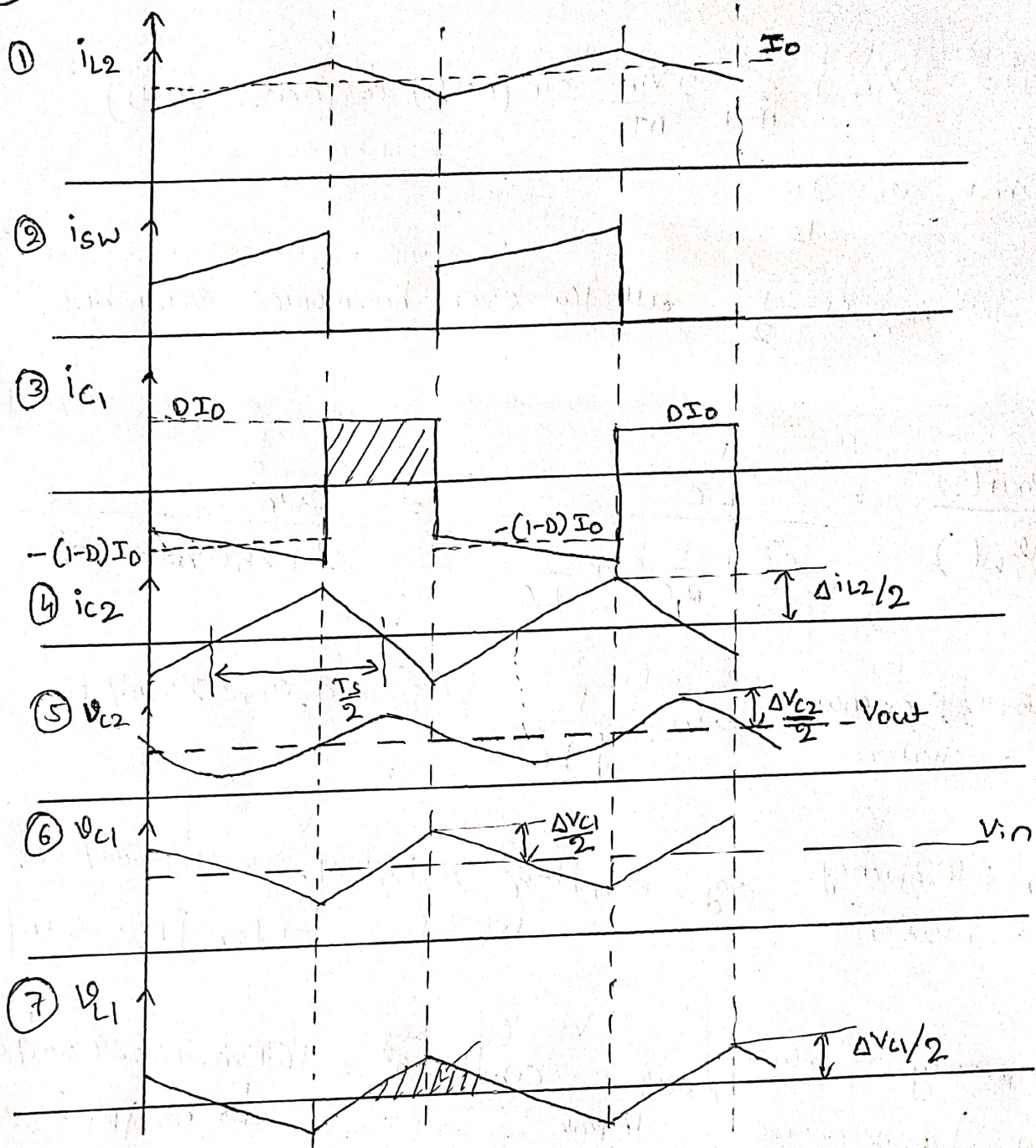

$$L_2 = \frac{(V_{in} - V_{out}) D T_s}{\Delta i_{L2}} = 75.5 \mu H$$


$$C_1 = \frac{D(1-D) I_O T_s}{\Delta v_{C1}} = 5.86 \mu F$$

$$C_2 = \frac{\Delta i_{L2} \cdot T_s}{8 \Delta v_{C2}} = 2.0833 \mu F$$

$$L_1 = \frac{\Delta v_{C1} T_s}{8 \Delta i_{L1}} = 60 \mu H$$

5)


DT_s :-

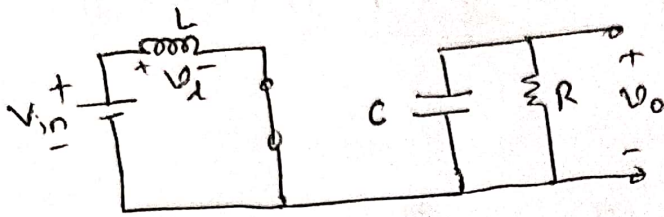

$$V_L = L \frac{di_L}{dt} = V_{in}$$

$$i_C = C \frac{dv_C}{dt} = -\frac{V_O}{R}$$

$(1-D)T_s$

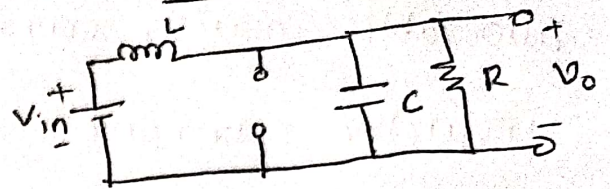

$$V_L = L \frac{di_L}{dt} = V_{in} - V_O$$

$$i_C = C \frac{dv_C}{dt} = i_L - i_O$$

$\Rightarrow$ applying volt-sec balance equation, $\langle V_L \rangle = \frac{1}{T_s} \int_0^{T_s} V_L(t) dt = 0$

and also applying small ripple approximation.

$$\frac{1}{T_s} \left[V_{in} DT_s + (V_{in} - V_O) (1-D) T_s \right] = 0 \Rightarrow \boxed{V_O = \frac{V_{in}}{1-D}}$$

$\Rightarrow$ applying charge-balance equation, $\langle i_C \rangle = \frac{1}{T_s} \int_0^{T_s} i_C(t) dt = 0$

$$\frac{1}{T_s} \left[\left(-\frac{V_O}{R} \right) DT_s + \left(I_L - \frac{V_O}{R} \right) (1-D) T_s \right] = 0$$

$$\Rightarrow \boxed{I_L = I_{in} = \frac{I_O}{1-D}}$$

also, applying small ripple approximation.

Now, during DT_s

$$C \frac{dv_C}{dt} = -\frac{V_O}{R}$$

We will look at their magnitude only.

$$\boxed{C = \frac{V_O DT_s}{R \Delta V_C}}$$

$\therefore$ at, $V_{in} = 5V \Rightarrow D = 0.6667 \Rightarrow \boxed{C = 88.8934 \mu F}$ ✓

at, $V_{in} = 10V \Rightarrow D = 0.3334 \Rightarrow C = 44.4534 \mu F$

Now, to calculate "L", it is mentioned that maximum allowable inductor current ripple is 20% of average inductor current.

$$\text{average inductor current} = I_L = I_{in} = \frac{I_o}{1-D}$$

$$\text{During } DT_s \Rightarrow V_L = L \frac{di_L}{dt} = V_{in} \Rightarrow L = \frac{V_{in} D T_s}{\Delta i_L}$$

$$\text{w.k.t. } V_o = \frac{V_{in}}{1-D} \Rightarrow L = \frac{V_o D(1-D) T_s}{\Delta i_L}$$

it is said that, $(\Delta i_L)_{\max} = 20\% \text{ of } I_L = 20\% \text{ of } \left(\frac{I_o}{1-D} \right)$

$$\therefore L = \frac{V_o D(1-D) T_s}{0.2 \left(\frac{I_o}{1-D} \right)} = \frac{D(1-D)^2 V_o T_s}{0.2 I_o}$$

$$\therefore \boxed{L = \frac{D(1-D)^2 V_o T_s}{0.2 I_o}}$$

at $V_{in} = 5V \Rightarrow I_{in} = 3A$, $\boxed{D = 0.6667}$, $\boxed{L = 111.1 \mu H}$
 $\boxed{V_o = 15V}$ $\boxed{I_o = 1A}$ $\boxed{T_s = 20 \mu s}$

at $V_{in} = 10V \Rightarrow I_{in} = 1.5A$, $D = 0.3334$, $\boxed{L = 222.22 \mu H}$ ✓
 $V_o = 15V$, $I_o = 1A$, $T_s = 20 \mu s$

so, if you use the value of $L = 222.22 \mu H$ at all other input voltages b/w 5V & 10V the ripple % will be less than 20%.

let us, look at the equation, $L = D(1-D)^2 \frac{V_o T_s}{0.2 I_o}$

let us generalize this, instead of 0.2, i will take 'x'

where $0 \leq x \leq 1$

$$\therefore L = D(1-D)^2 \frac{V_o T_s}{x I_o}$$

We can study, for a given value of 'L', at what 'D', x will be maximum, $\therefore$ we are interested in maximum % ripple?

$$\therefore x = D(1-D)^2 \frac{V_o T_s}{L I_o}$$

$$\frac{dx}{dD} = (3D^2 - 4D + 1) \frac{V_o T_s}{L I_o} = 0 \quad \{ \text{To maximize} \}$$

$$\therefore (D-1)(3D-1) = 0 \Rightarrow \boxed{D=1} \text{ or } \boxed{D=\frac{1}{3}}$$

you, can verify that $\boxed{D=\frac{1}{3}}$ is a maximum point

and $\boxed{D=1}$ is a minimum point.


$\therefore$ maximum ripple % will occur at $\boxed{D=0.3334}$

which JUST happens to be in our case ~~highest~~ ^{highest}

input voltage, i.e. at $V_{in}=10V$, $\boxed{D=0.3334}$ ^{for our case}

$\Rightarrow$ With changing input voltage the ~~duty~~ duty ratio and the average inductor current changes. The simple $D*(1-D)$ will hold only when the average inductor current remains constant, and only the ripple will change due to duty ratio.

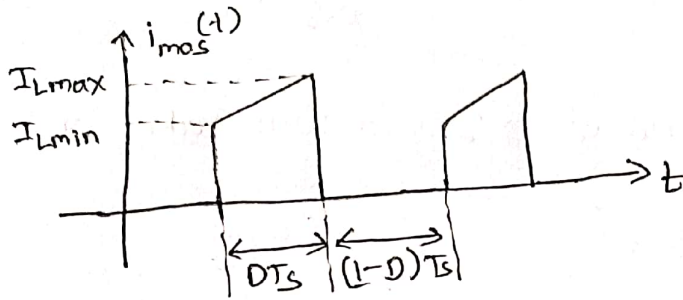① Determination of rms value of MOSFET current.



$$i_{mos}(t) = \begin{cases} \frac{(I_{Lmax} - I_{Lmin})}{DT_s} t + I_{Lmin}; & DT_s \\ 0; & (1-D)T_s \end{cases}$$

$$I_{mos,rms}^2 = \frac{1}{T_s} \int_0^{DT_s} \left[\frac{(I_{Lmax} - I_{Lmin})}{DT_s} t + I_{Lmin} \right]^2 dt$$

$$I_{mos,rms}^2 = \frac{1}{T_s} \left[\frac{\left(\frac{(I_{Lmax} - I_{Lmin})}{DT_s} t + I_{Lmin} \right)^3}{3 \frac{(I_{Lmax} - I_{Lmin})}{DT_s}} \right]_0^{DT_s}$$

$$I_{mos,rms}^2 = \frac{1}{T_s} \times \frac{DT_s}{3 [I_{Lmax} - I_{Lmin}]} \left[\left(\frac{(I_{Lmax} - I_{Lmin})}{DT_s} \cdot DT_s + I_{Lmin} \right)^3 - I_{Lmin}^3 \right]$$


$$I_{mos,rms}^2 = \frac{D}{3(I_{Lmax} - I_{Lmin})} \left[\left[(I_{Lmax} - I_{Lmin}) + I_{Lmin} \right]^3 - I_{Lmin}^3 \right]$$

$$I_{mos,rms}^2 = \frac{D}{3(I_{Lmax} - I_{Lmin})} [I_{Lmax}^3 - I_{Lmin}^3]$$

$$I_{mos,rms}^2 = \frac{D}{3(I_{Lmax} - I_{Lmin})} (I_{Lmax} - I_{Lmin}) [I_{Lmax}^2 + I_{Lmin}^2 + I_{Lmax} I_{Lmin}]$$

$$\therefore I_{mos,rms} = \sqrt{\frac{D}{3} [I_{Lmax}^2 + I_{Lmin}^2 + I_{Lmax} I_{Lmin}]}$$

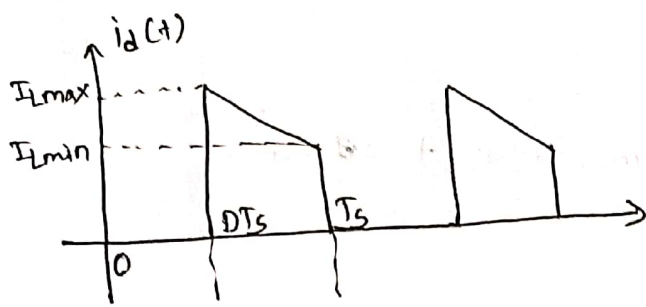Determination of RMS Value of Diode Current



$$i_d(t) = \begin{cases} \frac{I_{Lmin} - I_{Lmax}}{(1-D)T_s} t + I_{Lmax} ; DT_s < t < T_s \\ 0 ; 0 < t < DT_s \end{cases}$$

$$\Rightarrow I_{drms}^2 = \frac{1}{T_s} \int_{DT_s}^{T_s} \left[\frac{I_{Lmin} - I_{Lmax}}{(1-D)T_s} t + I_{Lmax} \right]^2 dt \quad \left| \begin{array}{l} \text{let} \\ a = \frac{I_{Lmin} - I_{Lmax}}{1-D} \end{array} \right.$$

$$\therefore I_{drms}^2 = \frac{1}{T_s} \int_{DT_s}^{T_s} \left[\frac{a}{T_s} t + I_{Lmax} \right]^2 dt$$

$$I_{drms}^2 = \frac{1}{T_s} \left[\frac{\left[\frac{a}{T_s} t + I_{Lmax} \right]^3}{3 \left(\frac{a}{T_s} \right)} \right]_{DT_s}^{T_s}$$

$$I_{drms}^2 = \frac{1}{T_s} \times \frac{T_s}{3a} \left[\left[\frac{a}{T_s} \cdot T_s + I_{Lmax} \right]^3 - \left[\frac{a}{T_s} \cdot DT_s + I_{Lmax} \right]^3 \right]$$

$$I_{drms}^2 = \frac{1}{3a} \left[(a + I_{Lmax})^3 - (aD + I_{Lmax})^3 \right]$$

$$I_{drms}^2 = \frac{1}{3a} \left[\left[a^3 + I_{Lmax}^3 + 3a^2 I_{Lmax} + 3a I_{Lmax}^2 \right] - \left[a^3 D^3 + I_{Lmax}^3 + 3a^2 D^2 I_{Lmax} + 3a D I_{Lmax}^2 \right] \right]$$

$$I_{drms}^2 = \frac{1}{3a} \left[a^3 (1-D^3) + 3a^2 I_{Lmax} (1-D^2) + 3a I_{Lmax}^2 (1-D) \right]$$

$$I_{drms}^2 = \frac{1}{3a} \left[a^3 (1-D)(1+D^2+D) + 3a^2 I_{Lmax} (1-D)(1+D) + 3a I_{Lmax}^2 (1-D) \right]$$

$$I_{drms}^2 = \frac{(1-D)}{3} \left[a^2 (1+D^2+D) + 3a I_{Lmax} (1+D) + 3 I_{Lmax}^2 \right]$$

substitute for a

$$I_{drms}^2 = \frac{(1-D)}{3} \left[\left[\frac{(I_{Lmin} - I_{Lmax})^2 (D^2 + D + 1)}{(1-D)^2} \right] + \left[\frac{3(I_{Lmin} - I_{Lmax}) I_{Lmax} (1+D)}{(1-D)} \right] + 3 I_{Lmax}^2 \right]$$

$$I_{drms} = \sqrt{\frac{(1-D)}{3} \left[\left[\frac{(I_{Lmin} - I_{Lmax})^2 (D^2 + D + 1)}{(1-D)^2} \right] + \left[\frac{3(I_{Lmin} - I_{Lmax}) I_{Lmax} (1+D)}{(1-D)} \right] + 3 I_{Lmax}^2 \right]}$$