

Assignment-2 - Solutions

① for, buck-boost, (CCM) $V_o = \frac{-V_{in} D}{1-D} \Rightarrow \text{if } V_o = -V_{in}, \text{ then } \boxed{D = \frac{1}{2}}$

② $V_{out} = V_{in}$

③ ZERO

④ Flux Linkage

⑤ Decrease

⑥ $\boxed{I_{avg} = \frac{10}{\pi} = 3.1831 A}, \quad \boxed{I_{rms} = \frac{10}{2} = 5 A}$

$$V_t I_{avg} + I_{rms}^2 r_d = 2.6465 W$$

⑦ during t_o :-

$$\text{power loss} = \frac{1}{2} \times t_o \times I_o \times V_k \times f_s = 0.0225 W$$

during t_a :-

$$\text{power loss} = \frac{1}{2} \times t_a \times I_{RM} \times V_k \times f_s = 0.005625 W$$

during t_b :-

$$\text{power loss} = \frac{(V_R - 2V_k) I_{RM} t_b f_s}{6} = 0.663667 W$$

$$\text{power loss during } (t_a + t_b) = \underline{0.669292 W.}$$

$$\text{power loss during } (t_o + t_a + t_b) = \underline{0.691792 W}$$

$$(8) \quad t_{\text{on}} = 5 \mu\text{s} \quad , \quad \text{S.F} = \frac{t_b}{t_a} = 0.5$$

$$t_{\text{on}} = t_a + t_b \Rightarrow t_{\text{on}} = t_a \left[1 + \frac{t_b}{t_a} \right]$$

$$\therefore t_a = \frac{5 \mu}{1.5} = 3.3334 \mu\text{s}$$

$$t_b = 1.6667 \mu\text{s}$$

$$\therefore I_{\text{RM}} = t_a \frac{di}{dt} = 3.3334 \mu \times \frac{80 \text{ A}}{\mu\text{s}} = \underline{266.672 \text{ A}}$$

$$\text{QRP} = \frac{1}{2} t_{\text{on}} \cdot I_{\text{RM}} = \underline{666.68 \mu\text{C}}$$

$$(10) \quad r(T_j) = \left[\frac{1.8R - R}{125 - 25} \right] (T_j - 25) + R$$

$$\text{for } r_1 \quad R = 1.8$$


$$r_1(T_j = 105^\circ) = 2.952 \Omega$$

$$\text{for } r_2 \quad R = 2$$

$$r_2(T_j = 105^\circ) = 3.28 \Omega$$

$$\text{for } r_3 \quad R = 2.2$$

$$r_3(T_j = 105^\circ) = 3.608 \Omega$$

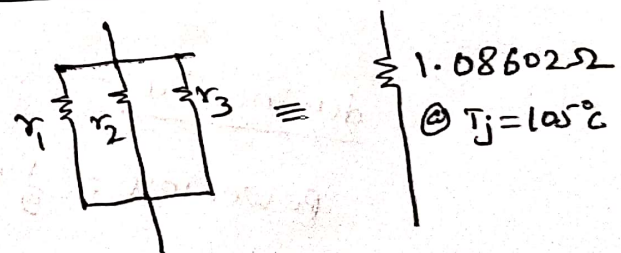

$$\text{power loss in } r_1 = \underline{4.994 \text{ W}}$$

$$\text{power loss in } r_2 = \underline{4.49481 \text{ W}}$$


$$\text{power loss in } r_3 = \underline{4.0862 \text{ W}}$$

$$\text{Total power loss} = \underline{13.575 \text{ W}}$$


$$I_{\text{RMS}} = I_0 \sqrt{D}$$

$$\boxed{I_{\text{RMS}} = 3.535534 \text{ A}}$$
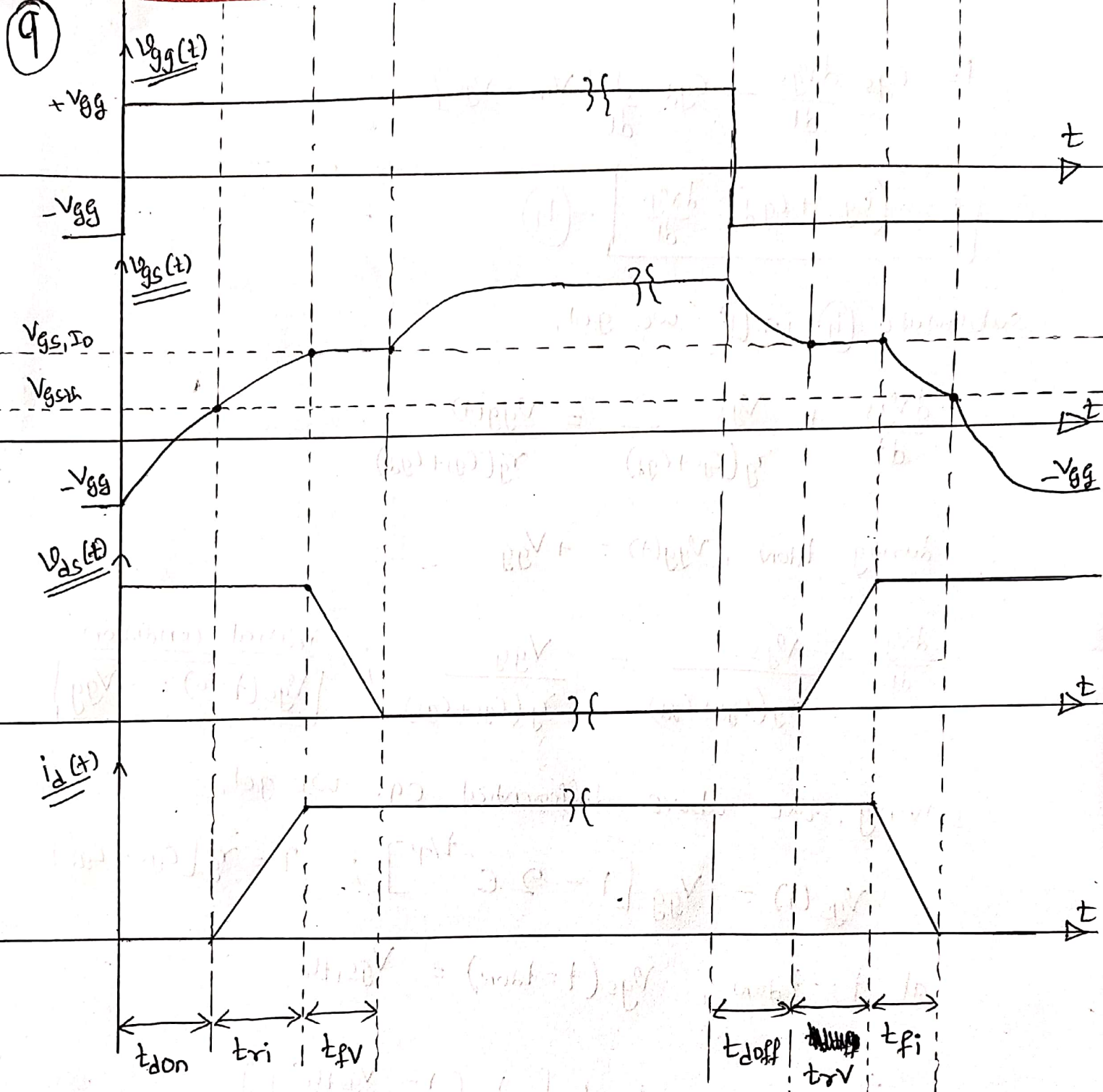
$$\therefore \underline{50\% \text{ duty.}}$$



(a) During turn-on delay (t_{don}):-

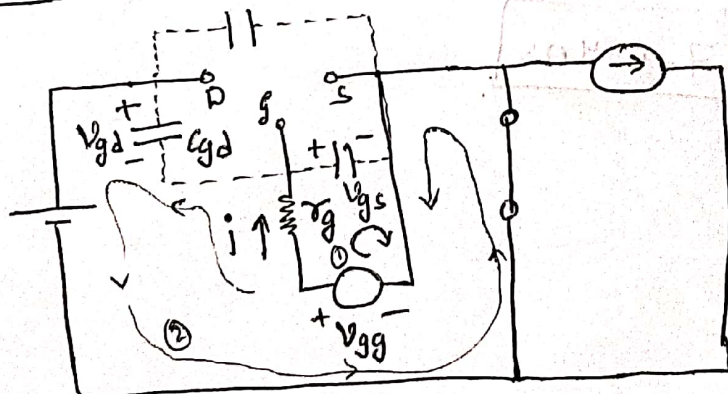

$$V_{gg}(t) - i r_g - V_{gs}(t) = 0 \quad (1)$$

$$V_{gg}(t) - i r_g + V_{gd}(t) - V_{in} = 0 \quad (2)$$

from (1) & (2)

$$V_{gs} + V_{gd} = V_{in} \quad (3)$$

$$\text{now, } i = C_{gs} \frac{dV_{gs}}{dt} + \left[-C_{gd} \frac{dV_{gd}}{dt} \right]$$

$$i = C_{gs} \frac{dv_{gs}}{dt} - C_{gd} \frac{d}{dt} [V_{in} - v_{gs}]$$

$$i = (C_{gs} + C_{gd}) \frac{dv_{gs}}{dt} \quad \text{--- (4)}$$

substitute (4) in (1) we get,

$$\frac{dv_{gs}}{dt} + \frac{v_{gs}}{\tau_g(C_{gs} + C_{gd})} = \frac{V_{gg}(t)}{\tau_g(C_{gs} + C_{gd})}$$

$\therefore$ during t_{don} , $V_{gg}(t) = +V_{gg}$

$$\frac{dv_{gs}}{dt} + \frac{v_{gs}}{\tau_g(C_{gs} + C_{gd})} = \frac{V_{gg}}{\tau_g(C_{gs} + C_{gd})} \quad ; \quad \begin{array}{l} \text{initial condition} \\ v_{gs}(t=0) = -V_{gg} \end{array}$$

solving, the above differential eq. we get,


$$v_{gs}(t) = V_{gg} [1 - 2e^{-t/\tau}] ; \quad \tau = \tau_g(C_{gs} + C_{gd})$$

at $t = t_{don}$, $v_{gs}(t = t_{don}) = V_{gs,th}$

$$\therefore t_{don} = -\tau \times \ln \left[\frac{1}{2} \left[1 - \frac{V_{gs,th}}{V_{gg}} \right] \right]$$

$$\therefore t_{don} = 57.689 \text{ ns}$$

b) during current rise interval (t_{ri})

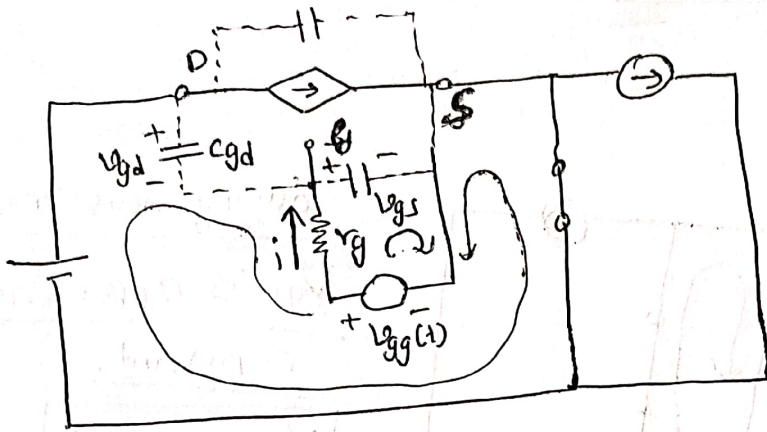

$$v_{gg}(t) - i r_g - v_{gs} = 0 \quad (1)$$

$$v_{gg}(t) - i r_g + v_{gd} - V_{in} = 0 \quad (2)$$

from (1) + (2)

$$v_{gs} + v_{gd} = V_{in} \quad (3)$$

$$i = C_{gs} \frac{dv_{gs}}{dt} + \left[-C_{gd} \frac{dv_{gd}}{dt} \right]$$

$$i = (C_{gs} + C_{gd}) \frac{dv_{gs}}{dt} \quad (4)$$

Substitute (4) in (1) we get,

$$\frac{dv_{gs}}{dt} + \frac{v_{gs}}{r_g(C_{gs} + C_{gd})} = \frac{V_{gg}}{r_g(C_{gs} + C_{gd})}$$

In this interval
initial condition

$$v_{gs}(t=0) = V_{gs,th}$$


Solution to above diff. eq. $\Rightarrow v_{gs}(t) = V_{gg} + \left[V_{gs,th} - V_{gg} \right] e^{-t/\tau}$; $\tau = r_g(C_{gs} + C_{gd})$

a) $t = t_{ri} \Rightarrow v_{gs}(t) = V_{gs,Io}$

$$\therefore t_{ri} = -\tau \times \ln \left[\frac{V_{gs,Io} - V_{gg}}{V_{gs,th} - V_{gg}} \right] = 18.31 \text{ ns}$$

$$\therefore \boxed{t_{ri} = 18.31 \text{ ns}}$$

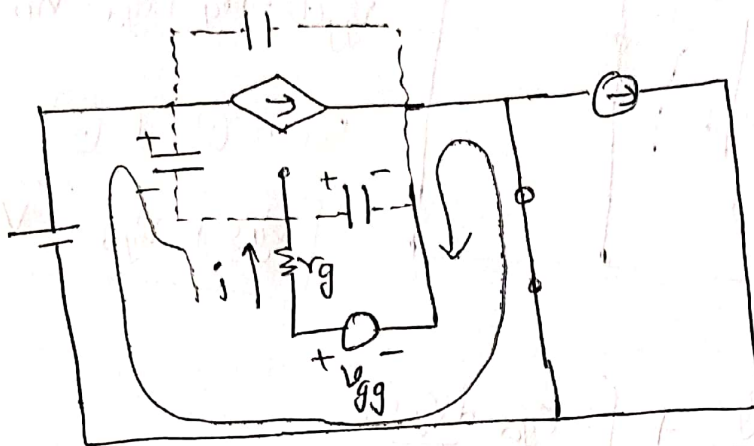(C) during voltage fall interval (t_{fv}):-



during this interval
 V_{gs} is approximately
constant.

$$V_{GS, IO} = 7V$$

$$V_{gd} + V_{gs} = V_{ds}, \text{ as } V_{gs} \text{ is constant}$$

$$\frac{dv_{gd}}{dt} = \frac{dv_{ds}}{dt}$$

$$-C_{gd} \frac{dv_{gd}}{dt} = \frac{V_{gg} - V_{gs,IO}}{r_g}$$

$$\frac{dv_{gs}}{dt} = - \left[\frac{V_{gg} - V_{gs, I_0}}{r_g C_{gd}} \right]$$


$$\therefore V_{ds}(t) = V_{in} - \left[\frac{V_{gg} - V_{gs, I_0}}{r_g C_{gd}} t \right]$$

$$\therefore \textcircled{a} \quad t = t_{fv} \Rightarrow v_d \approx 0$$

$$\therefore t_{fv} = \frac{V_{in} \times R_g \times C_{gd}}{V_{gg} - V_{gs,IO}} = 281.25 \text{ ns.}$$

$$\therefore t_{fv} = 281.25 \text{ ns}$$

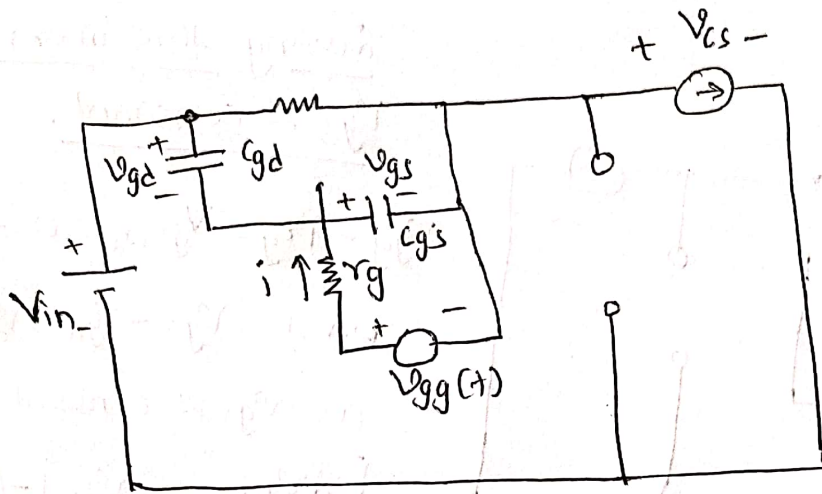(d) during turn-off delay. (t_{doff}):- $V_{gg}(t) = -V_{gg}$



$$V_{gg}(t) - i r_g - V_{gs} = 0 \quad (1)$$

$$V_{gg}(t) - i r_g + V_{gd} - V_{in} - V_{cs} = 0 \quad (2)$$

$$V_{cs} = V_{in} - I_o r_{aon}$$

approximately

$$V_{cs} \approx V_{in}$$

$$\therefore \text{eq. (2)} \rightarrow V_{gg}(t) - i r_g + V_{gd} = 0 \quad (3) \Rightarrow \text{from (1) \& (3)} \quad \boxed{V_{gs} = -V_{gd}}$$

$$i = C_{gs} \frac{dV_{gs}}{dt} + \int -C_{gd} \frac{dV_{gd}}{dt} \Rightarrow i = (C_{gs} + C_{gd}) \frac{dV_{gs}}{dt} \quad (4)$$

$$\text{substituting (4) in (1)} \Rightarrow \frac{dV_{gs}}{dt} + \frac{V_{gs}}{r_g(C_{gs} + C_{gd})} = \frac{-V_{gg}}{r_g(C_{gs} + C_{gd})}$$


solving the differential equation, we get,

$$V_{gs} = -V_{gg} + 2V_{gg} e^{-t/\tau}; \quad \tau = r_g(C_{gs} + C_{gd})$$

$$\therefore t_{doff} = -\tau \ln \left[\frac{V_{gs, I_o} + V_{gg}}{2V_{gg}} \right] \quad \because \begin{array}{|l} \text{at } t = t_{doff} \\ \downarrow \\ V_{gs}(t) = V_{gs, I_o} \end{array}$$

$$\therefore \boxed{t_{doff} = 17.833 \text{ ns}}$$

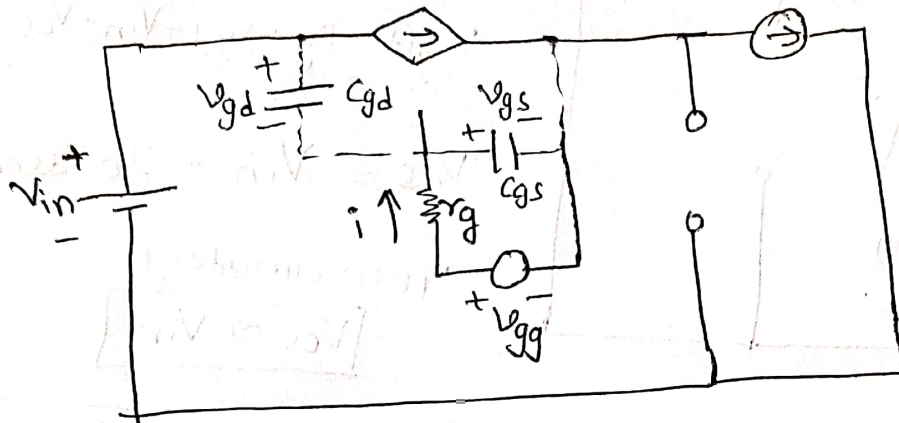(e) during voltage rise interval (t_{rv}):-



during this interval
 $V_{gs} \approx \text{constant}$.

$$V_{gg} - i r_g - V_{gs,IO} = 0 \quad (1)$$

$$\text{w.k.t. } V_{gs} + V_{gd} = V_{ds} \quad (2)$$

$\therefore$ as $V_{gs} \approx \text{constant}$

$$\boxed{\frac{dV_{gd}}{dt} = \frac{dV_{ds}}{dt}} \quad (3)$$

$$\therefore i = \frac{V_{gg}(t) - V_{gs,IO}}{r_g} = \frac{-V_{gs,IO} - V_{gs,IO}}{r_g}$$

$$-C_{gd} \frac{dV_{gd}}{dt} = - \left[\frac{V_{gs,IO} + V_{gs,IO}}{r_g} \right], \text{ as } \frac{dV_{gd}}{dt} = \frac{dV_{ds}}{dt}$$

$$\frac{dV_{ds}}{dt} = \frac{V_{gs,IO} + V_{gs,IO}}{r_g C_{gd}} \Rightarrow$$


$$\boxed{V_{ds} = \frac{(V_{gs,IO} + V_{gs,IO})}{r_g C_{gd}} \cdot t}$$

at the end of this interval, $V_{ds} \approx V_{in}$.

$$\therefore t_{rv} = \left[\frac{V_{in} \cdot r_g \cdot C_{gd}}{V_{gs,IO} + V_{gs,IO}} \right]$$

$$\therefore \boxed{t_{rv} = 102.27 \text{ ns}}$$

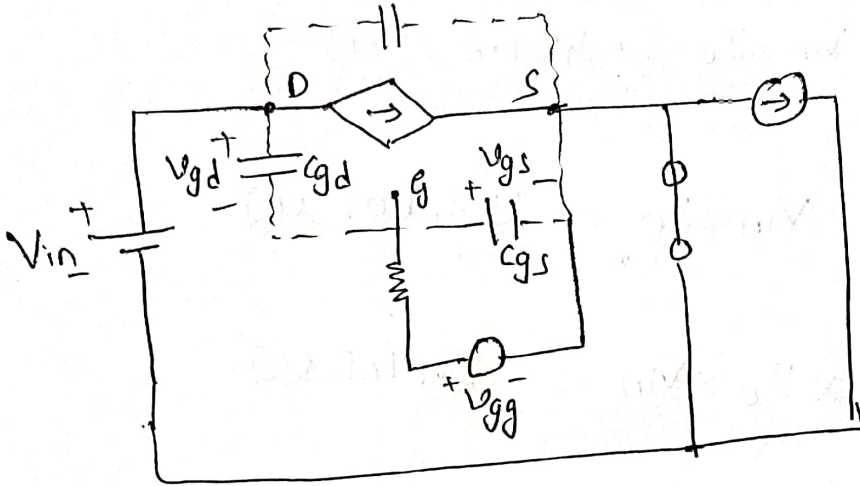f) During current fall interval (t_{fi}): -



$$V_{gg}(t) - i r_g - V_{gs} = 0 \quad (1) \quad V_{gg} - i r_g - V_{gd} - V_{in} = 0 \quad (2)$$

from (1) & (2) $V_{gs} + V_{gd} = V_{in}$

$$i = C_{gs} \frac{dV_{gs}}{dt} + \left[-C_{gd} \frac{dV_{gd}}{dt} \right] = (C_{gs} + C_{gd}) \frac{dV_{gs}}{dt} \quad (3)$$

Substitute (3) in (1),

$$\frac{dV_{gs}}{dt} + \frac{V_{gs}}{r_g(C_{gs} + C_{gd})} = \frac{-V_{gg}}{r_g(C_{gs} + C_{gd})} \quad \left| \begin{array}{l} @ t=0 \\ V_{gs} = V_{gs,IO} \end{array} \right.$$

solution to the above diff. eq. is,

$$V_{gs} = -V_{gg} + [V_{gs,IO} + V_{gg}] e^{-t/\tau}; \quad \tau = r_g(C_{gs} + C_{gd})$$

$$\therefore t_{fi} = -\tau \ln \left[\frac{V_{gs,th} + V_{gg}}{V_{gs,IO} + V_{gg}} \right] \quad \left| \begin{array}{l} @ t=t_{fi} \\ V_{gs} = V_{gs,th} \end{array} \right.$$

$$\therefore t_{fi} = 8.43 \text{ ns}$$

$$(a) E_{ri} = \frac{1}{2} \times t_{ri} \times I_o \times V_{in} = 27.34 \mu J$$

$$(b) E_{fv} = \frac{1}{2} \times t_{fv} \times V_{in} \times I_o = 421.875 \mu J$$

$$(c) E_{rv} = \frac{1}{2} \times t_{rv} \times V_{in} \times I_o = 153.405 \mu J$$

$$(d) E_{fi} = \frac{1}{2} \times t_{fi} \times I_o \times V_{in} = 12.645 \mu J$$

Energy lost during the MOSFET ON time.

$$(e) E_{on} = I_o \times (I_o \times r_{ds(on)}) \times \left[(0.5 T_s) - (t_{don} + t_{ri} + t_{fv}) + t_{doff} \right]$$

$$\therefore E_{on} = 1.23303 \text{ mJ}$$

$$\therefore \text{Total power loss in mosfet} = [E_{ri} + E_{fv} + E_{rv} + E_{fi} + E_{on}] \times f_s$$

$$= \underline{\underline{36.97 \text{ W.}}}$$