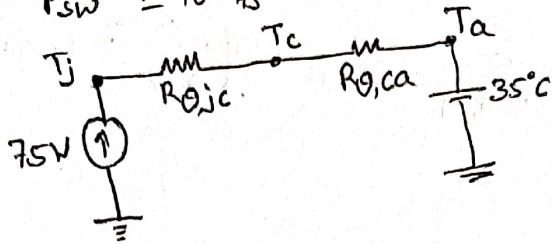


⑤

$$P_{cond} = 50W$$

$$P_{sw} = 10^{-3} \times 25 = 25W$$




$$\frac{T_j - T_a}{(R_{\theta jc} + R_{\theta ca})} = 75W$$

$$\left[\frac{T_j - T_a}{75} \right] - R_{\theta jc} = R_{\theta ca}$$

$$R_{\theta ca} = \left[\frac{150 - 35}{75} \right] - 1 = 0.533 \text{ } ^\circ\text{C/W}$$

⑥

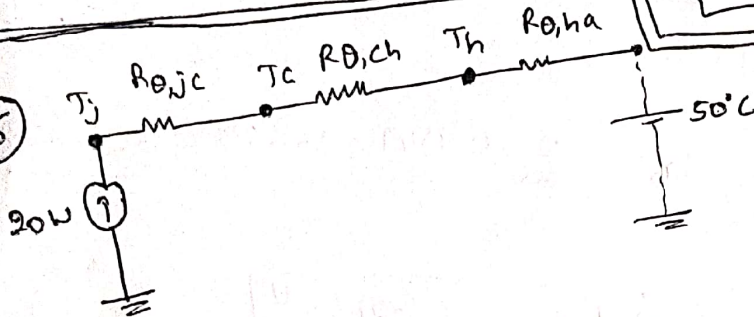

$$\frac{T_j - T_a}{20} = R_{\theta jc} + R_{\theta ch} + R_{\theta ha}$$

$$\frac{T_j - 50}{20} = 0.5 + 1.5 + R_{\theta ha}$$

$$\therefore R_{\theta ha} = \left[\frac{100 - 50}{20} \right] - 0.5 - 1.5$$

$$R_{\theta ha} = 0.5 \text{ } ^\circ\text{C/W}$$

$$\text{Now, } T_c = T_j - (R_{\theta jc} \times 20W)$$

$$T_c = 100 - 10 = 90^\circ\text{C}$$

⑦

$$C = - \frac{(T_{s12})}{R \ln \left[\frac{V_{min}}{V_{max}} \right]} = - \frac{(T_{s12})}{\left[\frac{V_o^2}{P} \right] \ln \left[\frac{V_{min}}{V_{max}} \right]}$$

$$= 2.098 \text{ mF}$$

$$\text{for (a)} \quad C = - \frac{20 \times 10^{-3}}{\left[\frac{\left(\frac{325.269 + 310.269}{2} \right)^2}{500} \right] \ln \left[\frac{310.269}{325.269} \right]}$$

$$\text{for (b)} \quad C = - \frac{10 \times 10^{-3}}{\left[\frac{\left(\frac{325.269 + 310.269}{2} \right)^2}{500} \right] \ln \left[\frac{310.269}{325.269} \right]} = 1.0488 \text{ mF}$$

$$\text{for (c)} \quad C = - \frac{(20 \times 10^{-3}) \div 6}{\left[\frac{\left(\frac{565.685 + 550.685}{2} \right)^2}{500} \right] \ln \left[\frac{550.685}{565.685} \right]} = 199.046 \text{ } \mu\text{F}$$



⑧ output voltage of a q-pulse rectifier

$$V_{or} = V_m \frac{q}{\pi} \sin\left(\frac{\pi}{q}\right) \left[1 - \sum_{n=9, 2q, \dots}^{\infty} \frac{2}{n^2-1} \cos\left(\frac{n\pi}{q}\right) \cos(n\omega t) \right]$$

for $q=6$,

$$V_{or} = 0.9549 V_m \left[1 + \frac{2}{35} \cos(6\omega t) - \frac{2}{143} \cos(12\omega t) + \dots \right]$$

first dominant non-DC frequency component voltage $V_{or6} = \frac{2}{35} \cdot 0.9549 \times 565.685 = \underline{\underline{30.867V}}$

40dB attenuation by LC filter $\therefore V_{out,6} = 0.30867V$

Load is 100kW $\therefore R = \frac{V_o^2}{P} = \frac{(0.9549 \times 565.685)^2}{100 \times 10^3} = \underline{\underline{2.9179\Omega}}$

$$\therefore \frac{1}{I_o} = \frac{0.9549 \times 565.685}{100 \times 10^3} \Rightarrow \boxed{I_o = 185.126A}$$

$$\therefore \omega L = \frac{30.867 + 0.30867}{\left[\frac{0.2 \times 185.126}{2} \right]} = 1.68H. \Rightarrow \boxed{L = 0.9mH}$$

$$\text{now, } \frac{V_o(s)}{V_i(s)} = \frac{1/LC}{s^2 + \frac{1}{RC}s + \frac{1}{LC}} = \frac{\omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

$$20 \log_{10} \left| \frac{V_o(s)}{V_i(s)} \right| = 20 \log_{10} \left| \frac{1}{\left[1 - \frac{\omega^2}{\omega_n^2} \right] + j \frac{2\xi\omega}{\omega_n}} \right| = -40dB.$$

$$\frac{\omega^4}{\omega_n^4} - 2 \frac{\omega^2}{\omega_n^2} + 4\xi^2 \frac{\omega^2}{\omega_n^2} + 1 = 10,000$$

$$\left[\left(\frac{\omega^2}{\omega_n^2} \right)^2 + (4\xi^2 - 2) \left(\frac{\omega^2}{\omega_n^2} \right) - 9,999 \right] = 0$$

$$\frac{\omega^2}{\omega_n^2} = \frac{-(4\xi^2 - 2) \pm \sqrt{(4\xi^2 - 2)^2 + 39,996}}{2}$$

$$\text{for } \xi = 0 \Rightarrow \frac{\omega^2}{\omega_n^2} = 101$$

$$\text{for } \xi = 0.5 \Rightarrow \frac{\omega^2}{\omega_n^2} = 100.49$$

$$\boxed{\text{for } \xi = 0.707 \Rightarrow \frac{\omega^2}{\omega_n^2} = 100}$$

$$\text{for } \xi = 1 \Rightarrow \frac{\omega^2}{\omega_n^2} = 99.$$

$$\omega_n^2 = \frac{(2\pi \times 300)^2}{100} \Rightarrow \boxed{\omega_n = 2\pi \times 30}$$

$$\text{Now, } \omega_n = \frac{1}{\sqrt{LC}} = 2\pi \times 30.$$

$$C = \frac{1}{(2\pi \times 30)^2 \times L} = \frac{1}{(2\pi \times 30)^2 \times 1.68 \times 10^{-3}}$$

$$\boxed{C = 16.75 \mu F} = 31.2 \text{ mF.}$$

9

$$② \quad P_{\text{Load}} = \frac{V_o^2}{R} \Rightarrow V_o = \sqrt{P_{\text{Load}} \times R} = \sqrt{3900 \times 37}$$

$$\therefore V_{\text{out}} = 379.8684 \text{ V}$$

$$① \quad V_{\text{rms}} I_{\text{rms}} = 3900 \text{ W}$$

$$I_{\text{rms}} = \frac{3900}{230} = 16.9565 \text{ A}$$

$$\therefore I_{\text{max}} = 23.9801 \text{ A}$$

$$③ \quad I_{\text{out}} = \sqrt{\frac{P_{\text{Load}}}{R}} = \sqrt{\frac{3900}{37}} = 10.2667 \text{ A}$$

10

Now, w.k.t the pfc shapes the inductor current like

$$I_{\text{in}} = I_L = I_m |\sin \omega t|$$

for boost converter, $\frac{I_{\text{out}}}{I_{\text{in}}} = (1-D) = \frac{I_{\text{out}}}{I_m |\sin \omega t|}$

Now, CCM

$$V_{\text{out}} = \frac{V_{\text{in}}}{1-D} = \frac{V_m |\sin \omega t|}{\frac{I_o}{I_m |\sin \omega t|}}$$

$$V_{\text{out}} = \frac{V_m \cdot I_m}{I_o} |\sin^2 \omega t|$$

$$V_{\text{out}} = \frac{V_m I_m}{2 I_o} - \frac{V_m I_m}{2 I_o} |\cos(2\omega t)|$$